

Electrical Engineering



Electronics and Communication Engineering

Instrumentation Engineering

Network Theory




Lecture No. 05

Basics of Network Theory

By- Pankaj Shukla sir

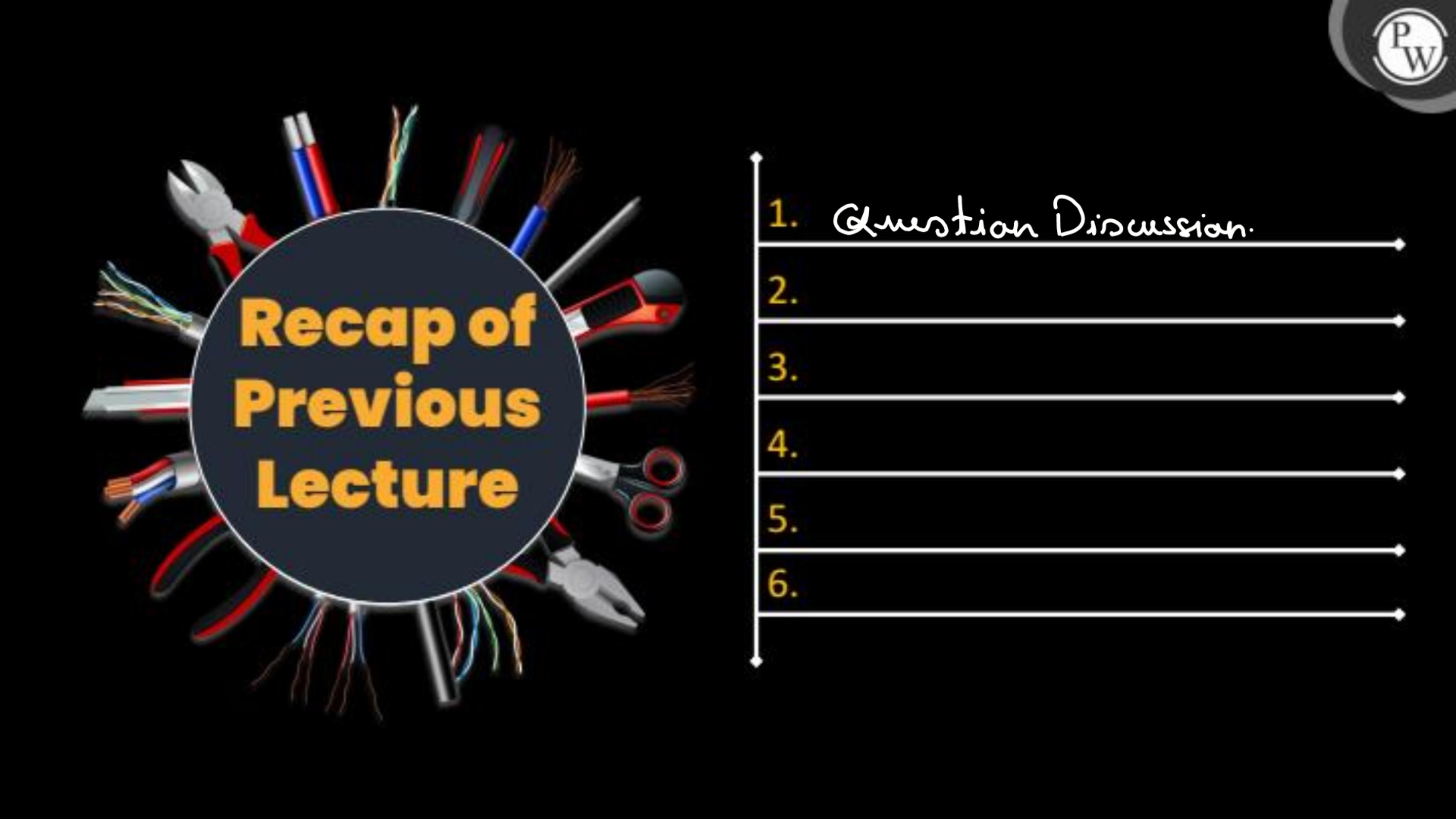

The background of the slide features a dark, slightly textured surface. Overlaid on it are several electrical components: a pair of red-handled pliers on the left, a black microphone with a red and white cable in the center, and a coiled black power cord with multiple colored (red, blue, green) wires extending from its end. A large, semi-transparent circular overlay contains the main text.

Recap of Previous Lecture

1. Question Discussion.

2.

3.

4.

5.

6.




Topics to be Covered

1. Question Discussion.
2. Series & Parallel operation.
- 3.
- 4.
- 5.
- 6.

Question


- Inspection Method - QL.

The value of I_o _____ A.

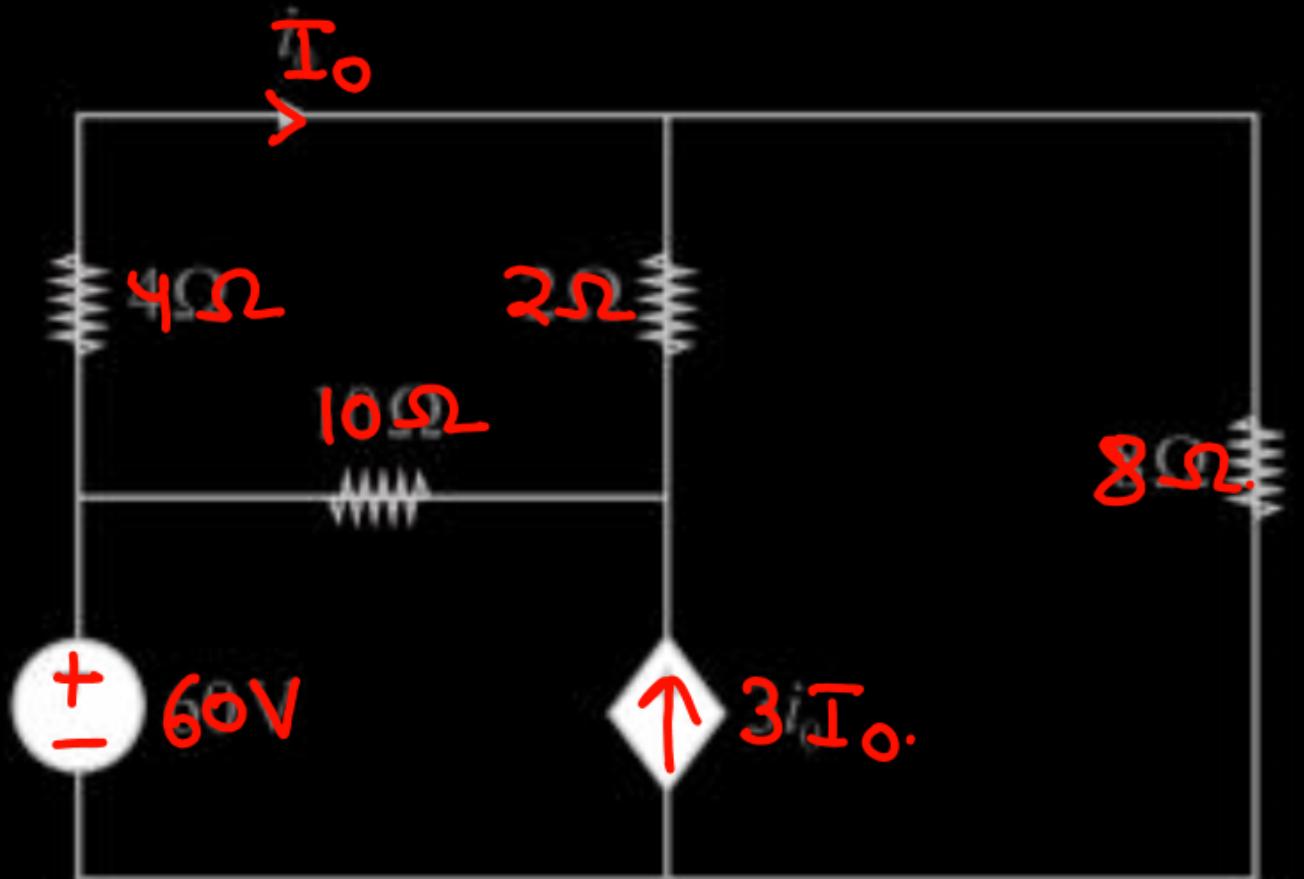

Question

The value of I_0 _____ A.

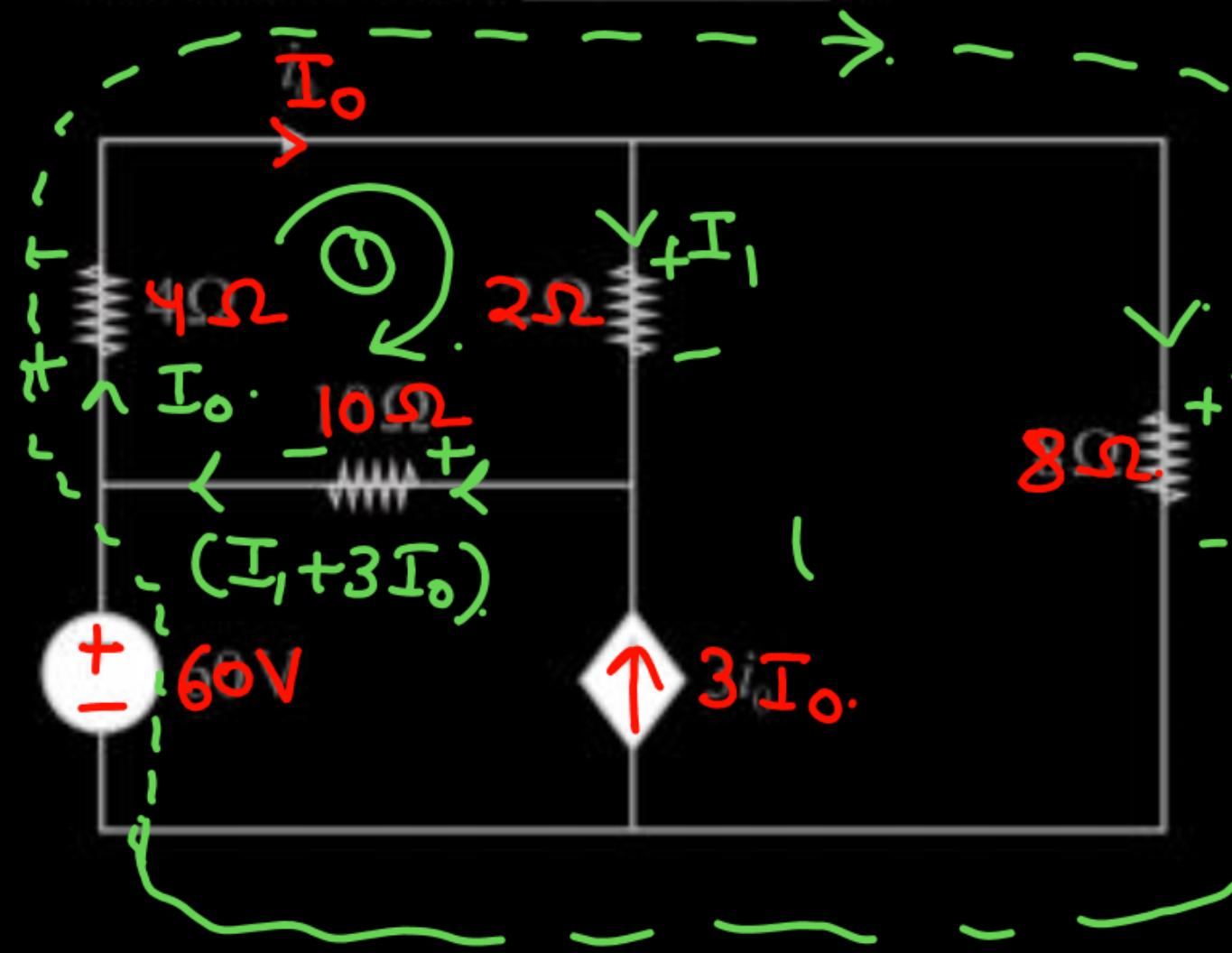

$$\left[I_0 = \frac{60 \times 12}{416} = 1.7307 \right] \boxed{A.} \quad I_0(34 \times 8 + 12 \times R) = 0 + 60 \times 12.$$

• KVL - 01.

$$4 \times (I_0) + 2 \times I_1 + 10 \times (I_1 + 3I_0) = 0$$

$$\boxed{[34I_0 + 12I_1 = 0]} \quad \textcircled{1}$$

KVL - 02.

$$60 = 4I_0 + 8 \times (I_0 - I_1)$$

$$12I_0 - 8I_1 = 60 \quad \textcircled{2}$$


$$8 \times [34I_0 + 12I_1 = 0]$$

$$12 \times [12I_0 - 8I_1 = 60]$$

Question

6 In the circuit shown in figure, if the current through the $2\ \Omega$ resistor is zero, the power delivered by current source of $1A$ is


• Inspection Method - ① .

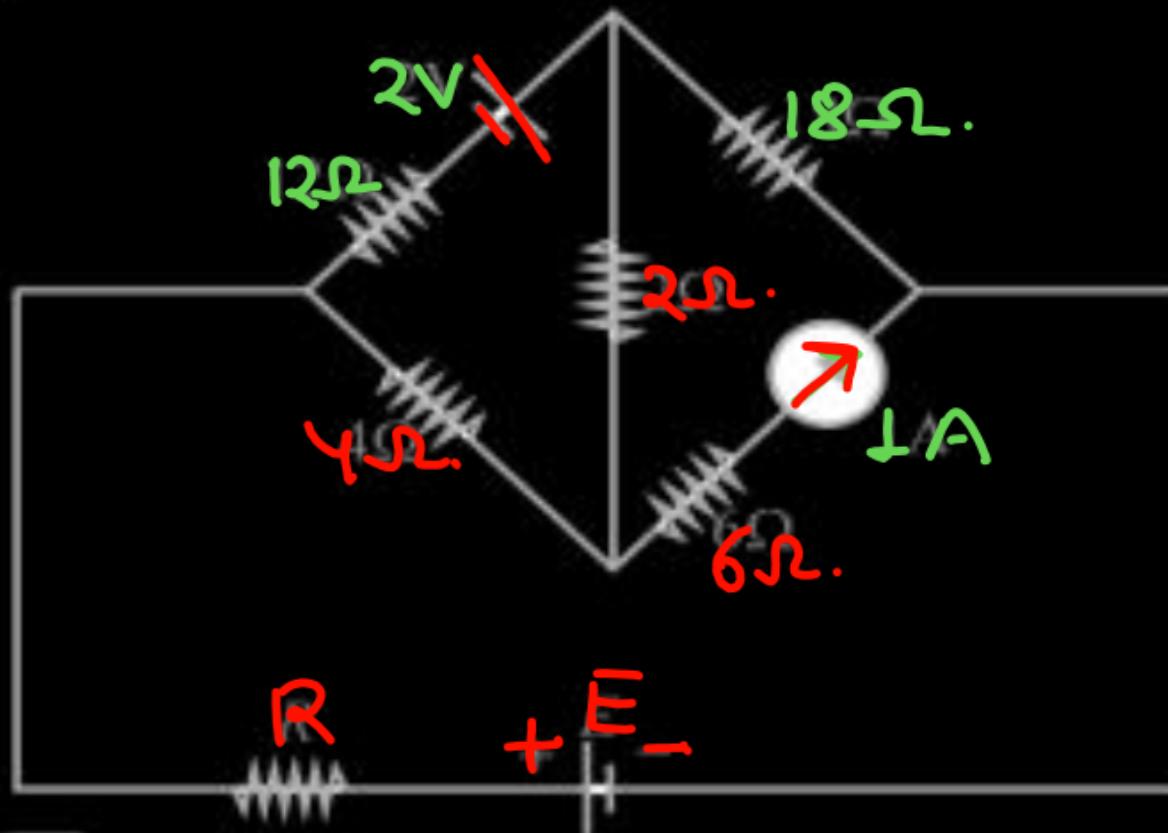

- A 3 W
- B -3 W
- C 6 W
- D -8 W

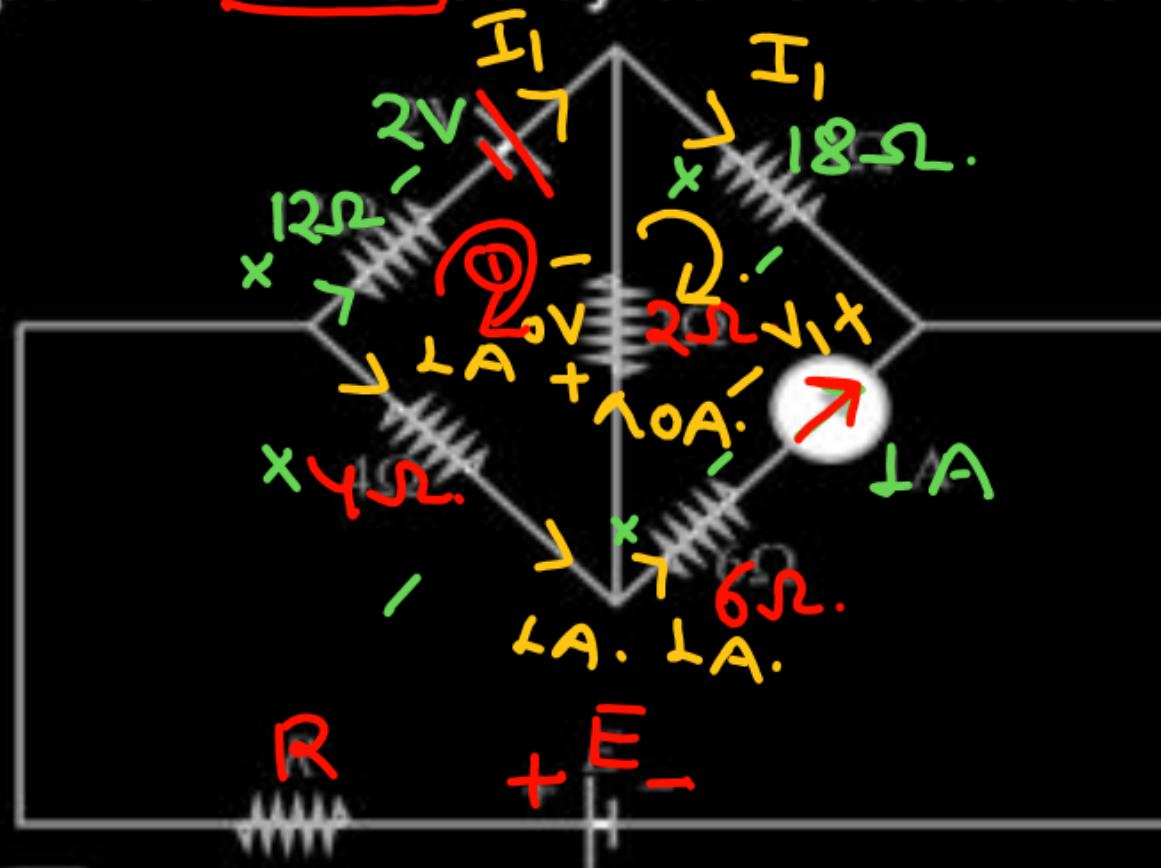Question

6 In the circuit shown in figure, if the current through the 2 ohm resistor is zero, the power delivered by current source of 1A is



- A 3 W
 - B -3W
 - C 6 W
 - D -8W

- Inspection Method - 01 ! $P_{LA} = V_t \times L$.

KVL →

$$4 \times 1 + 2 = 12 I_1$$

$$|RI_1| = 6$$


$$[I_1 = \frac{1}{2} A] = 0.5 A$$

$\kappa \nabla L \rightarrow$

$$\sqrt{1+18I_1} = 6x_1.$$

$$V_1 = 6 - 18I_1 = 6 - 18 \times 0.5 = (-3 \text{ volt})$$

— 1 —

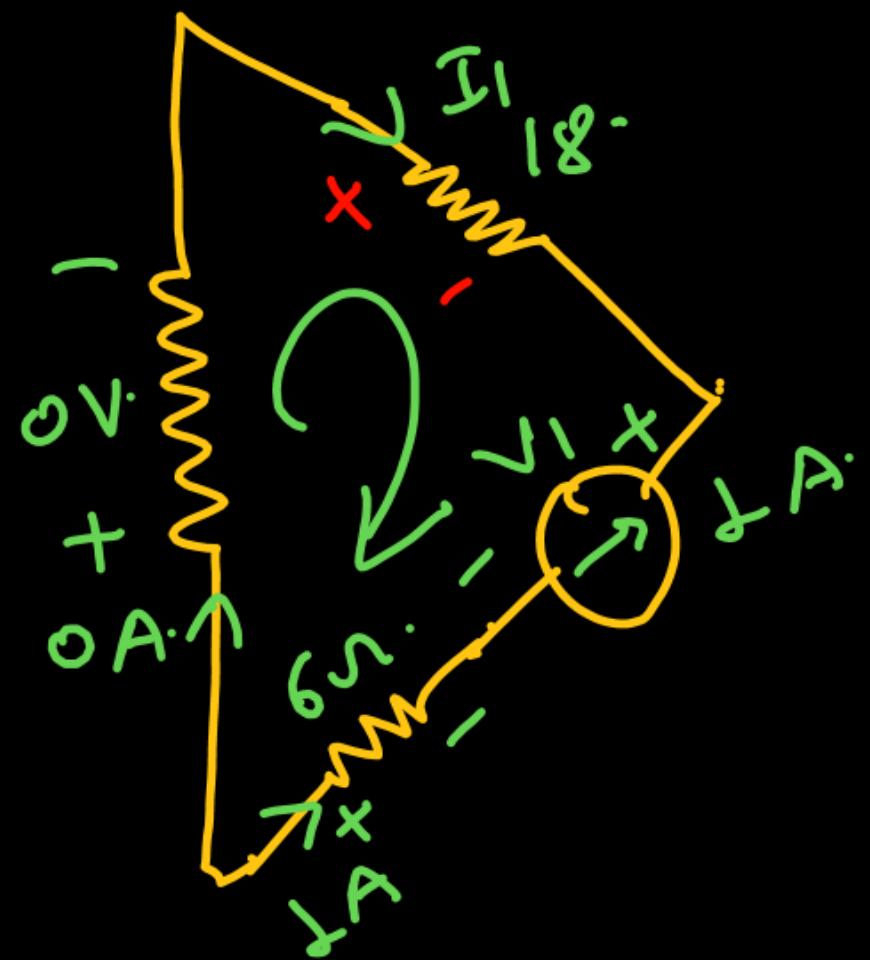


$$6 \times 1 = V_1 + 18 I_1$$

$$\boxed{V_1 = 6 - 18 I_1}$$

Question

The circuit is shown below find the value of V & I . • (Inspection Method).


20V

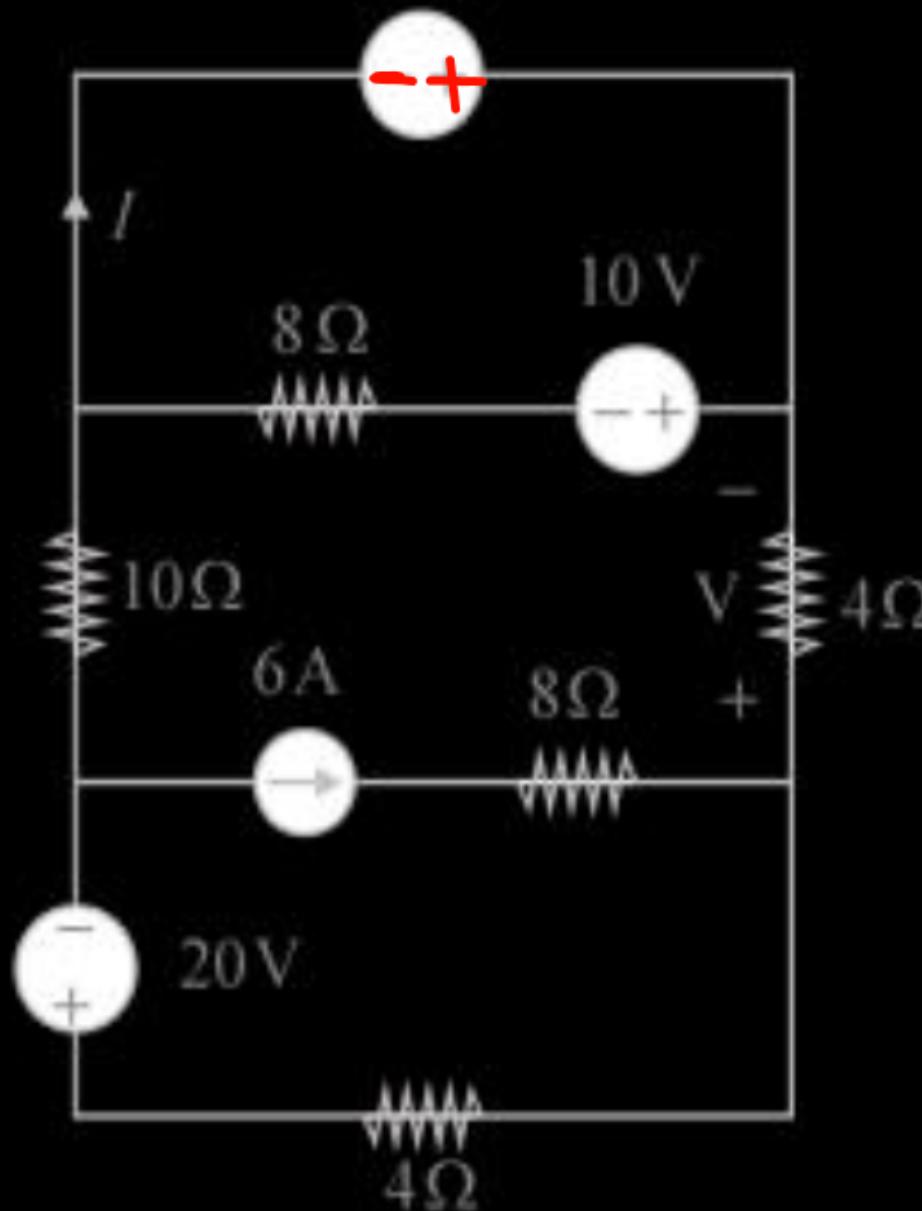

• Two Equation

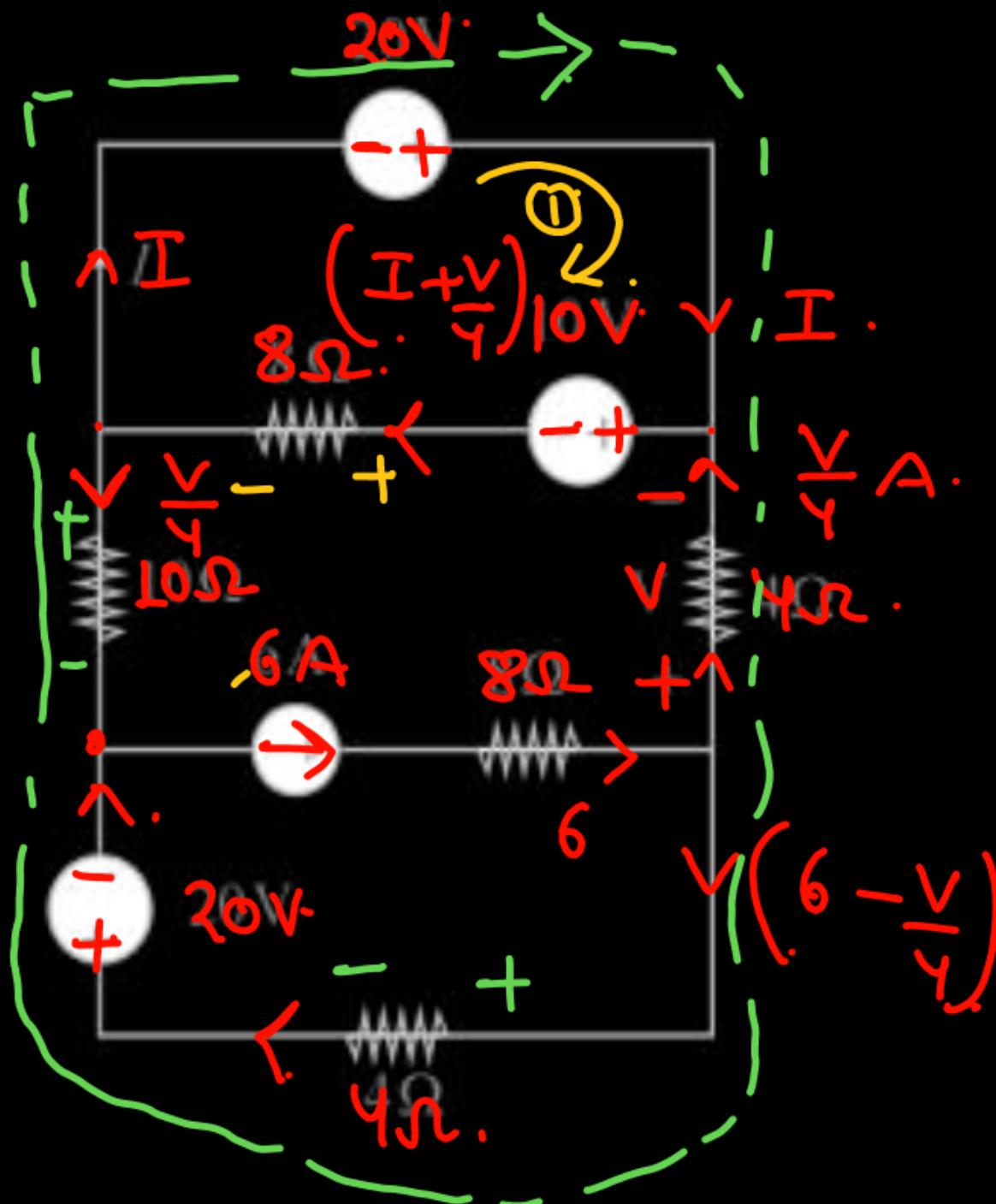Question

The circuit is shown below find the value of V & I . • (Inspection Method).



- Two equations.
- KVL - 01.

$$20 = 10 + 8 \times \left(I + \frac{V}{4} \right)$$

$$8I + 2V = 10$$

$$\left[4I + V = 5 \right]$$

$$KVL - 02.$$

$$20 + V + \frac{V}{4} \times 10 = 4 \times \left(6 - \frac{V}{4} \right) + 20$$

$$V \left(1 + \frac{10}{4} + 1 \right) = 24$$


$$\left[V = \frac{24}{4.5} = 5.33 \text{ volt} \right].$$

$$\cdot \left[I = \frac{5 - V}{R} = \frac{5 - 5.33}{4} = -0.0833 \text{ A} \right].$$

Inspection method

#Q. In the given circuit, the current I_x (in mA) is _____.


[GATE-2024-1M]

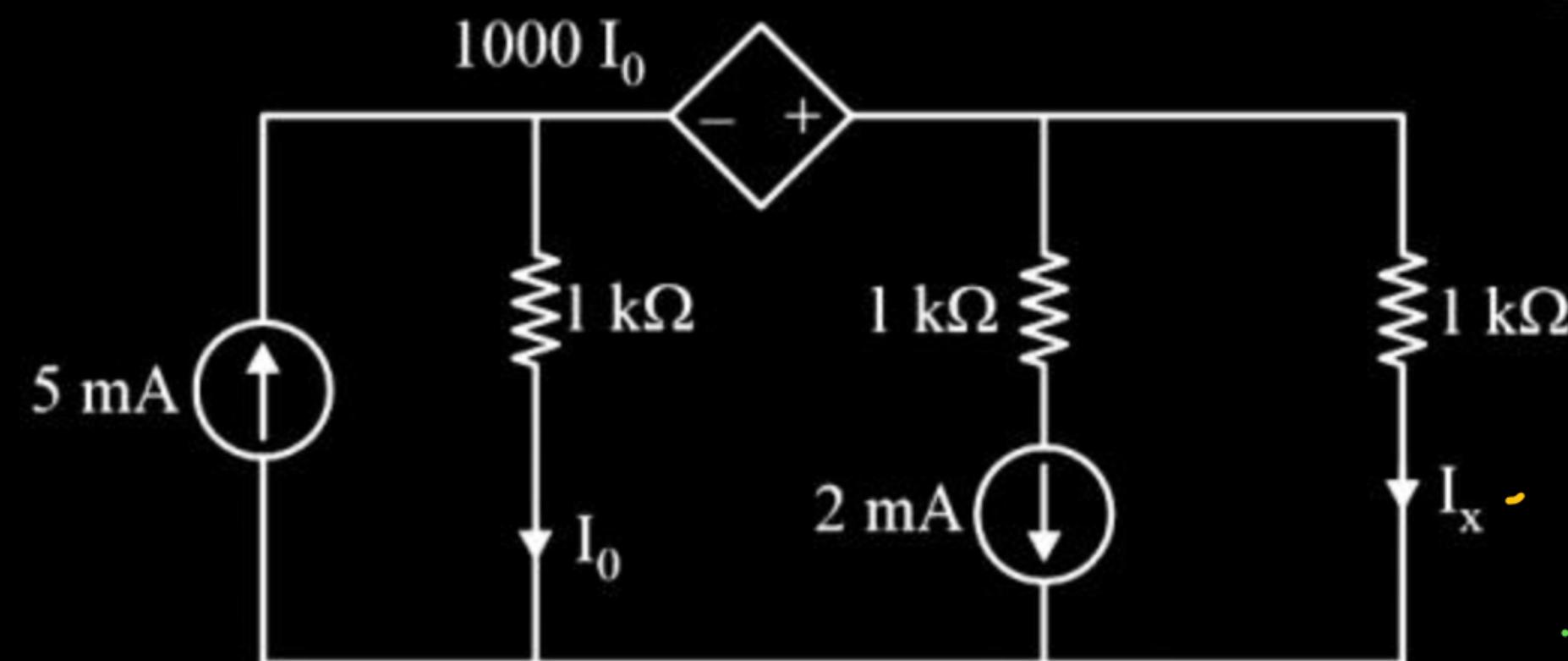

Inspection method

#Q. In the given circuit, the current I_x (in mA) is _____.

[GATE-2024-1M]

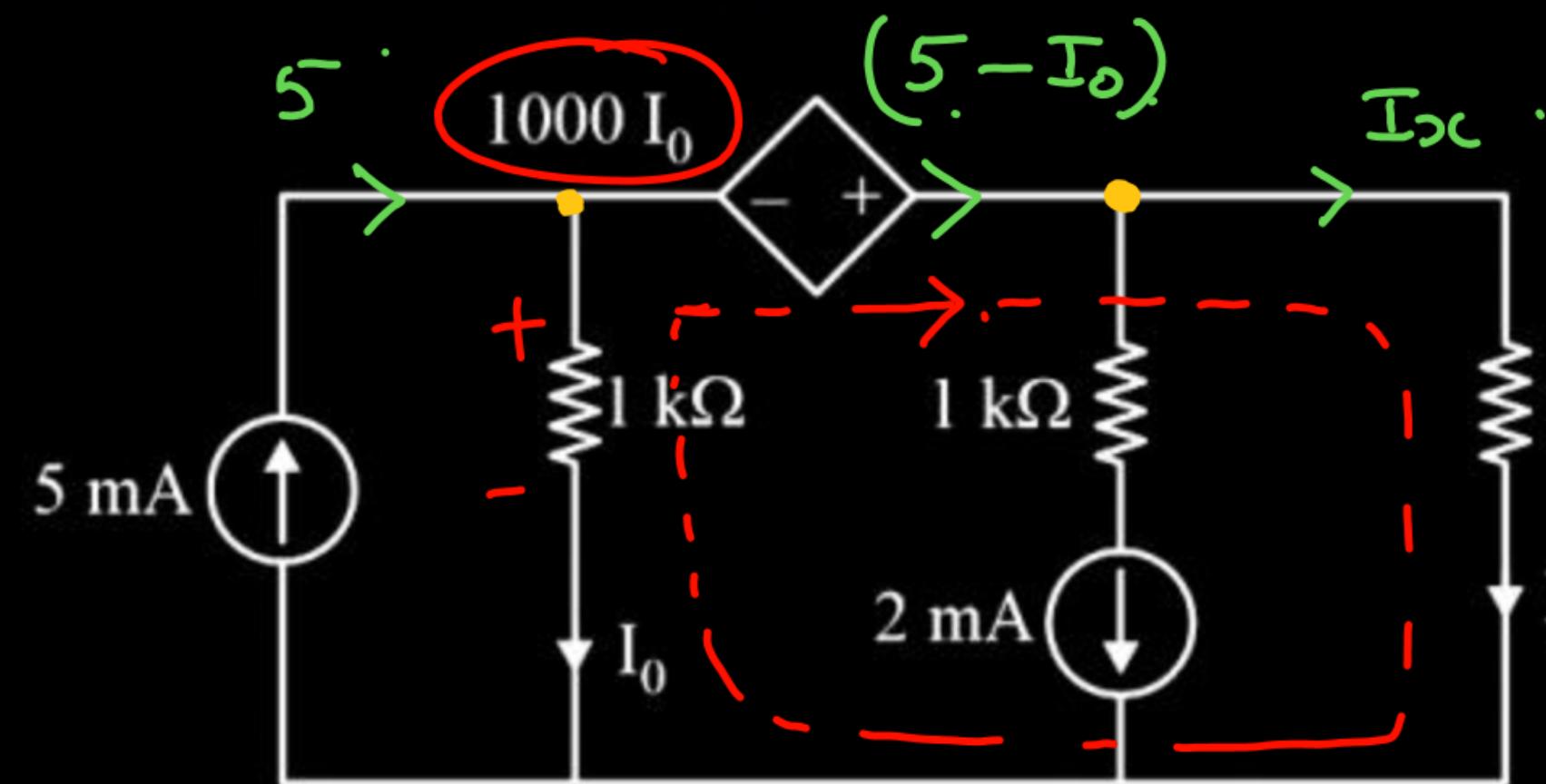

$$\begin{aligned} & [2I_0 - I_x = 0] \\ & 5 - I_0 = I_x + 2 \\ & I_{DC} + I_0 = 3 \text{ mA} \end{aligned}$$

$$1 \times 10^3 \times I_0 + 1000 I_0 = 1000 \times I_x$$

$$I_0 + I_0 = I_x, \quad 2I_0 = I_{DC}$$

$$2I_o - I_x = 0$$

$$2 \times [I_o + I_x = 3 \times 10^{-3}]$$

$$I_x (-1 - 2) = 0 - 6 \times 10^{-3}$$

$$[I_x = 2 \text{ mA}]$$

$$\bullet \quad 2I_o = I_x$$

$$[I_o = \frac{I_x}{2} = 1 \text{ mA}]$$

Note: ① if in a circuit, we have.

$$R \rightarrow k\Omega$$

$$I \rightarrow m A$$

Independent Sources →

→ Voltage Source → Volt.

↳ Current Source → mA.

Then no need to convert milli into A or Ω . Apply directly.

② if the circuit contains:

$$R \rightarrow k\Omega, I \rightarrow mA$$

Independent Sources →

Voltage → Volt.

Current → mA.

Dependent Source →

Voltage.

Current Source.


} unit is not mentioned.

Then convert milli \rightarrow (A) .
or. (Ω)


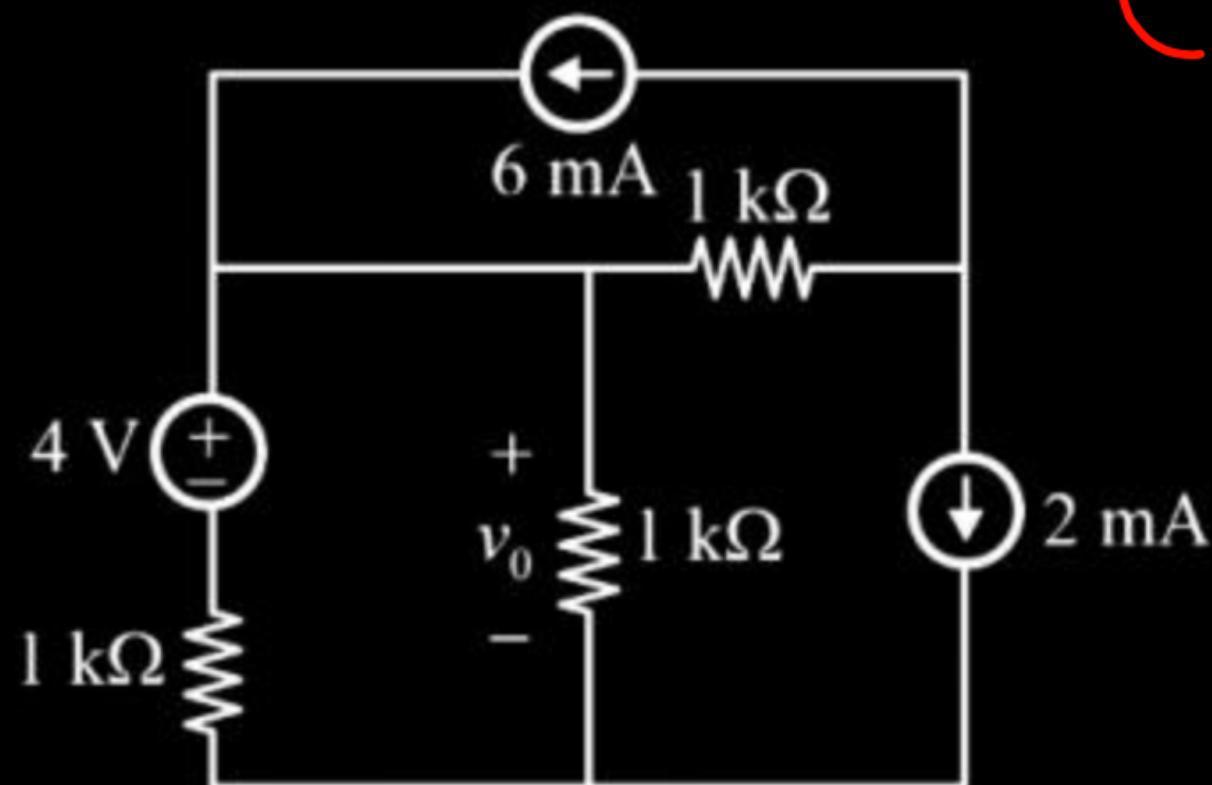
#Q. Consider the circuit shown in the figure.

Find $V_o \rightarrow$
(Inspection method).




The value of v_0 (rounded off to one decimal places) is _____ V.

[GATE-2021-1M]

#Q. Consider the circuit shown in the figure.

Find $V_o \rightarrow$

(Inspection method).

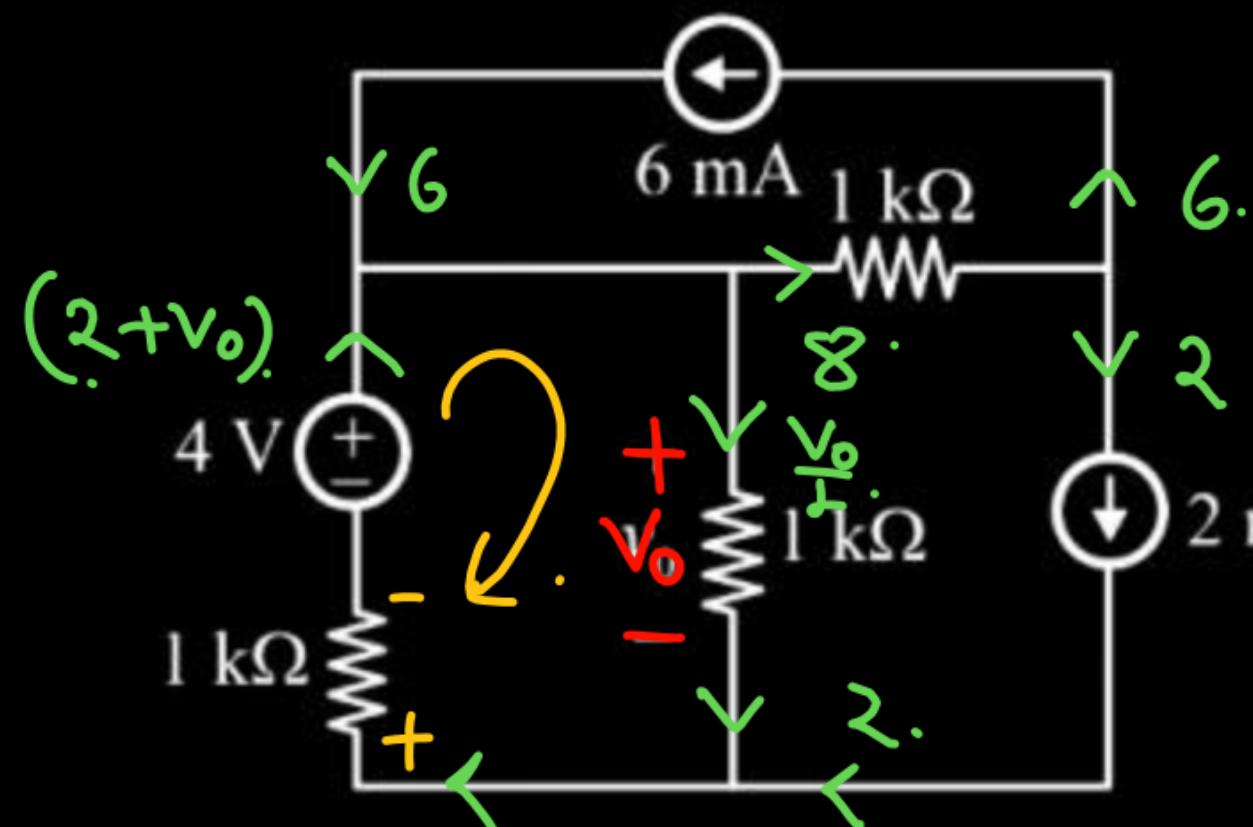

$$\bullet V = V_o + 1 \times (2 + V_o)$$

$$V = V_o + 2 + V_o$$

$$2V_o = 2$$

$$V_o = (\perp \text{ volt})$$



The value of V_o (rounded off to one decimal places) is _____ V.

[GATE-2021-1M]

Topic: (Series & Parallel operation)

① Series operation:

(a) Resistors:

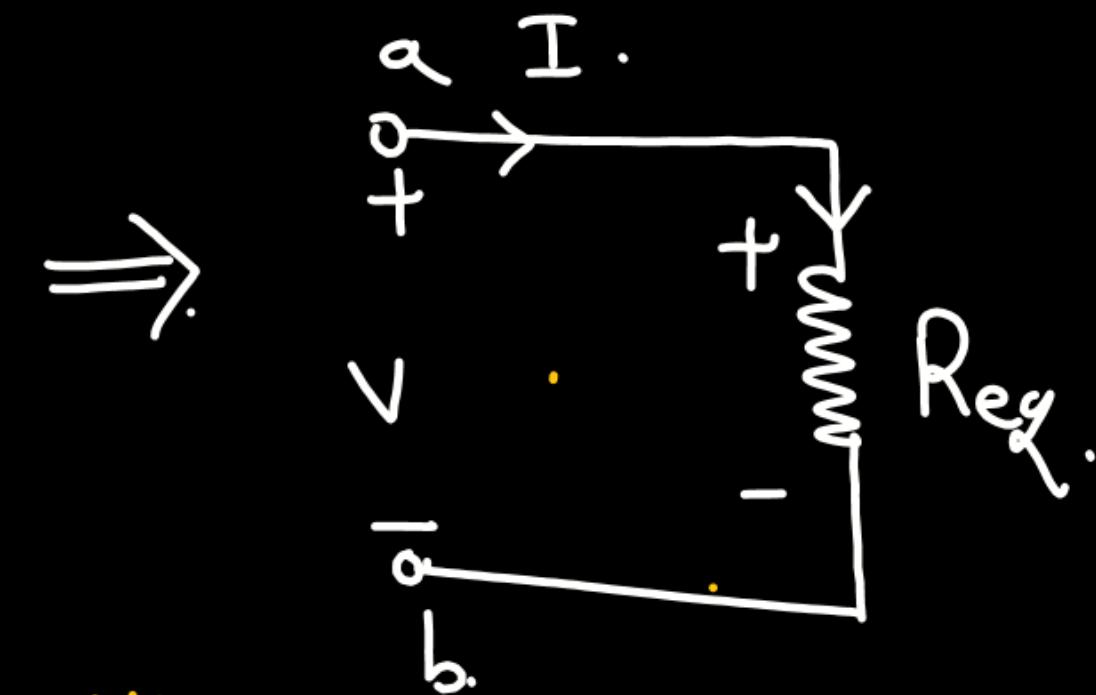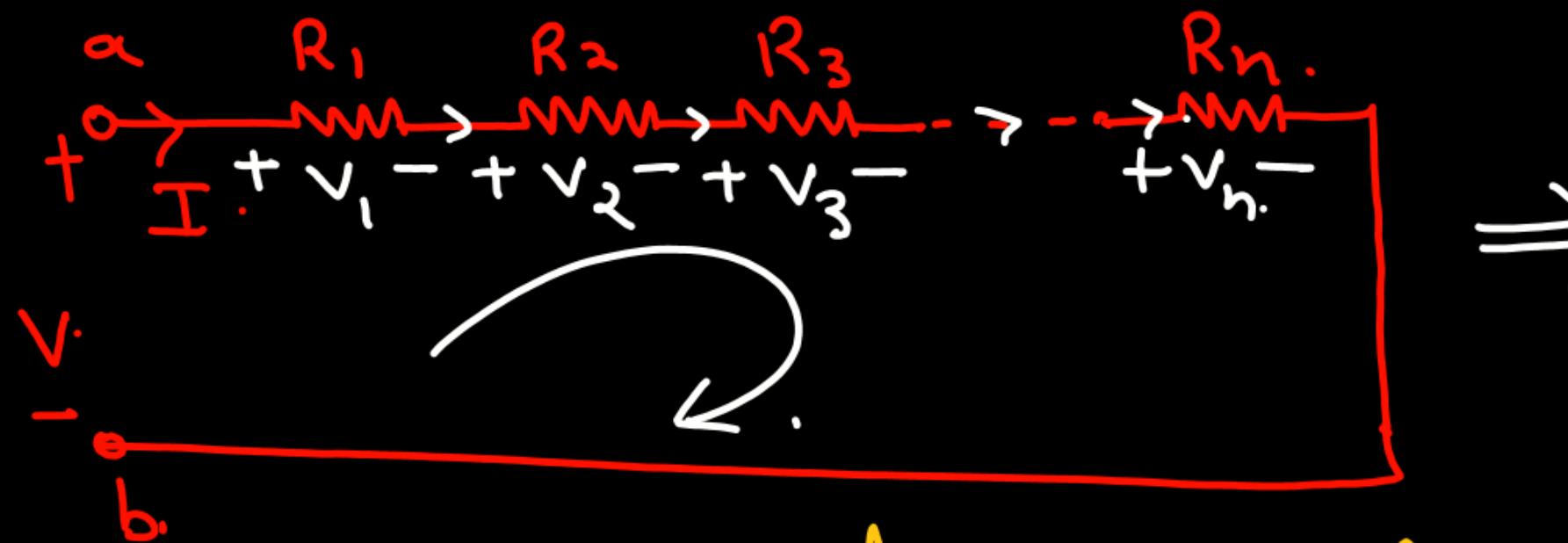

- Current in each element will always remain same.
- Voltage across each resistor may or may not remain same.

$$\bullet V = I \cdot R_{\text{eq}}. \quad \left[\frac{V}{I} = R_{\text{eq}} \right]$$

- Applying KVL,

$$V = V_1 + V_2 + V_3 + \dots + V_n.$$

$$V = I R_1 + I R_2 + I R_3 + \dots + I R_n.$$

$$\left[\frac{V}{I} = R_{eq} = R_1 + R_2 + R_3 + \dots + R_n \right]$$

- Hence, there is a concept known as Voltage Division Rule (VDR). Comes into picture that is used to calculate the voltage across each resistor connected in series.

$$V_1 = I \cdot R_1 = V \cdot \left(\frac{R_1}{R_{eq}} \right)$$

$$V_2 = I \cdot R_2 = V \cdot \left(\frac{R_2}{R_{eq}} \right)$$

$$V_h = I R_h = V \cdot \left(\frac{R_h}{R_{eq}} \right).$$

Now, voltage across any resistor (x) .

$$\left. \begin{aligned} V_x &= V \times \frac{R_x}{R_{\text{eq}}} \\ \therefore x &= 1, 2, 3, \dots n. \end{aligned} \right] \rightarrow (\text{General expression of VDR})$$

- if all resistors are of same value


$$[R_1 = R_2 = R_3 = R_4 = \dots = R_n = R]$$

$$[R_{\text{eq}} = [R + R + R + \dots + R] = nR]$$

$$\left. \begin{aligned} V_x &= V \times \frac{R}{nR} = \frac{V}{n} \end{aligned} \right]$$

(b) Series operation of Voltage Sources:

(1) Ideal sources. (Simply Apply KVL).



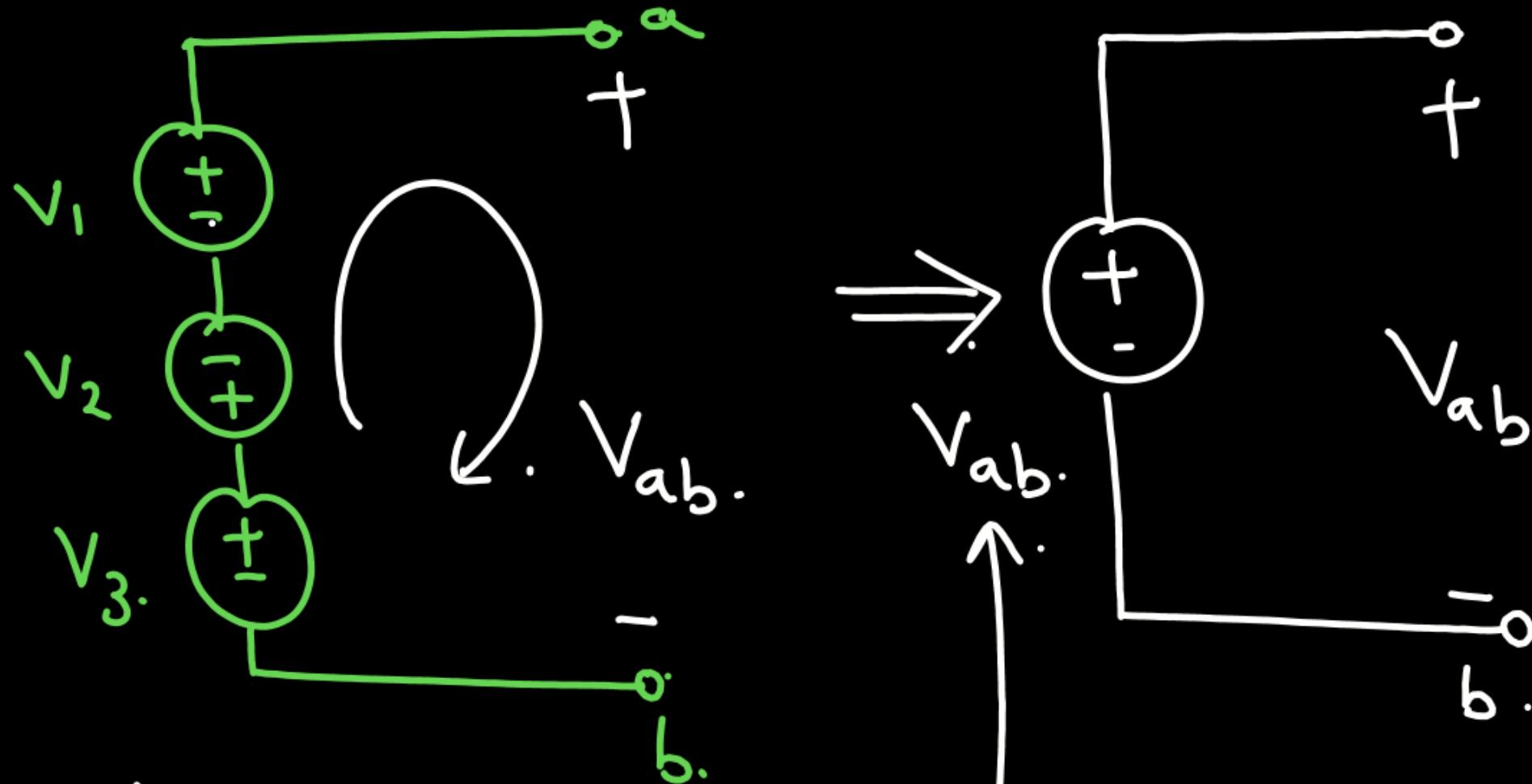


$$V_3 + V_1 = V_2 + V_{ab.}$$

$$(V_{ab} = V_1 - V_2 + V_3)$$

②

Practical Voltage Source:

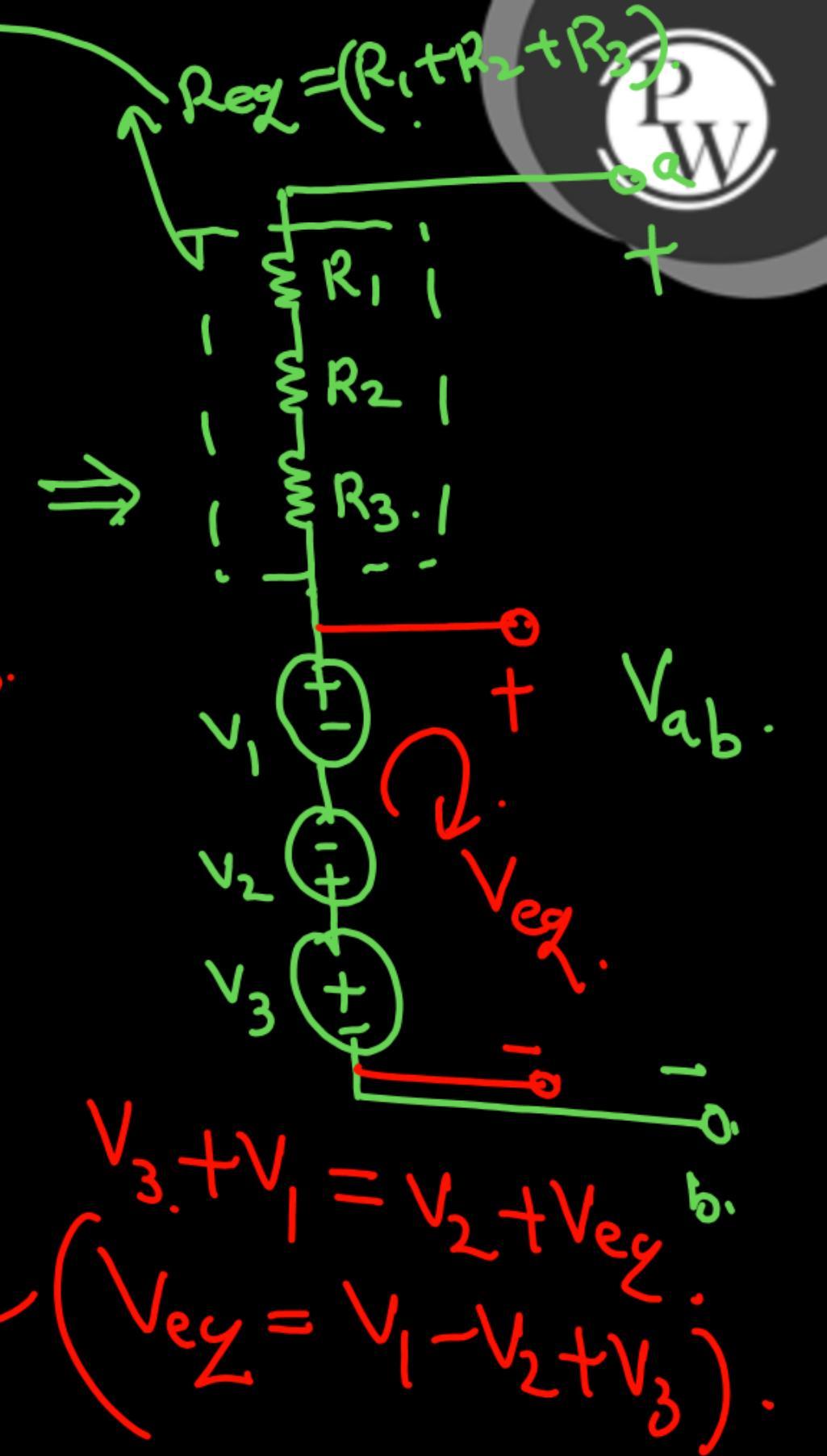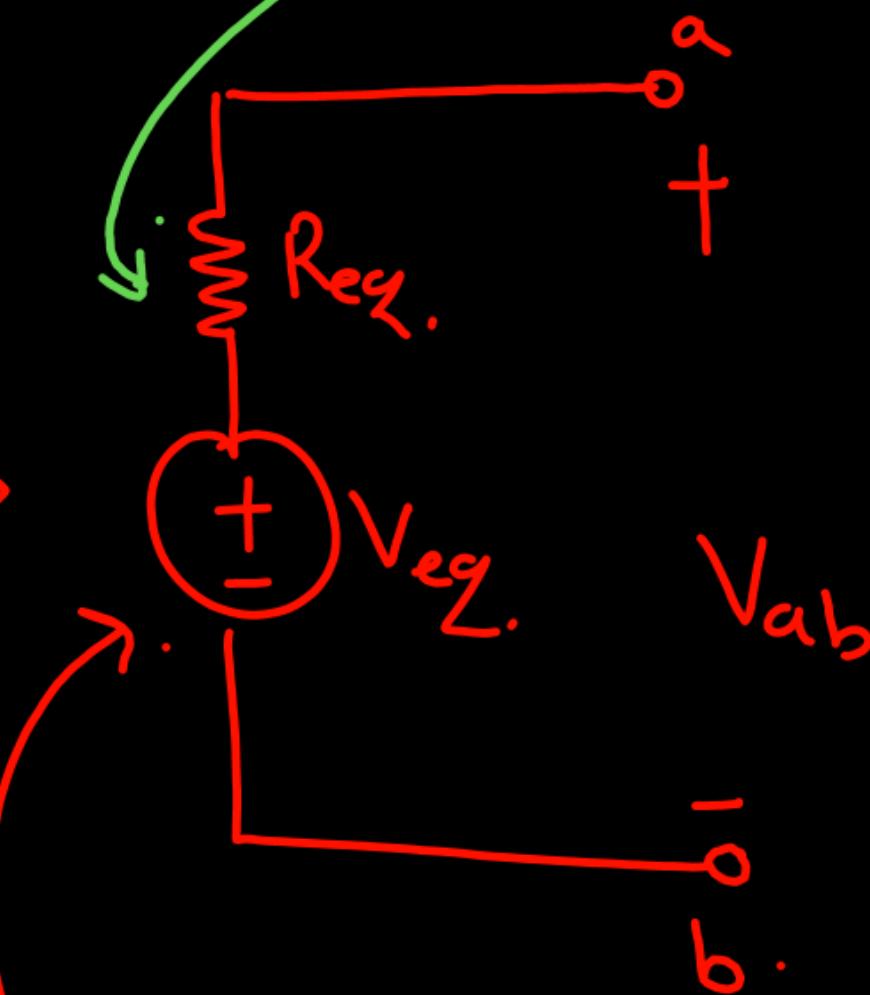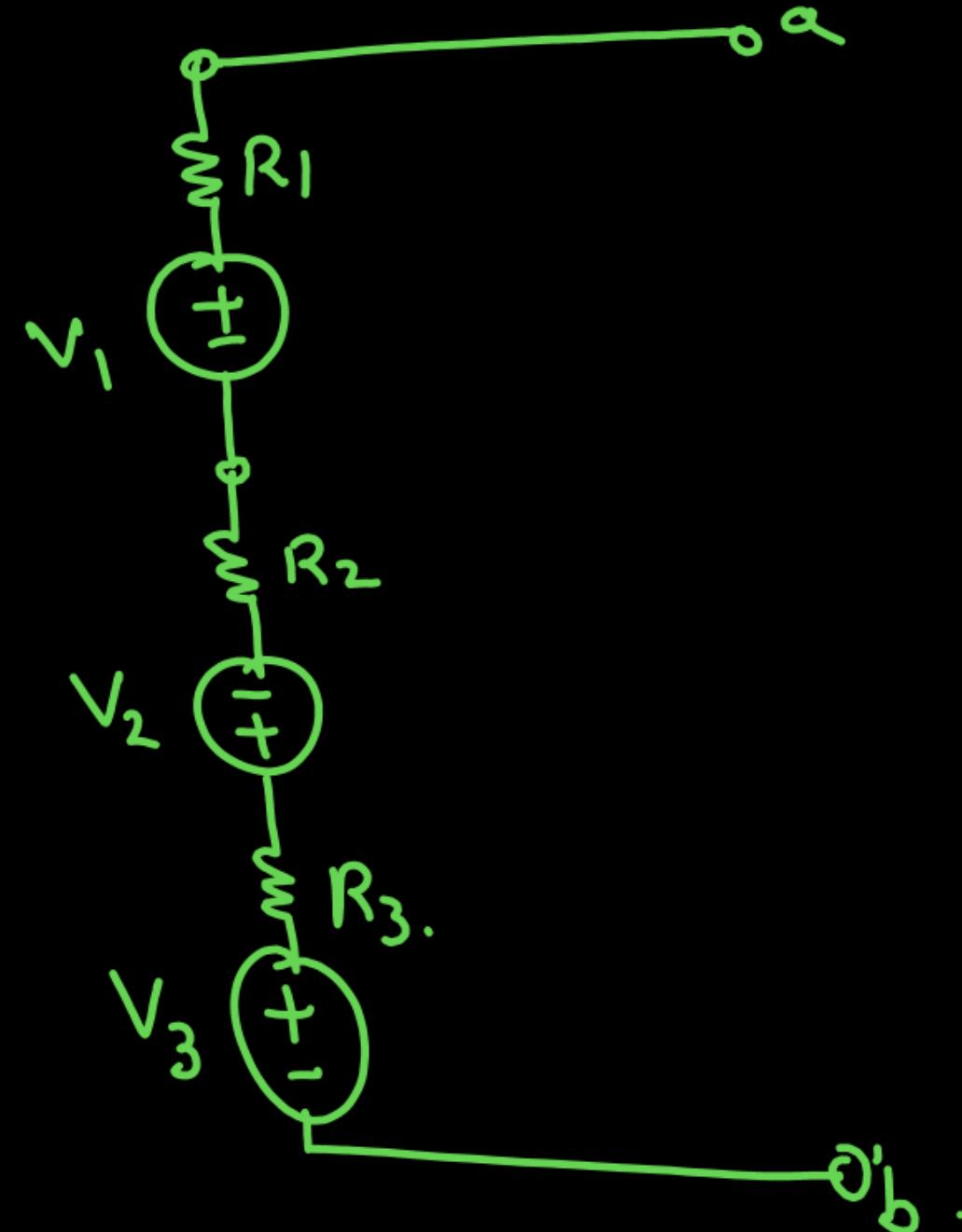


(c) Series operation of current sources:

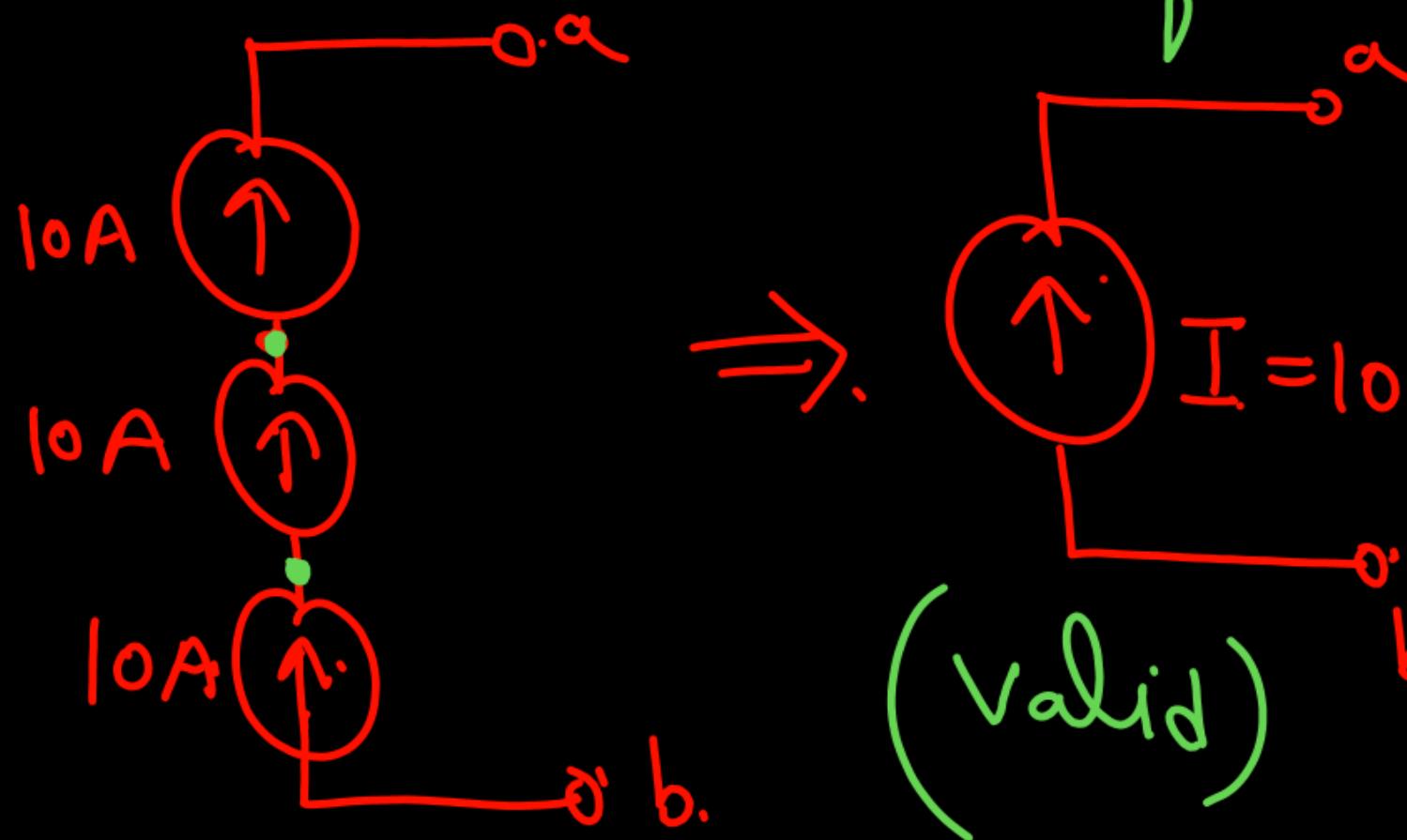
(1) Ideal current sources:

"For Series operation of Ideal current sources."


/ the magnitude & Direction of all Ideal current sources Must be Same so that KCL will be satisfied."




(Valid)

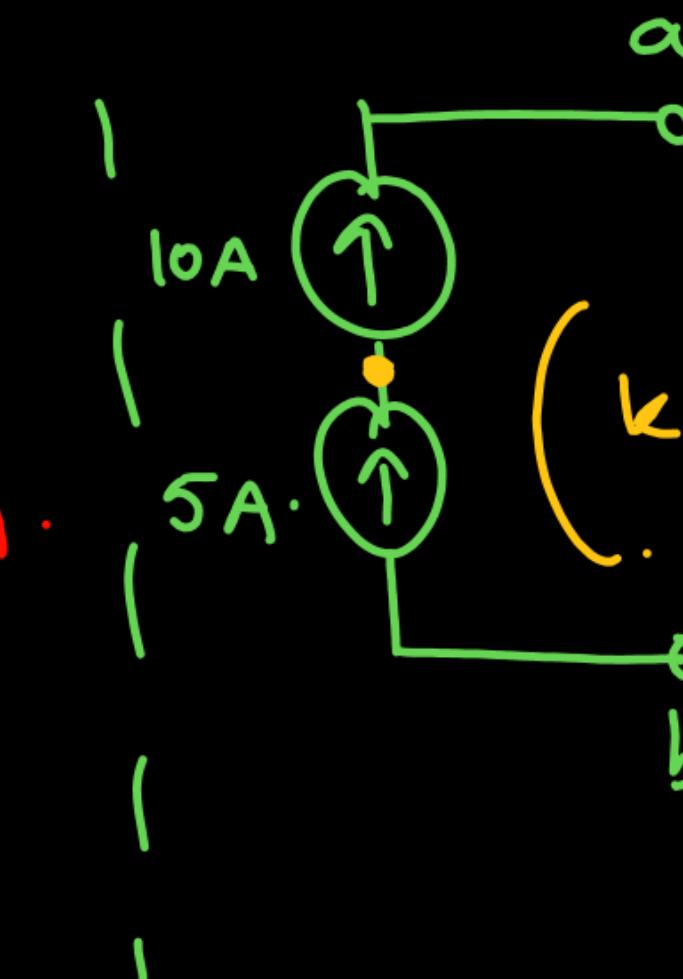

(KCL failed Hence it is not a valid ckt)

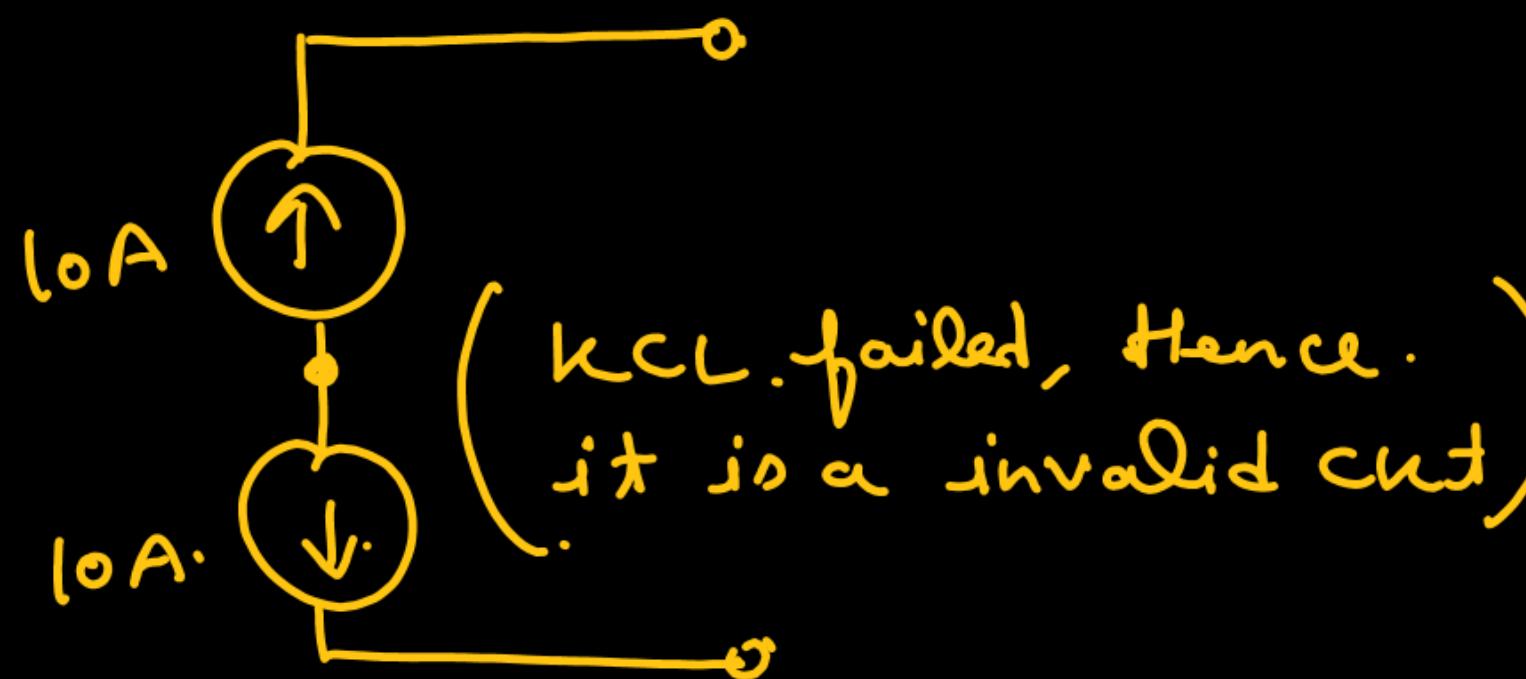

(2) Practical Current Sources:


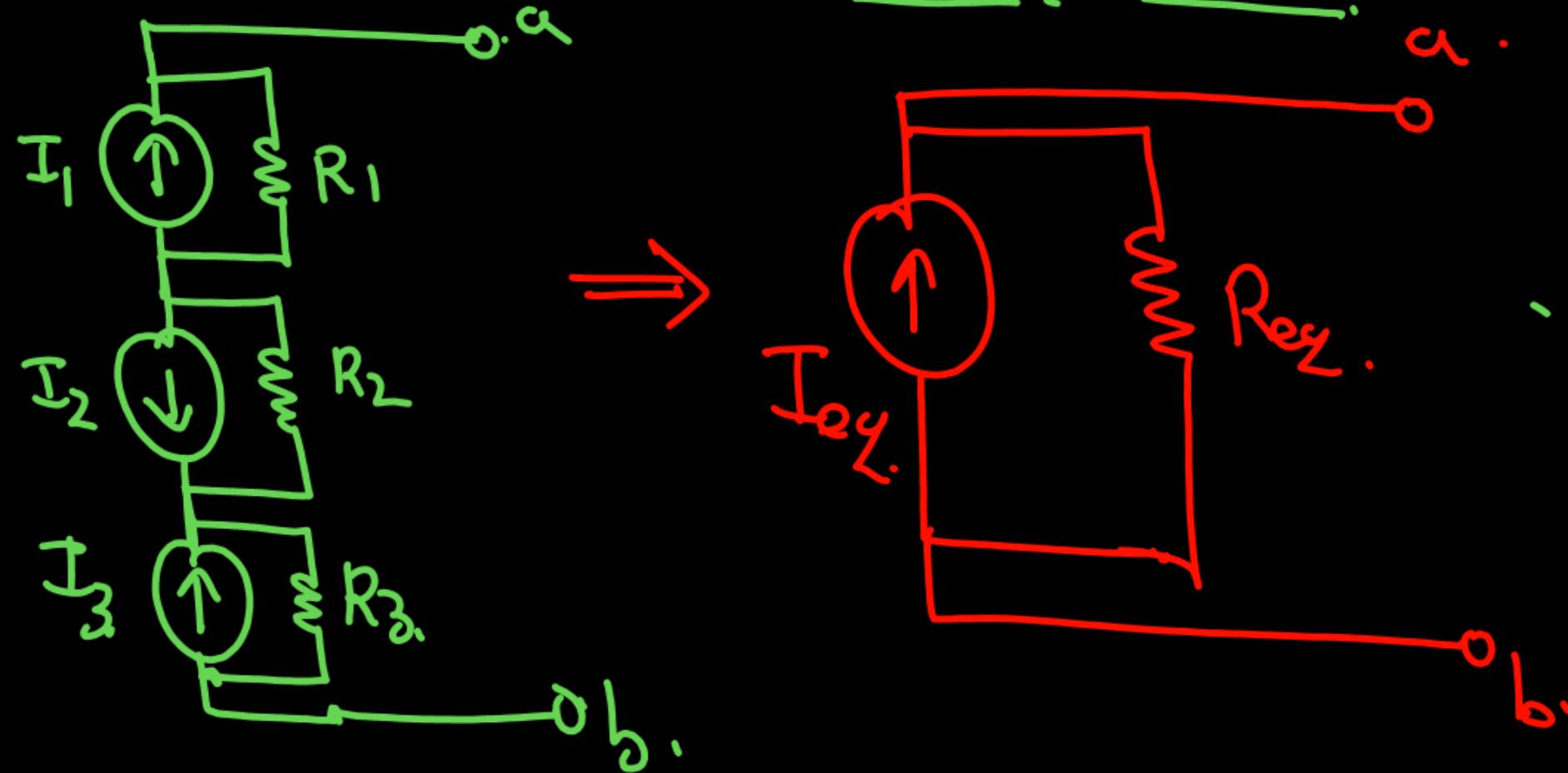


- Here there is no such conditions what we have. Discussed in Ideal current case. Any kind of Practical current source can be series connected.
- This operation is given by Dual Millman's theorem.

②

Parallel operation:

(a) Resistors:

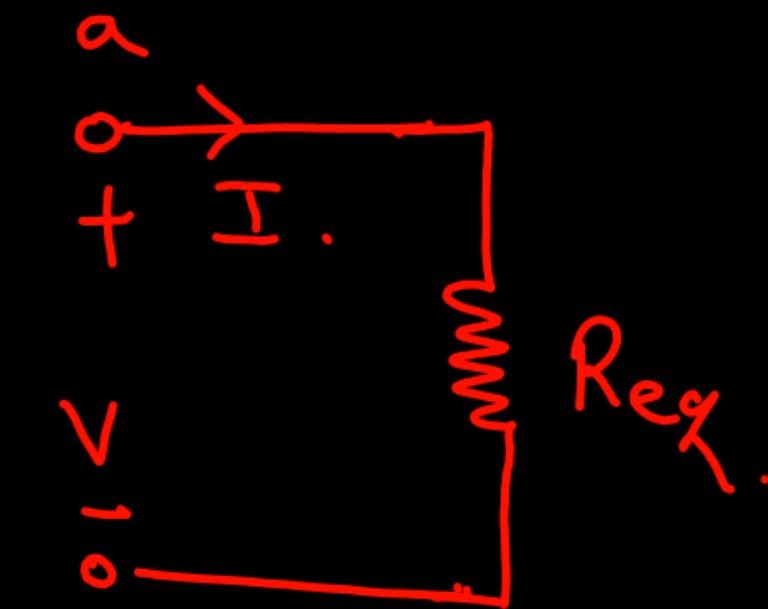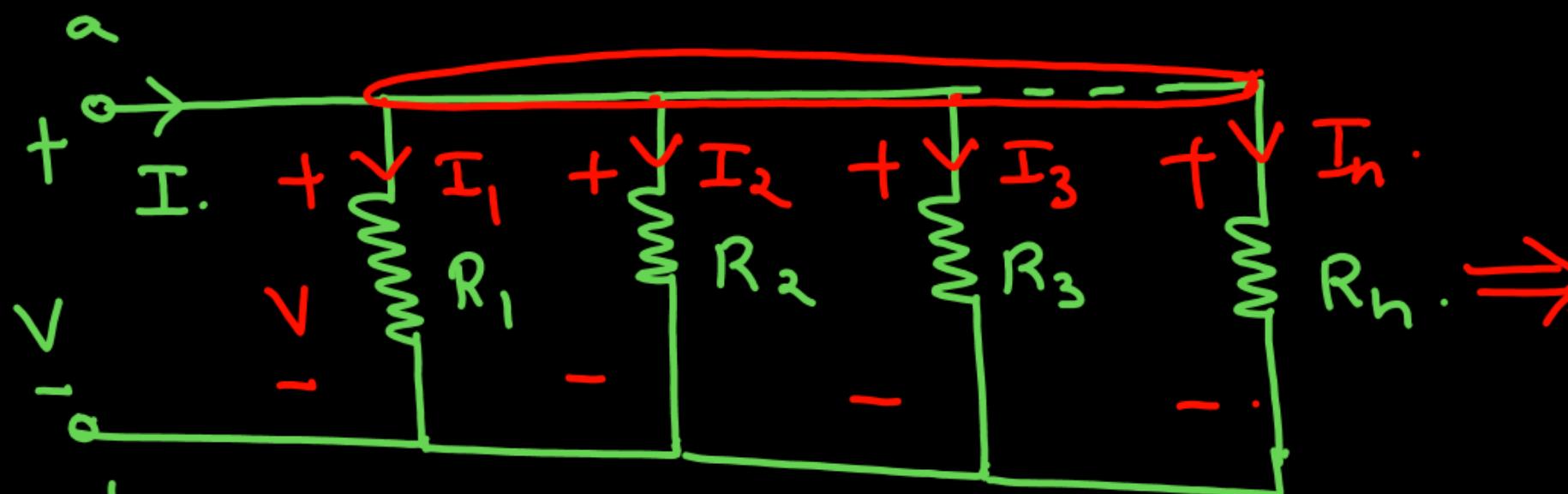

- b.
- Voltage across each element will remain same always.
- Current in each resistor may or may not remain same.

$$\text{b. } V = I R_{eq}.$$

$$\left[\frac{I}{R_{eq}} = \frac{I}{V} = G_{eq} \right]$$

- Applying KCL,

$$I = I_1 + I_2 + I_3 + \dots + I_n.$$

$$I = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} + \dots + \frac{V}{R_n}.$$

$$\left[\frac{I}{V} = \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n} \right] \rightarrow \text{in terms of Resistors. } (\Omega).$$



$$\left[G_{eq} = G_1 + G_2 + G_3 + \dots + G_n \right] \rightarrow \text{in terms of conductance. } (\text{S})$$

- Here a concept comes into picture, known as current division rule (CDR). that is used to find current in any Parallelly connected Resistor.

$$I_1 = \frac{V}{R_1} = I \cdot \left(\frac{Req}{R_1} \right) = I \cdot \left(\frac{G_1}{G_{eq}} \right).$$

$$I_2 = \frac{V}{R_2} = I \cdot \left(\frac{Req}{R_2} \right) = I \cdot \left(\frac{G_2}{G_{eq}} \right)$$

$$I_h = \frac{V}{R_h} = I \cdot \left(\frac{Req}{R_h} \right) = I \cdot \left(\frac{G_h}{G_{eq}} \right)$$

Hence, current in any resistor (x) connected in Parallel,

$$\left[I_x = I \times \frac{Req}{R_x} = I \times \frac{G_{x \cdot}}{G_{eq}} \right]$$

$\therefore x = 1, 2, 3, \dots, h.$

• If all resistors are same value.

$$[R_1 = R_2 = R_3 = \dots = R_h = R]$$

General formula
of CDR.

$$\frac{1}{R_{eq}} = \frac{1}{R} + \frac{1}{R} + \dots + \frac{1}{R} = \left(\frac{h}{R}\right)$$

$$[R_{eq} = \frac{R}{h}]$$

$$\cdot [G_{eq} = G_1 + G_1 + \dots + G_1 = h \cdot G_1].$$

• CDR →

$$[I_x = I \times \frac{R_{eq}}{R_x} = I \times \frac{R/h}{R} = \frac{I}{h}]$$

$$[I_{x'} = I \times \frac{G_{eq}}{G_x} = I \times \frac{G_1}{h G_1} = \frac{I}{h}]$$

(b) Parallel operation of Voltage Sources!



[Sunday → 3 to 5 PM]
↳ [3rd August]

• [4 to 7] → August → (class nahi)

✓ 7 → onwards → {Sat & Sunday} → full
Practice sheet



Thank you
GW
Soldiers!

