

Electrical Engineering



Electronics and Communication Engineering

Instrumentation Engineering



Lecture No. 04

Basics of Network Theory



By- Pankaj Shukla sir



Recap of Previous Lecture

1. KVL & KCL.

2. Powers & energy concept.

3.

4.

5.

6.



Topics to be Covered

1. Question Discussion.

2.

3.

4.

5.

6.

How to Solve Numericals Based on Concepts we have studied.




We will apply in 95% of the cases, the
(Inspection Method) to the Desired value.

In this method:

- (1) We will find the current in each branch of the circuit by using KCL.
- (2) Now we will apply KVL in the loops of circuit & Develop the equation in terms of variables.
- (3) Now solve the Equations Developed & find the Desired response.


Note:

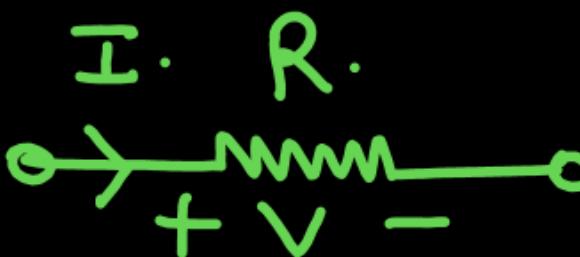- (1) while applying "Inspection Method" it is recommended that maintain number of variables in the circuit less than two are equal to two.
- (2) Follow the sign conventions as given below.




Current Direction known.

(Case-I)

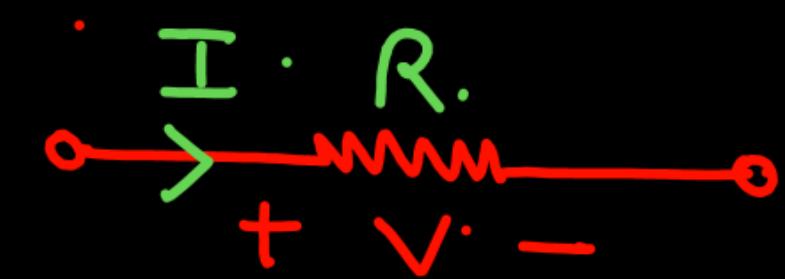

Voltage Polarity is known.
(Case-II)

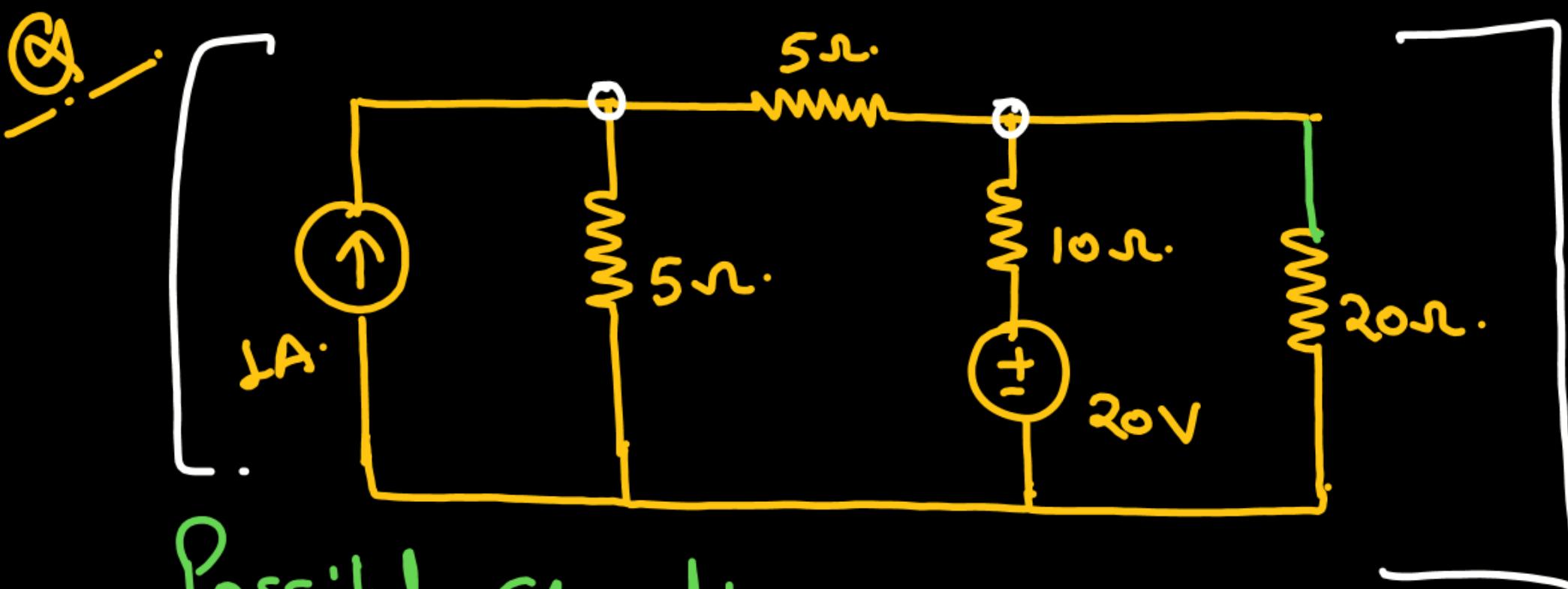

Possible Questions:

- (1) Find the current in 20Ω .
- (2) Find the Total Power Delivered in the ckt.
- (3) Find the total Power Dissipated in the circuit.
- (4) Find the total consumed Power in the circuit.



• (Inspection Method - 01).


$$| \quad KVL - 02.$$

$$| \quad 20 + 10 \times (I - I_1 - I) = 20I.$$

$$| \quad 20 + 10 - 10I_1 - 10I = 20I.$$

$$10I_1 + 30I = 30.$$

$$[I_1 + 3I = 3] - \textcircled{2}$$

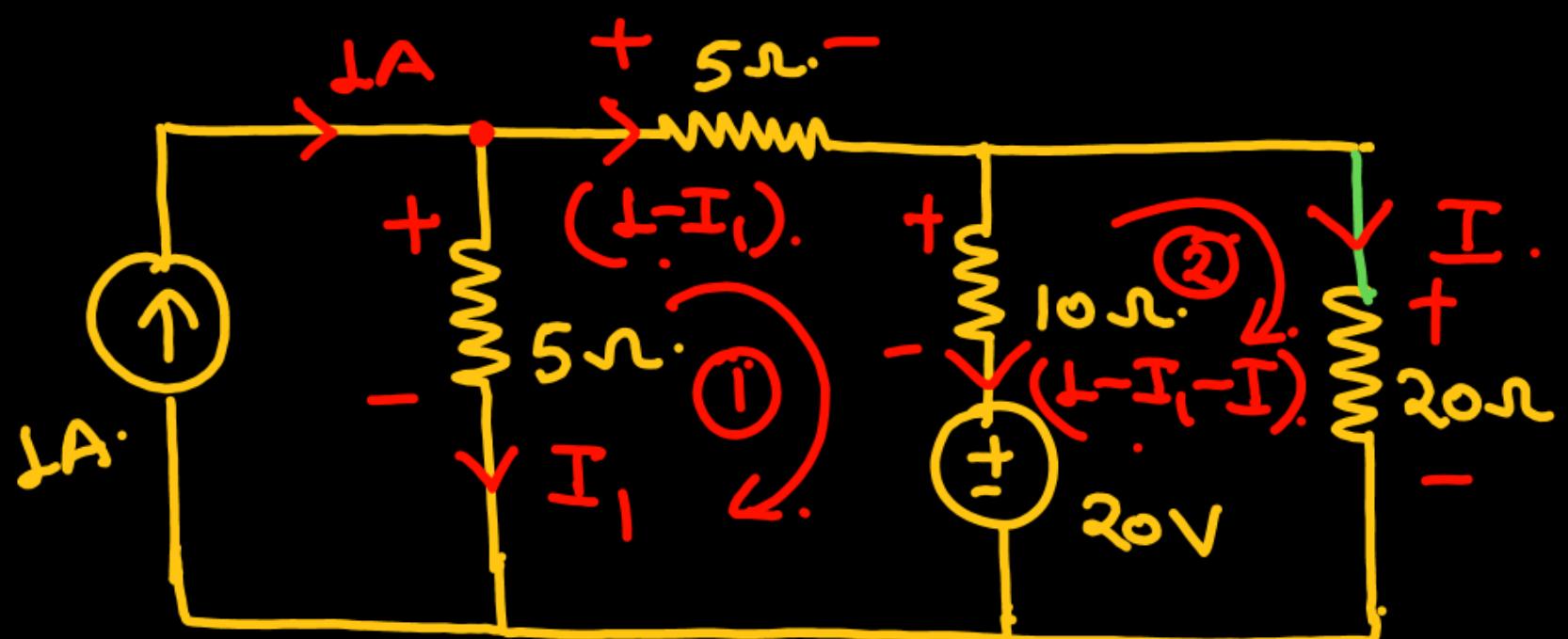

• $KVL \rightarrow \textcircled{1}$

$$5I_1 = 5 \times (I - I_1) + 10 \times (I - I_1 - I) + 20$$

$$5I_1 = 5 - 5I_1 + 10 - 10I_1 - 10I + 20.$$

$$20I_1 + 10I = 35.$$


$$[4I_1 + 2I = 7] - \textcircled{1}$$

$$4I_1 + 2I = 7$$
$$4 \times [I_1 + 3I = 3]$$

$$I(2 - 3 \times 4) = 7 - 3 \times 4.$$

$$\left[I = \frac{-5}{-10} = +\frac{1}{2} = 0.5 A \right]$$
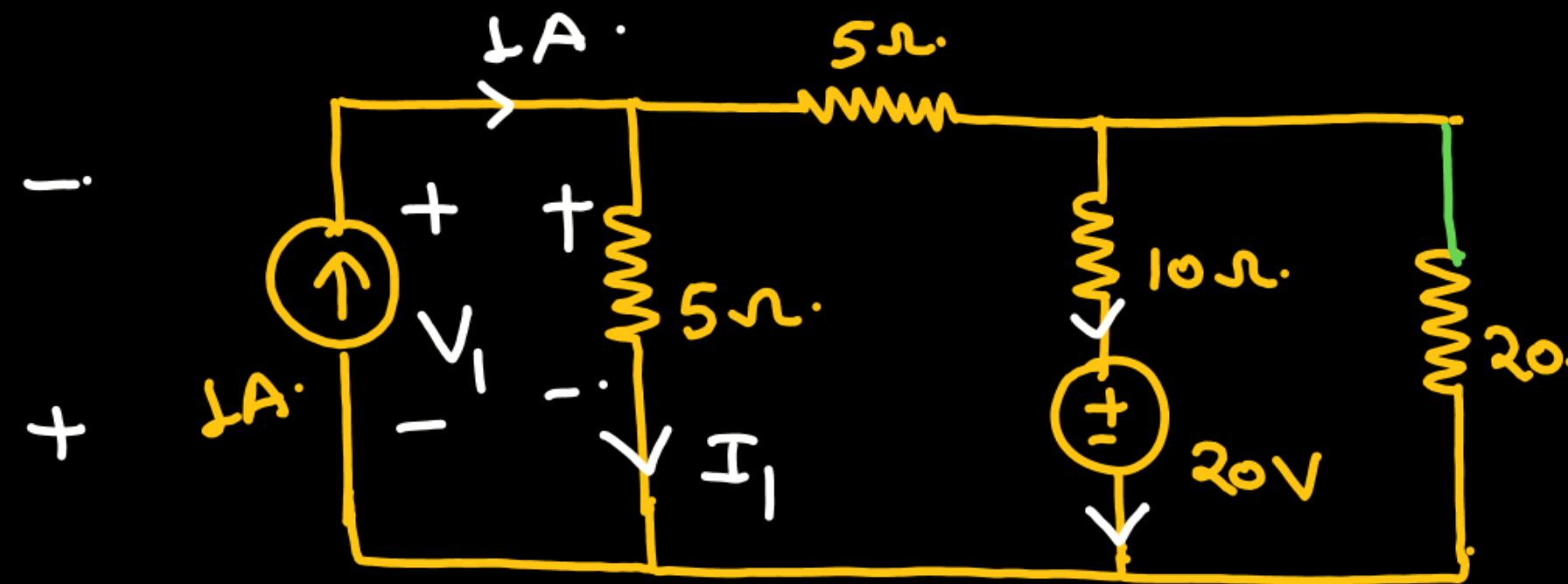
$$\therefore \left[I_1 = 3 - 3I = 3 - 3 \times \frac{1}{2} = 1.5 \right]$$



$P_T(\text{defined})$
 $= 20 + 7.5$
 $= 27.5 \text{ watt}$
 $= P_T(\text{absorb}) = P_T(\text{consumed})$

• $P_T(\text{defined}) = ?$


$$P_{20V} = 20 \times (1 - I_1 - I) = 20 \times (1 - 1.5 - 0.5) = -20 \text{ W(A).}$$

$$P_{1A} = V_1 \times 1 = (5 \times I_1) \times 1 = 5 \times 1.5 \times 1 = 7.5 \text{ W(D).}$$

$$-7.5 \text{ W(A).}$$
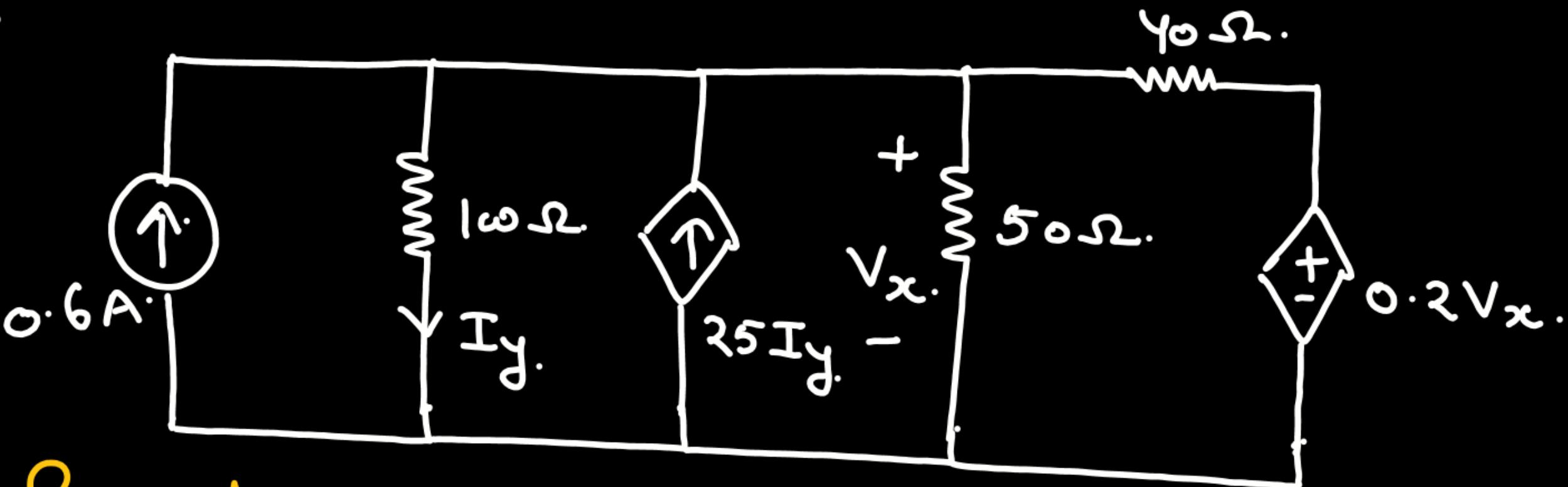
$$\cdot [P_T(\text{dissipated}) = P_T(\text{absorb}) - O = 27.5 \text{ watt}]$$






Possible Questions:

① Find V_x & I_y .

③ Find the P_T (delivered), P_T (absorb), P_T (dissipated)

• Inspection method.

—OL.

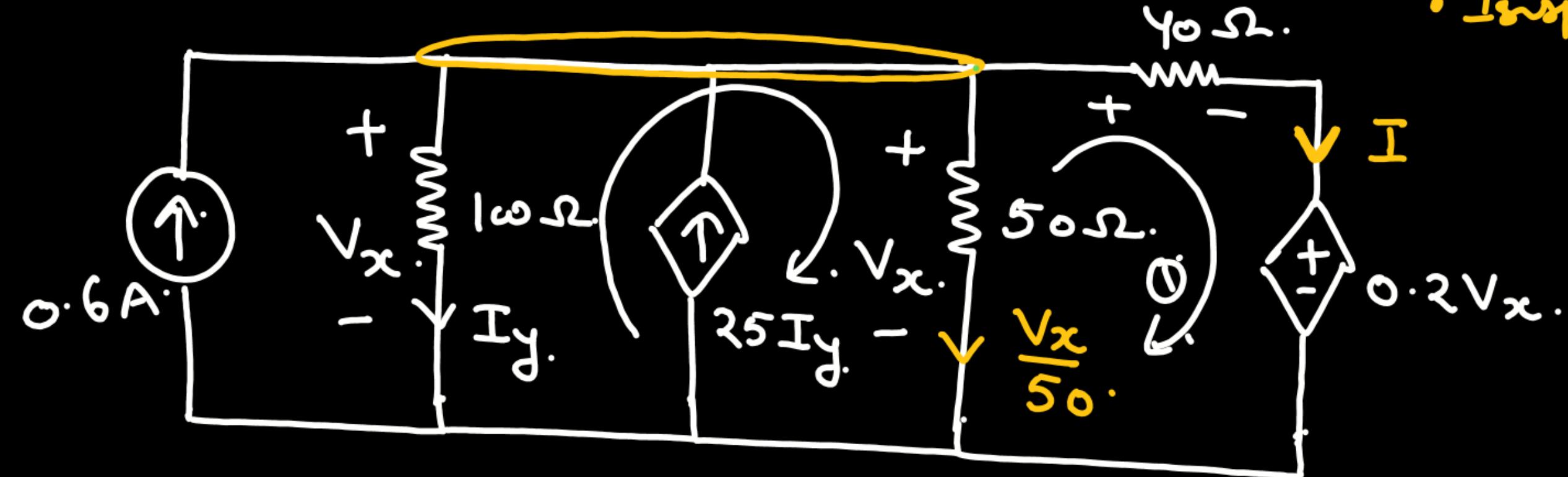

$$I + \frac{V_x}{50} + I_y = 0.6 + 25I_y$$

$$\bullet \text{ KVL} \rightarrow (0.1) I = (0.6 + 25I_y - I_y - \frac{V_x}{50}) \neq (0.6 + 24I_y - 0.02V_x)$$

$$V_x = 0.2V_x + 40 \times (0.6 + 24I_y - 0.02V_x)$$

$$V_x (1 - 0.2 + 40 \times 0.02) - 40 \times 24I_y = 40 \times 0.6$$

$$1.6V_x - 960I_y = 24 \quad \text{--- (1)} \quad | \quad V_x = 100 \times I_y$$

• KVL - 02.

$$V_x = I_y \times 100$$

$$[V_x - 100I_y = 0] \quad \text{--- (2)}$$


$$\bullet 1.6 \times [V_x - 100I_y = 0]$$

$$\underline{- 1.6V_x - 960I_y = 24}$$

$$\underline{\underline{I_y(-100 \times 1.6 + 960) = 0 - 24}}$$

$$\left[I_y = -\frac{24}{800} = -0.03 A \right]$$

$$| \quad V_x = 100 \times (-0.03) \\ | \quad = (-3 \text{ volt})$$

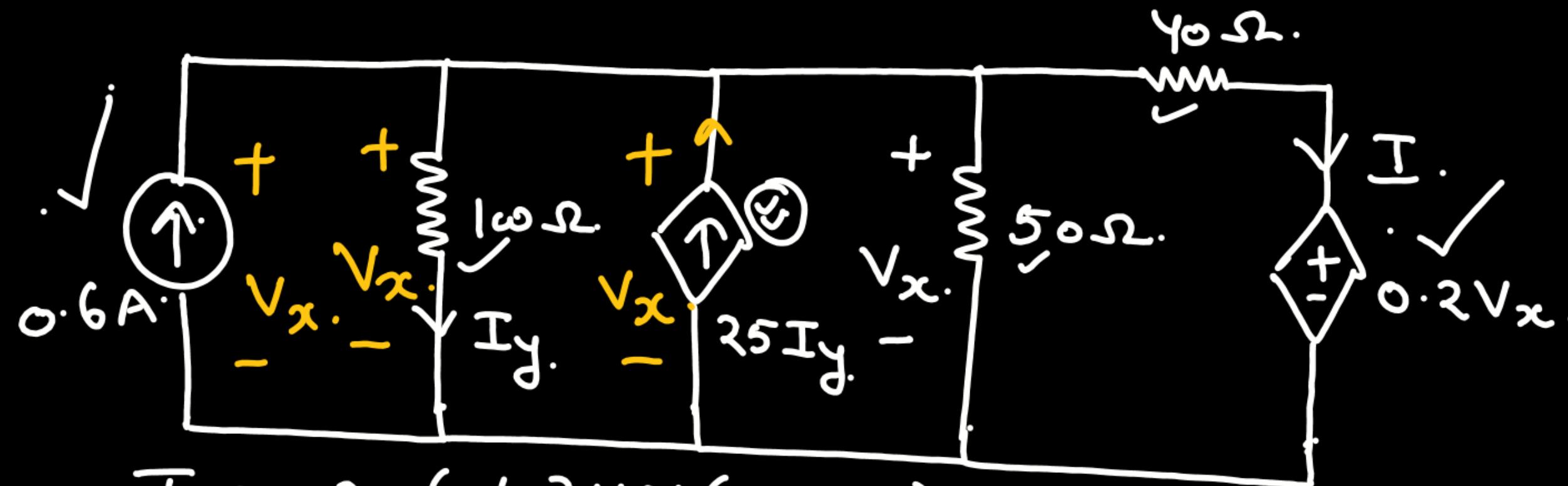

$$I = 0.6 + 24 \times (-0.03) - 0.02 \times (-3).$$

$$[I = 0.6 - 0.72 + 0.06 = -0.06 \text{ A}].$$

$$P_{0.2Vx} = (0.2 \times Vx) \times I = 0.2 \times (-3) \times (-0.06) = 0.036 \text{ watt}$$

$$(A).$$

$$P_{0.6A} = 0.6 \times Vx = 0.6 \times (-3) = -1.8 \text{ W (D)}.$$

an. -0.036 watt

$$+1.8 \text{ W (A)}. \quad (D).$$

$$P_{25I_y} = (25I_y) \times V_x = 25 \times (-3) \times (-0.03)$$

$$= 2.25 \text{ W(D)} \quad \text{or} \quad 2.25 \text{ W(A)}$$



$$P_T(\text{defined}) = P_T(\text{absorb}) = P_T(\text{consumed}).$$


$$= (2.25 \text{ W})$$

$$P_T(\text{dissipated}) = 2.25 - P_{0.6} - P_{0.2Vx}$$

$$= (2.25 - 1.8 - 0.036)$$

$$= (0.414 \text{ W})$$


Q.

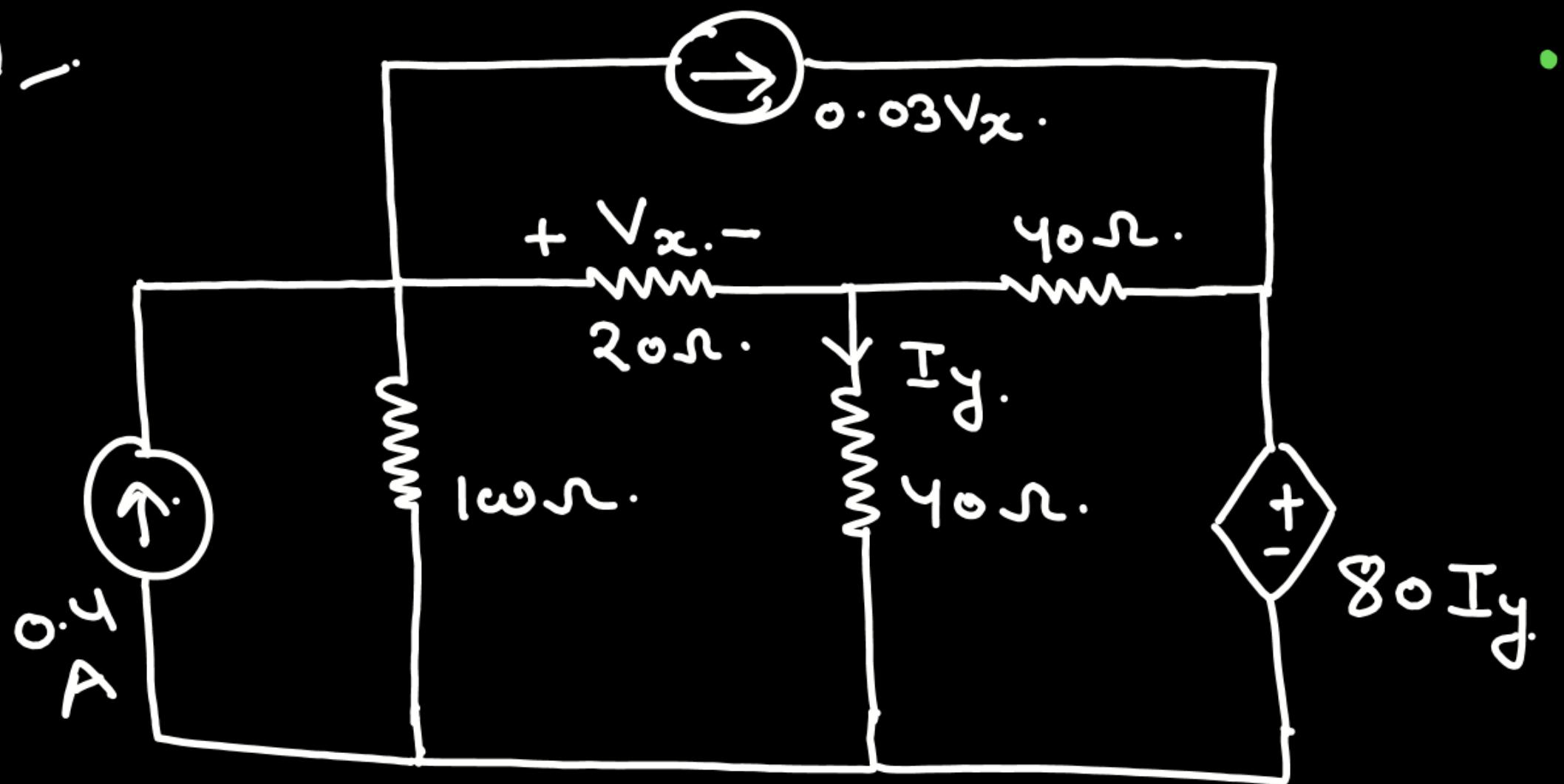

• Inspection Method.

Possible Question:

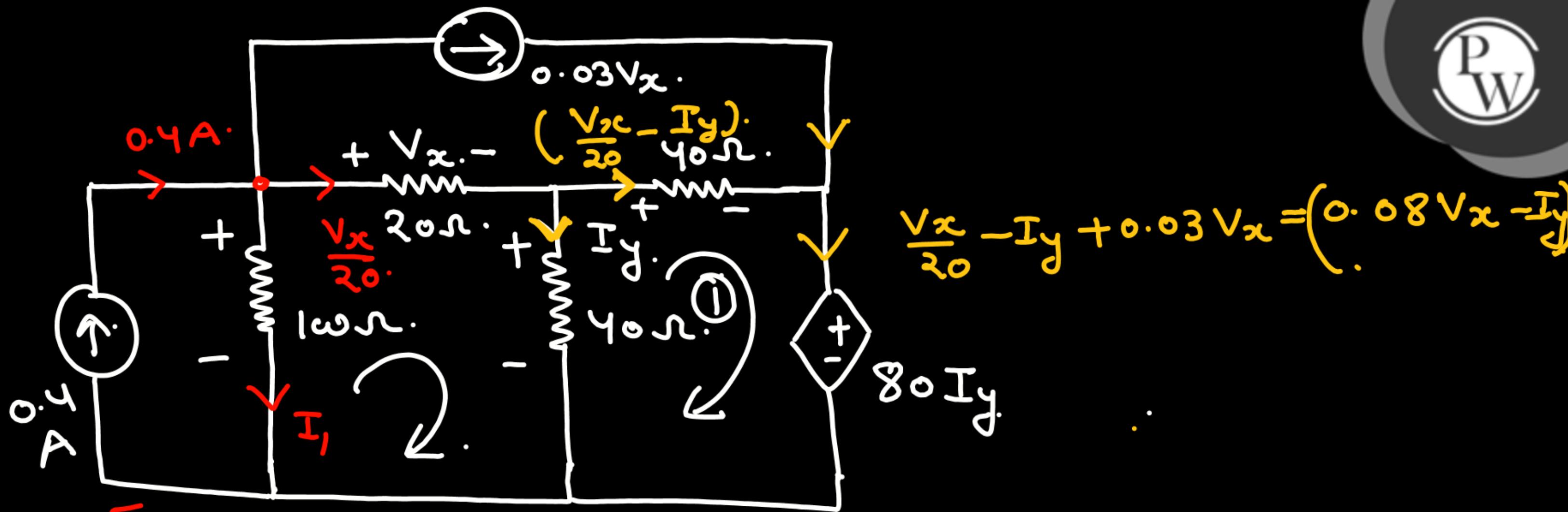- (1) Find V_x & I_y .
- (2) Find P_T (defined).



$$\frac{V_x}{20} - I_y + 0.03V_x = (0.08V_x - I_y)$$

$$[I_1 = 0.4 - \frac{V_x}{20} - 0.03V_x = 0.4 - 0.08V_x]$$

KVL-OL.

$$\left. \begin{aligned} 40I_y &= 40 \times (0.05V_x - I_y) + 80I_y \\ I_y(40 - 80 + 40) &- 2V_x = 0 \end{aligned} \right\} \quad \begin{aligned} 0 - 2V_x &= 0 \\ [V_x &= 0V] \end{aligned}$$

• KVL - 02 →

$$1\omega \times I_1 = V_x + 40 I_y.$$

$$1\omega \times (0.4 - 0.08 V_x) = V_x + 40 I_y$$


$$40 I_y = 1\omega \times 0.4.$$

$$\left[I_y = \frac{1\omega \times 0.4}{40} = 1A \right]$$

•



8

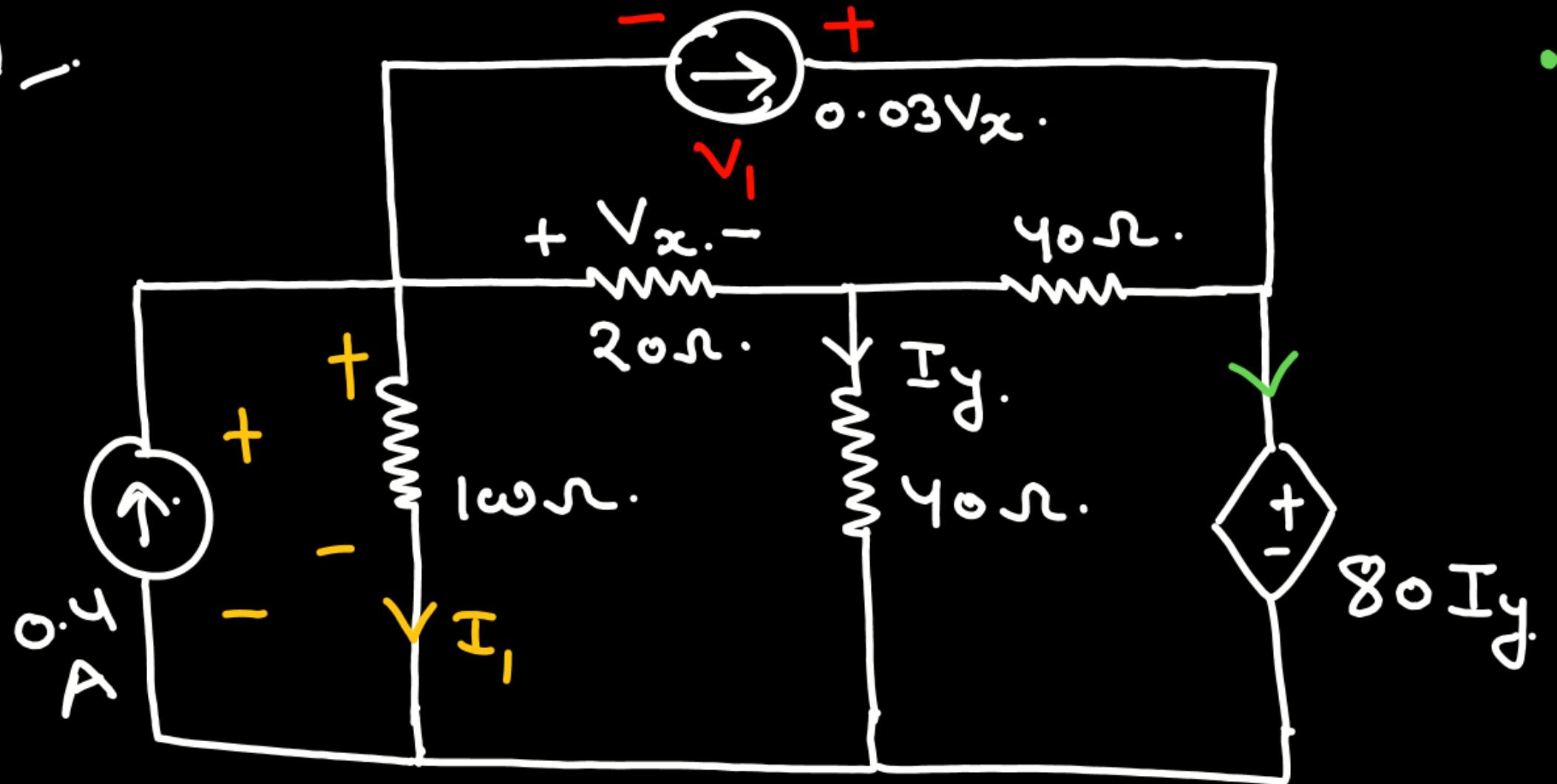

- Inspection Method.



$$P_{80I_y} = 80 \times I_y \times (0.98V_x - I_y) = -80W \text{ (A) on } +80W \text{ (D)}.$$


$$\begin{aligned}
 P_{0.4A} &= 0.4 \times (\omega \times I_1) = 0.4 \times \omega \times (0.4 - 0.08V_x) \\
 &= 16W(1) \text{ or } -16W(A).
 \end{aligned}$$


$$P_{0.03V_x} = (0.03V_x) \times V_I = 0 \text{ W}$$


$$\begin{aligned} P_T(\text{delivered}) &= P_T(\text{absorb}) = P_T(\text{consumed}) \\ &= 80 + 16 = 96 \text{ W} \end{aligned}$$

$$P_T(\text{dissipated}) = 96 - 0 = 96 \text{ Watt}$$

- Inspection Method \rightarrow QL

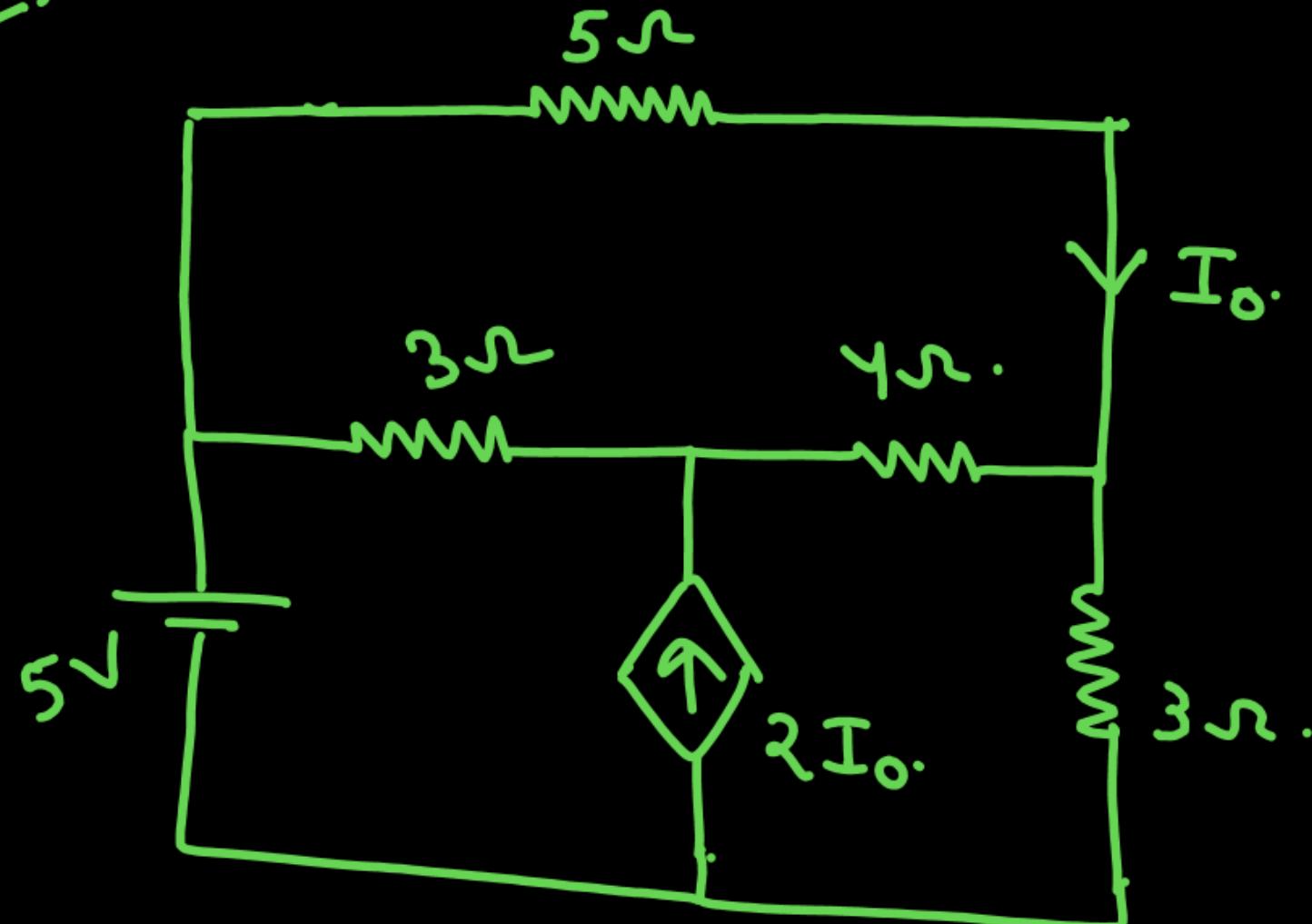

Find the current $I_o = ?$

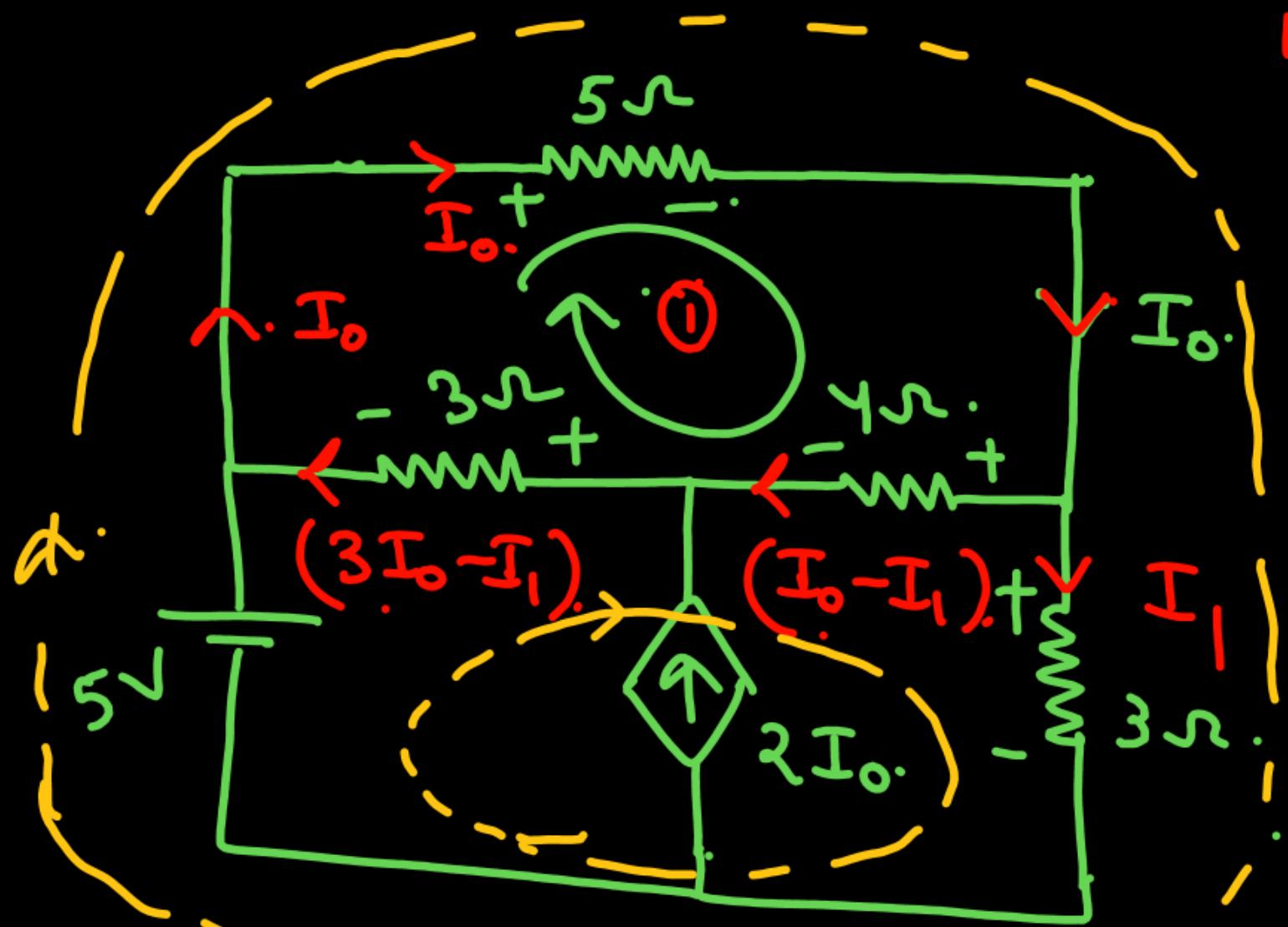

KVL-01.

$$5I_0 + 4 \times (I_0 - I_1) + 3 \times (3I_0 - I_1) = 0.$$

$$[18I_0 - 7I_1 = 0] \quad \text{--- (1)}$$

KVL-02.

$$5 + 3 \times (3I_0 - I_1) + 4 \times (I_0 - I_1) = -3I_1$$

$$13I_0 - 10I_1 = -5 \quad \text{--- (2)}$$

$$\left\{ \begin{array}{l} I_0 = \frac{35}{89} = 0.3932 \\ I_1 = 0.4 \text{ A} \end{array} \right.$$

$$10 \times [18I_0 - 7I_1 = 0].$$


$$7 \times [13I_0 - 10I_1 = -5].$$

$$\overline{I_0 \times (180 - 13 \times 7) = +5 \times 7}.$$



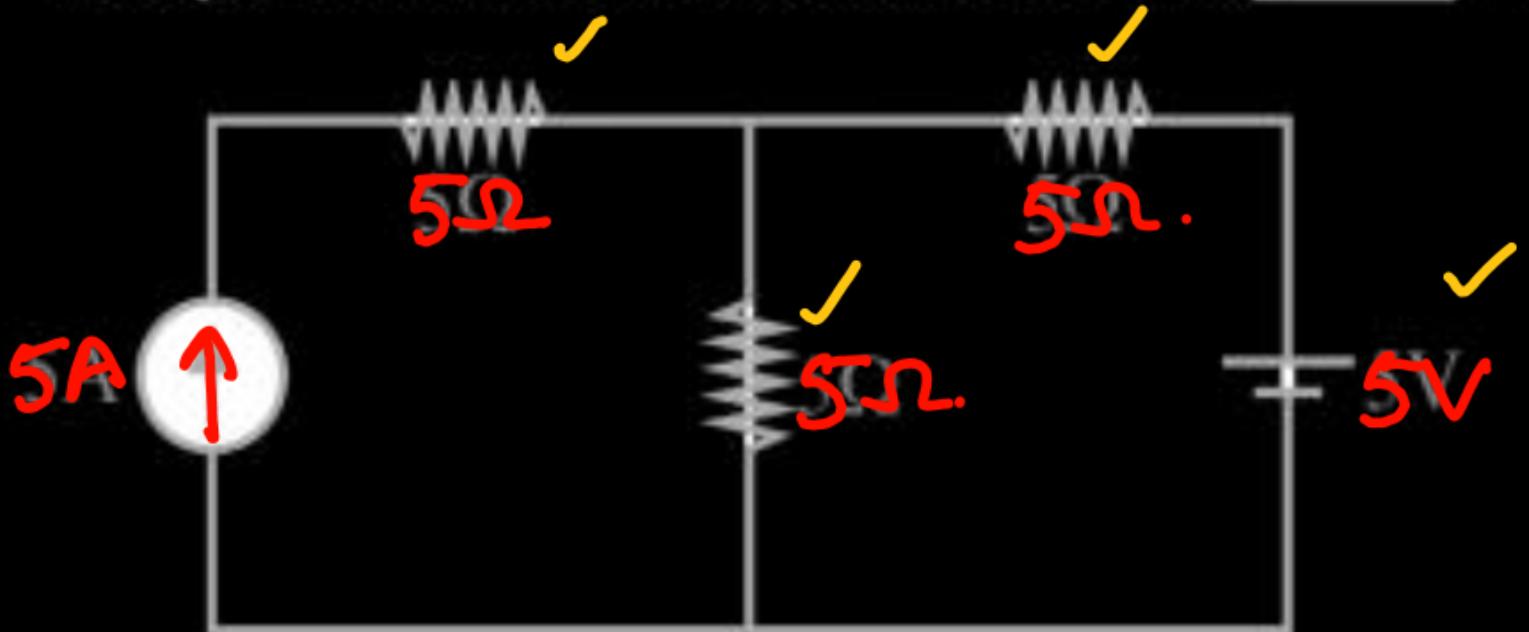Question

Total power consumed in the circuit below is _____ W.




$$P_T(\text{Defined}) = P_T(\text{absorbed}) = P_T(\text{consumed})$$



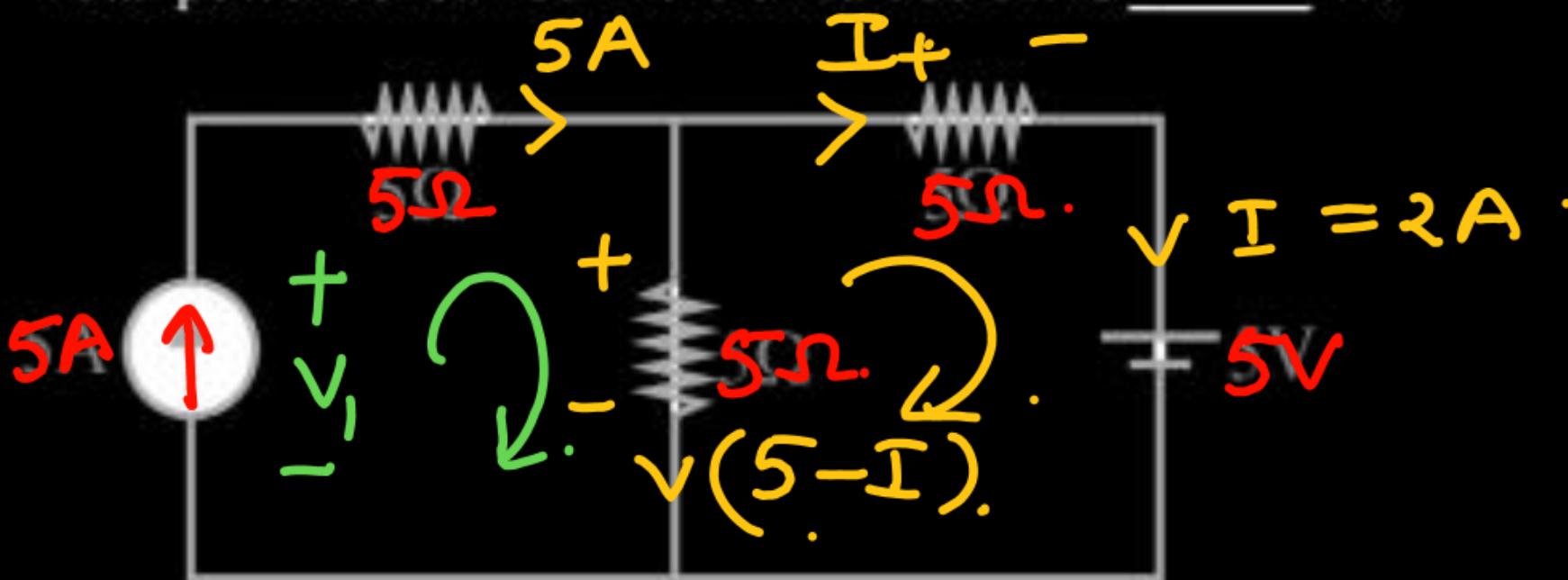Question

Total power consumed in the circuit below is ____ W.



$$5 \times (5 - I) = 5 + 5I$$

$$25 - 5I = 5 + 5I$$

$$10I = 20$$

$$[I = 2A]$$

$$P_{5V} = 5 \times 2 = 10W(A).$$

or.

$$-10W(D)$$

$$P_{5A} = V_1 \times 5 = 40 \times 5 = 200$$

$$= -200W(A), (D)W$$

$$\begin{aligned} V_1 &= 5 \times 5 + 5 \times (3) \\ &= 25 + 15 \\ &= 40 \text{ volt.} \end{aligned}$$

$$P_T(\text{del}) = P_T(\text{absorb}) = P_T(\text{consumed}) = 200 \text{ Watt}$$

$$\bullet \quad [P_T(\text{dissipated}) = 200 - 10 = 190 \text{ W}]$$

@pankaj shukla sirc pw

↓
telegram.
—



Thank you
GW
Soldiers!

