

Electrical Engineering



Electronics and Communication Engineering

Instrumentation Engineering

Network Theory



Lecture No. 03

Basics of Network Theory

By- Pankaj Shukla sir





Recap of Previous Lecture

1. Basic electrical Quantity
2. Energy conservation.
3. Condition for circuit
- 4.
- 5.
- 6.




Topics to be Covered



1. Different types of Sources.
2. KVL & KCL.
3. Question Discussion.
- 4.
- 5.
- 6.


Topic-04 (Different kind of Sources).

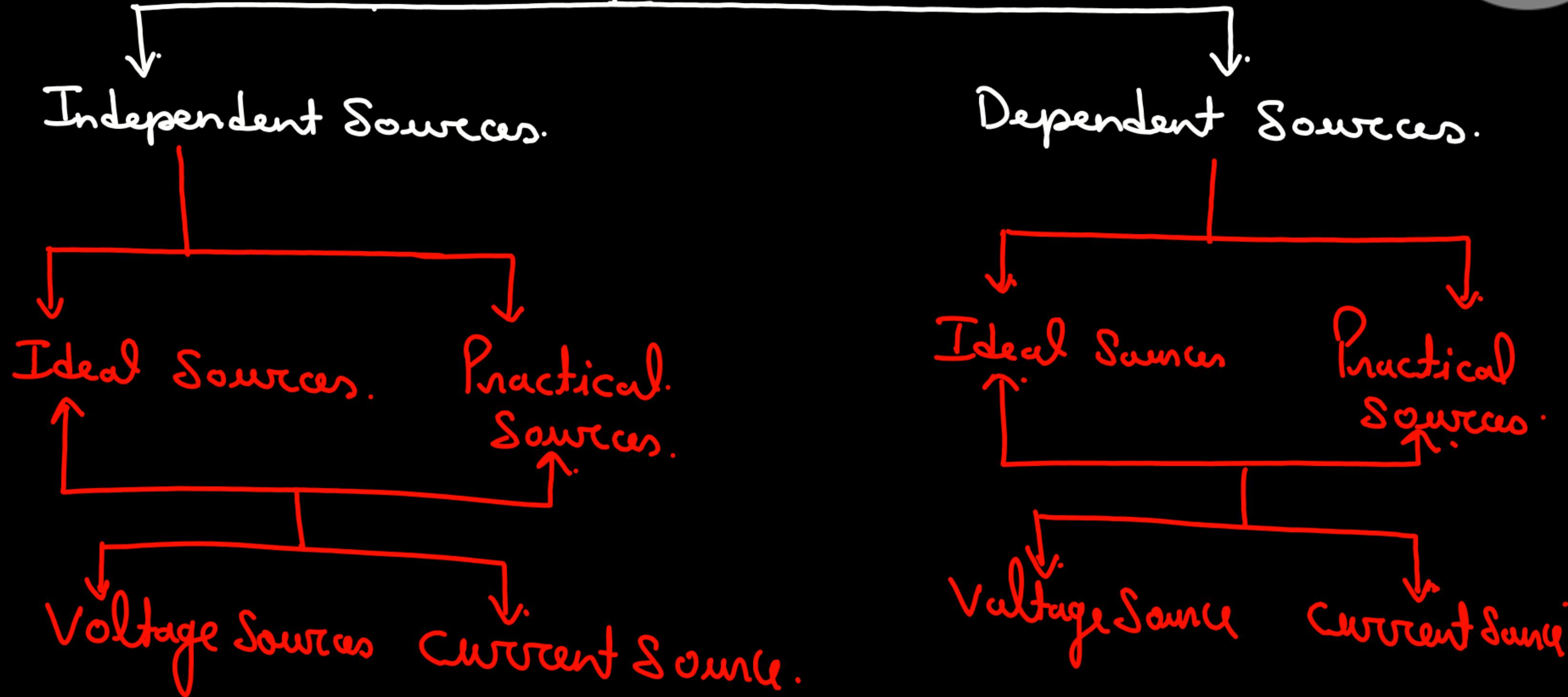


(1) Independent Sources:

(a) Voltage Sources:

(1) Ideal voltage Source:

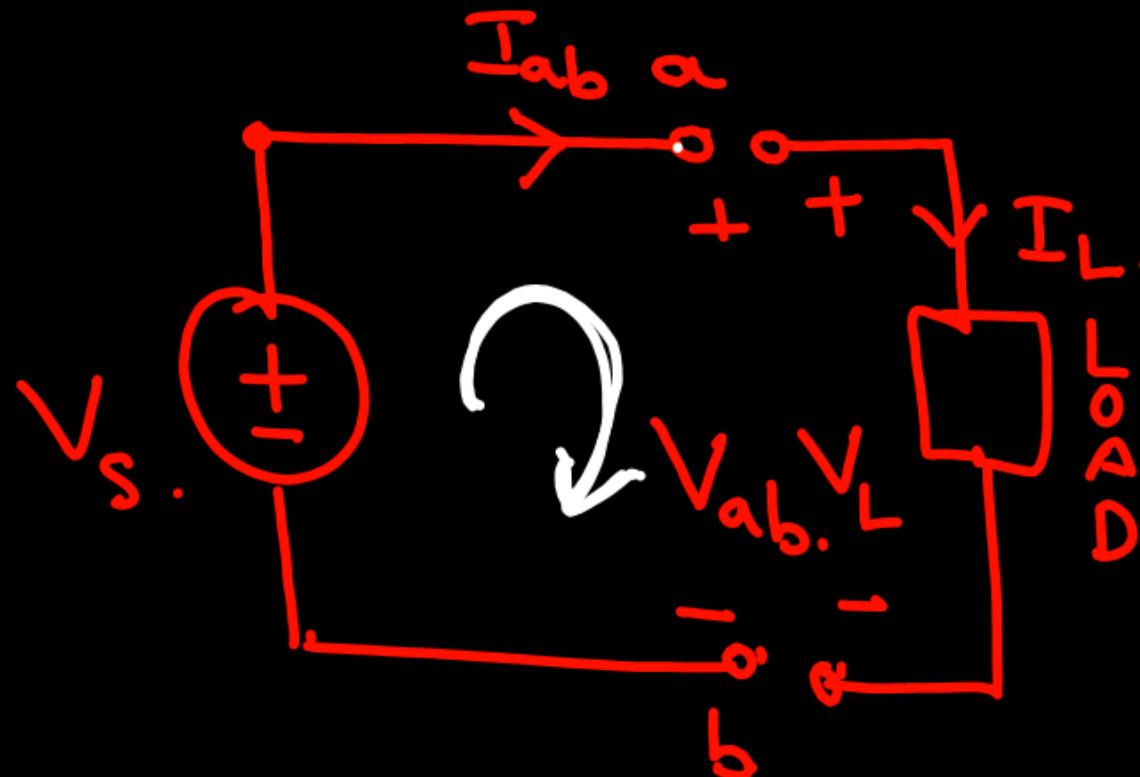

• I_{ab} V_s V_{ab} curve:

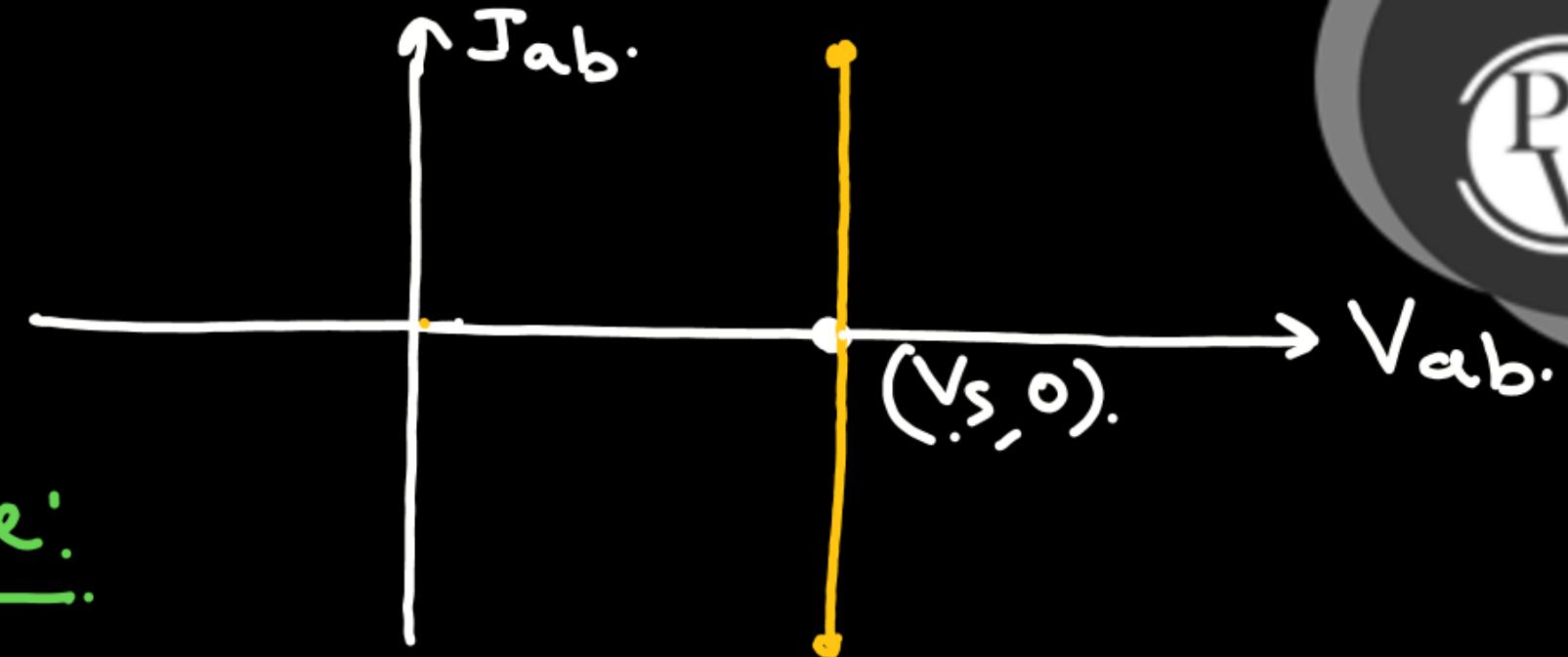


• $V_{ab} = V_s \rightarrow$ Always (fixed).

↳ Independent of Load.

$I_{ab} \Rightarrow \oplus, \ominus, 0 \rightarrow$ can be any value.

↳ It will depend upon the load.

(2) Practical voltage Source:

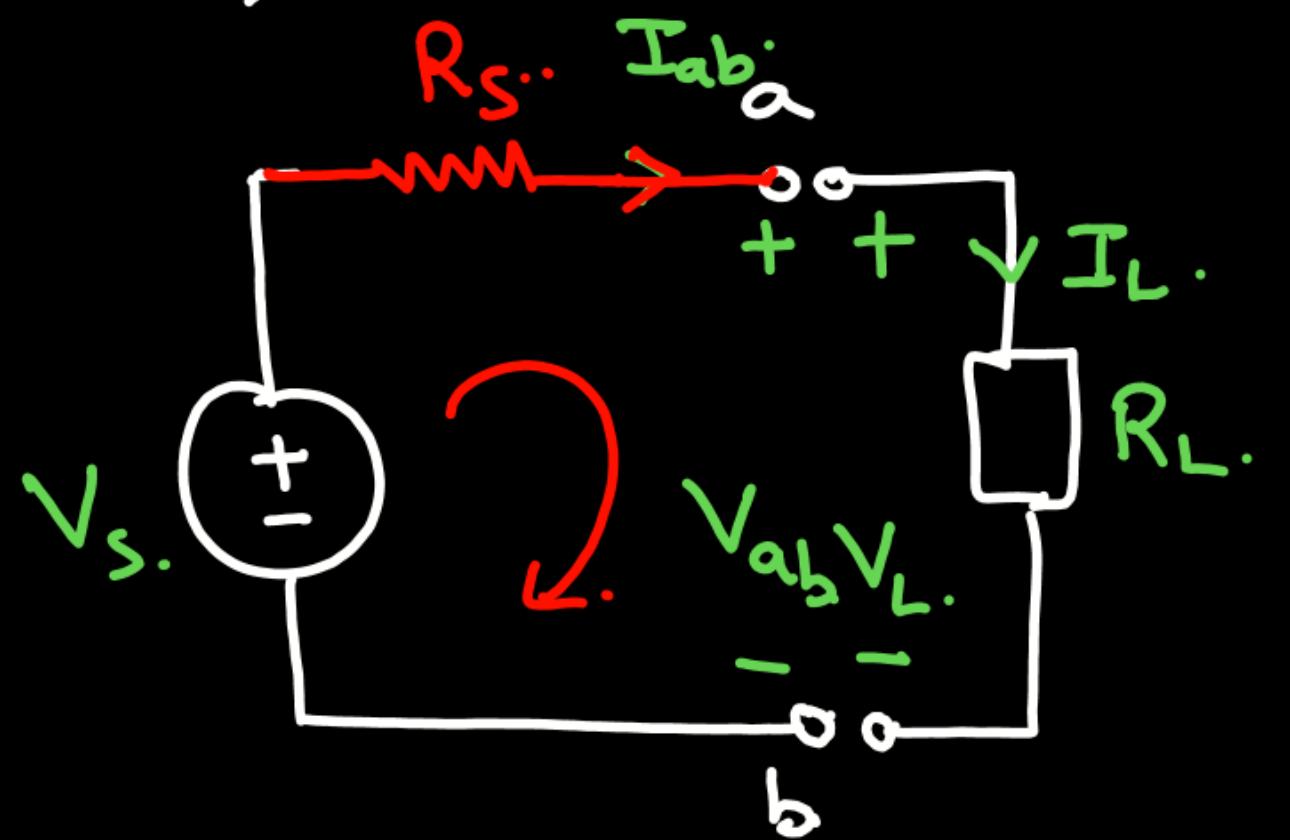

- $V_{ab} \rightarrow I_L$ is not fixed. i.e it can be any value.
- $I_{ab} \rightarrow I_L$ can be any value.
Hence V_{ab} & I_{ab} both are decided by Load.
- $[V_{ab} = V_s - I_{ab} \times R_s]$

$\frac{I_{ab}}{V_s} \cdot V_s = V_{ab}$ curve:


$$V_{ab} = V_s - I_{ab} \cdot R_s.$$

$$I_{ab} = \frac{V_s - V_{ab}}{R_s}.$$

$$I_{ab} = \frac{V_s}{R_s} - V_{ab} \times \left(\frac{1}{R_s} \right)$$

$$I_{ab} = -\left(\frac{1}{R_s}\right) \cdot V_{ab} + \left(\frac{V_s}{R_s}\right)$$


$$\boxed{y = -m \cdot x + C}$$

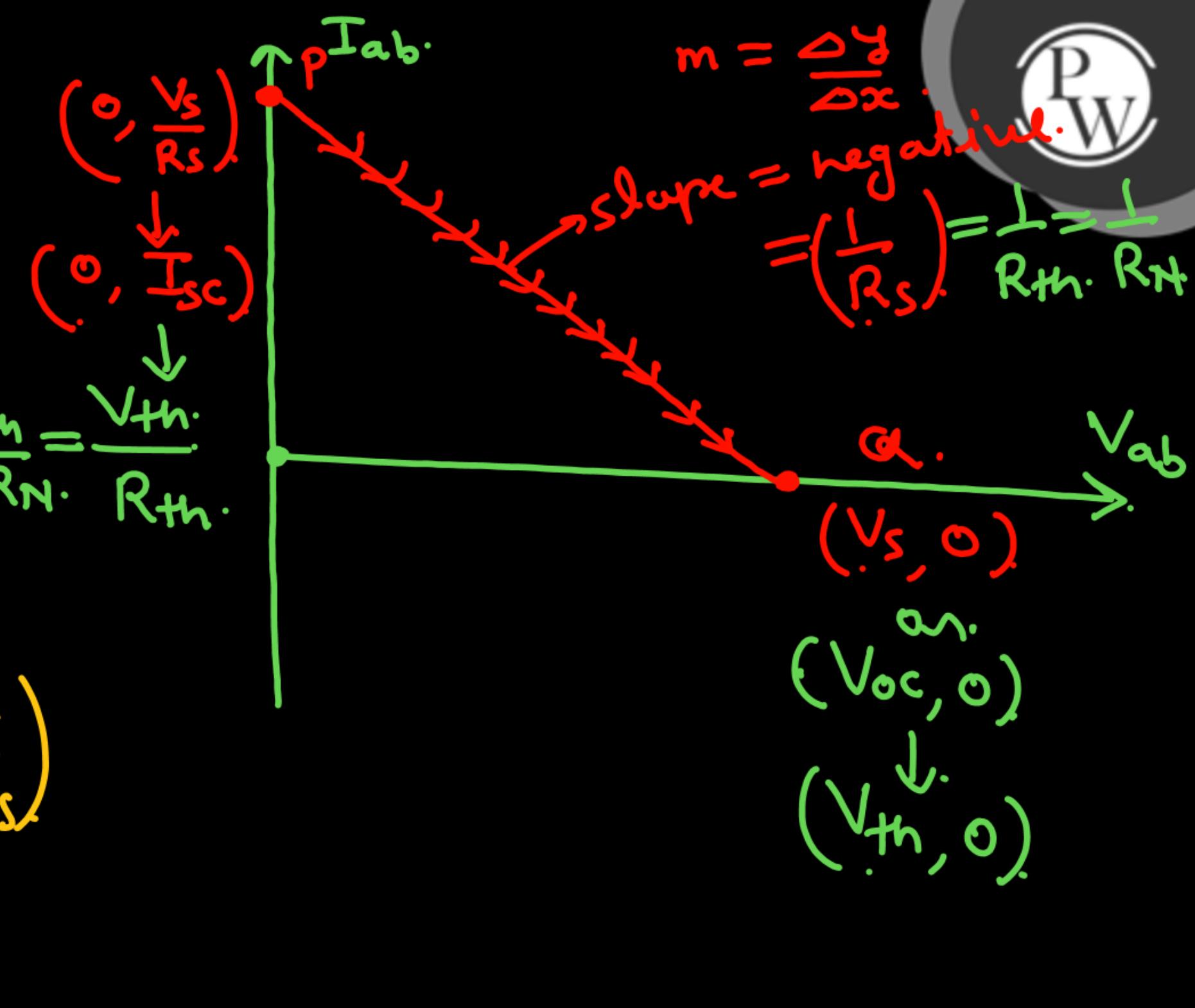

Conclusion:

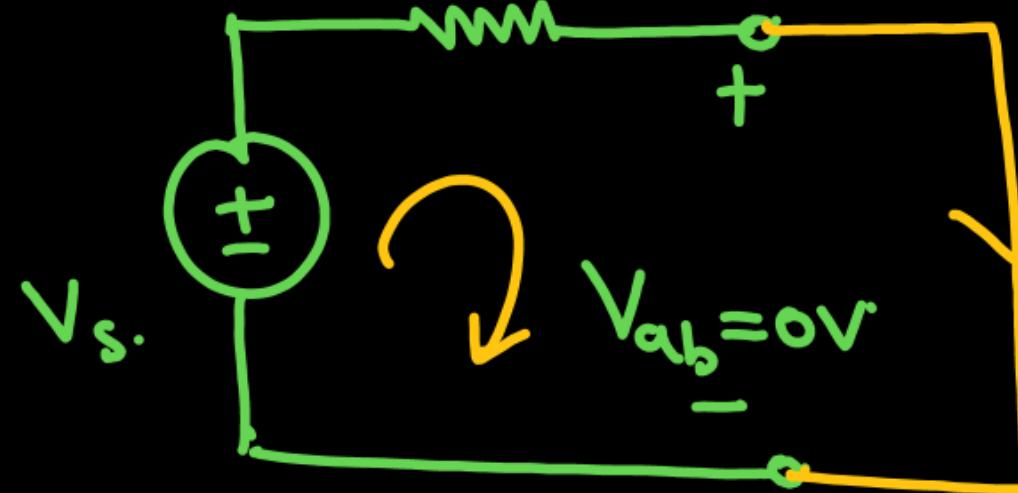(1) at point (P) \rightarrow


$$V_{ab} = 0V \quad \& \quad I_{ab} = \frac{V_s}{R_s} = I_{sc} = I_N = \text{Norton current.}$$



$$I_{ab} = \frac{V_s}{R_s} = \text{short circuit current.}$$

(2)



at point (Q) \rightarrow

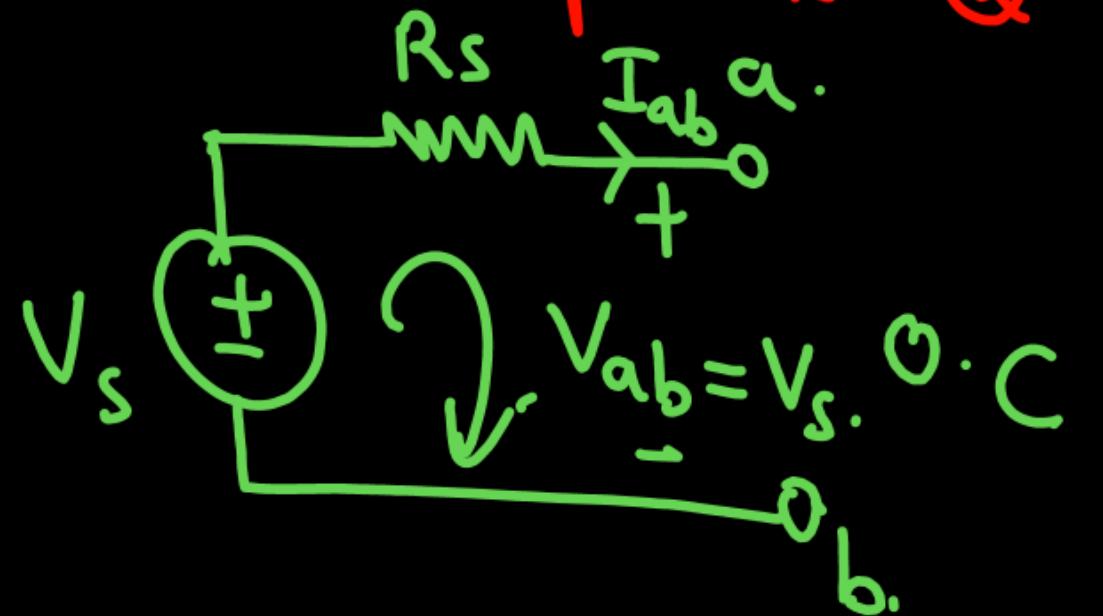

$$V_{ab} = V_s, \quad I_{ab} = 0A \rightarrow \text{open circuit}$$


$$V_{ab} = V_s = V_{oc} = \text{open circuit voltage} \\ = V_{th} = \text{Thevenin Voltage.}$$

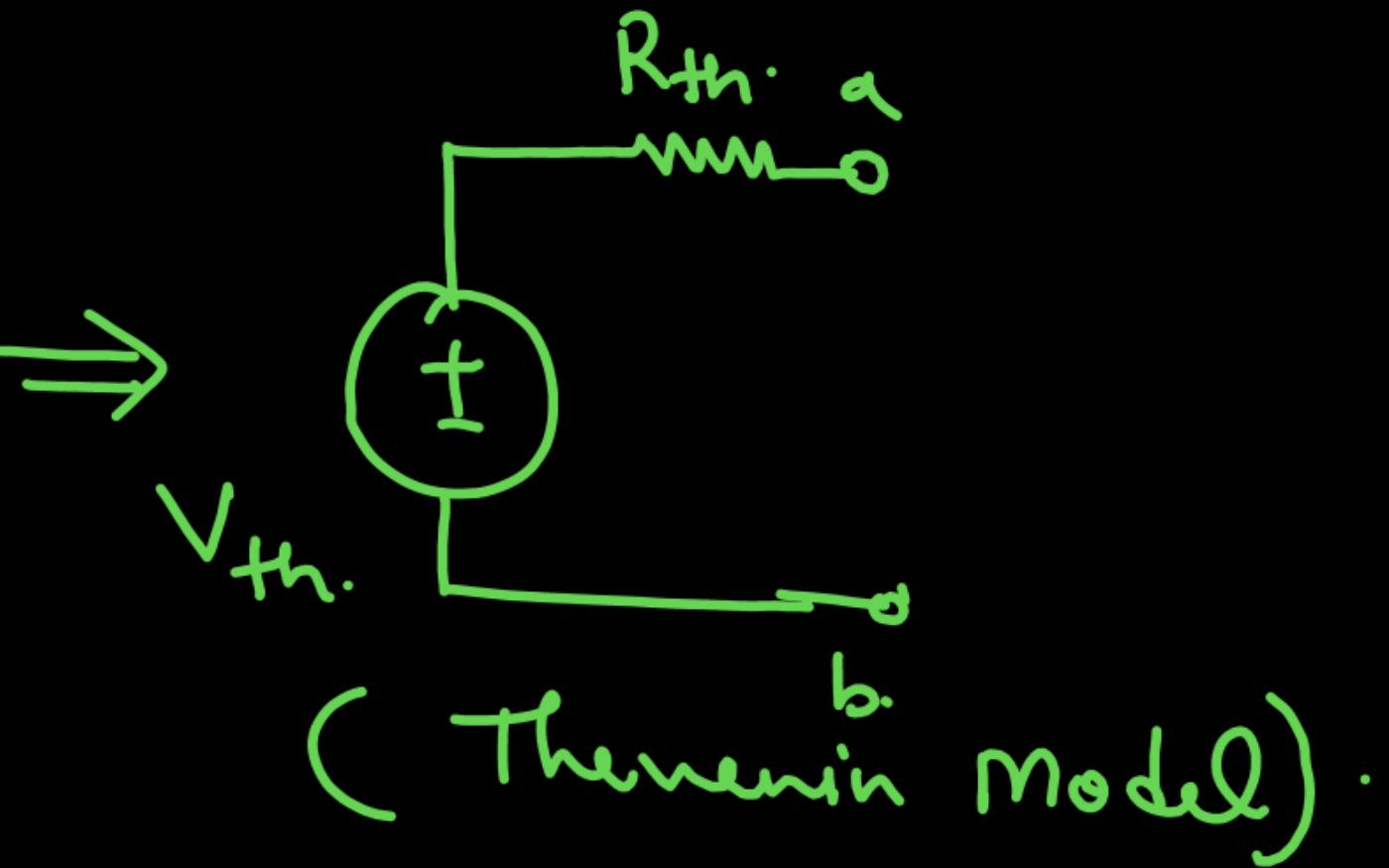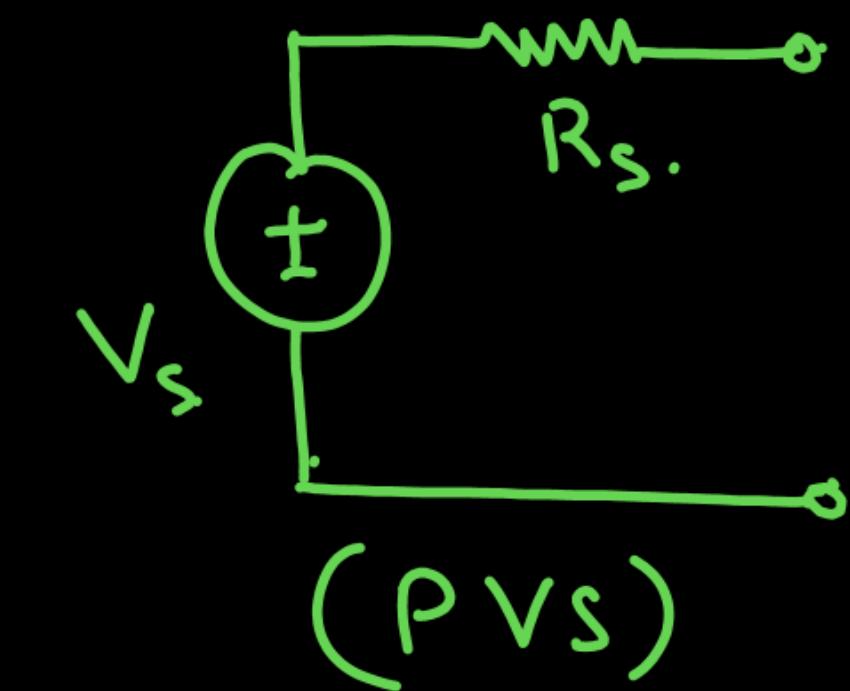Hence, a Practical voltage Source is equivalent of
Thevenin model..



(b) Current Source:

(1) Ideal current Source:

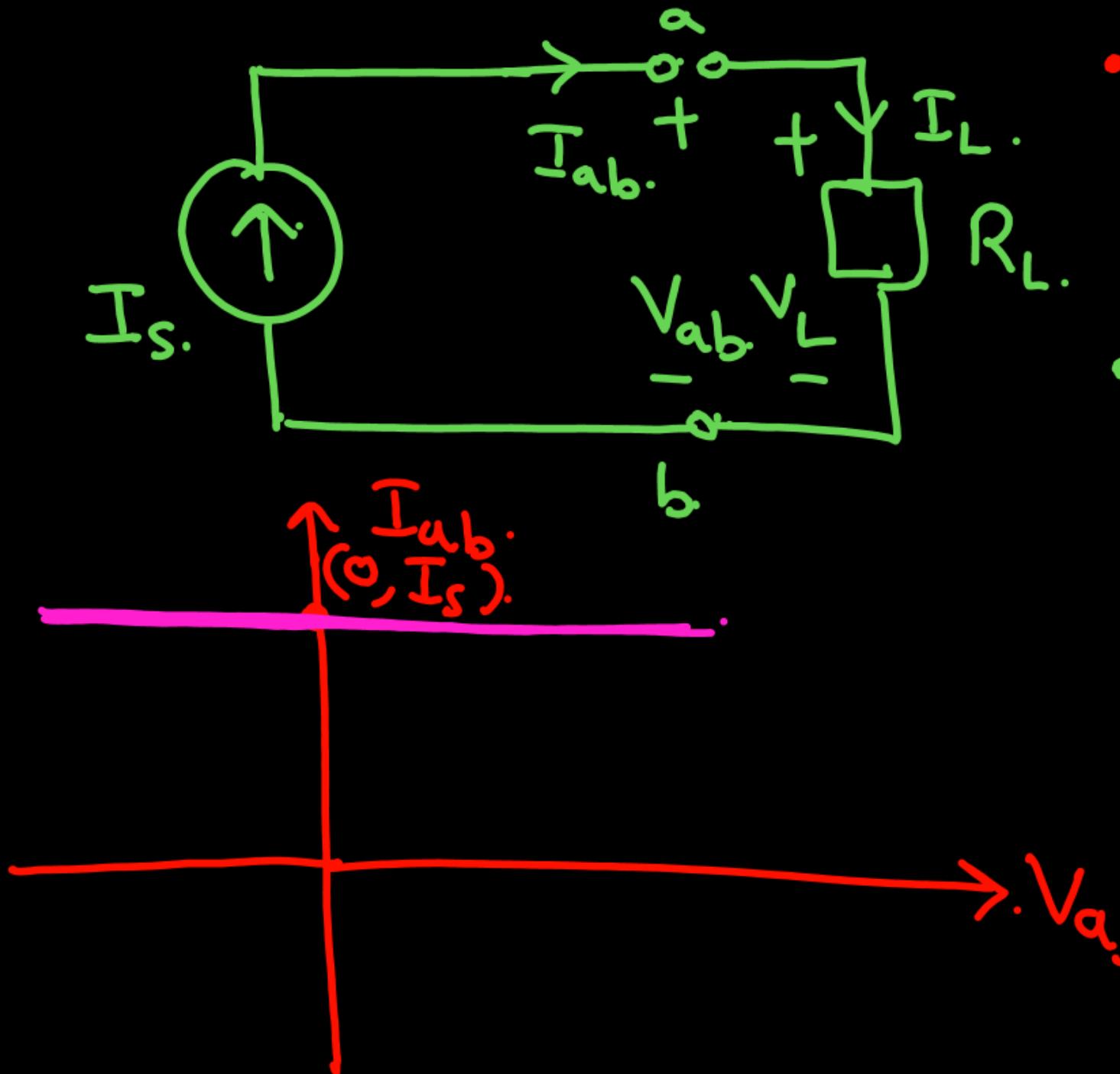

- $I_{ab} = I_S \rightarrow$ Always (fixed).


↳ Independent of Load.

- $V_{ab} \rightarrow$ Can be any value.
($+, 0, -$).

↳ It depends upon the load.

- $I_{ab} \vee V_{ab}$ curve (I-V curve).

② Practical current Source:

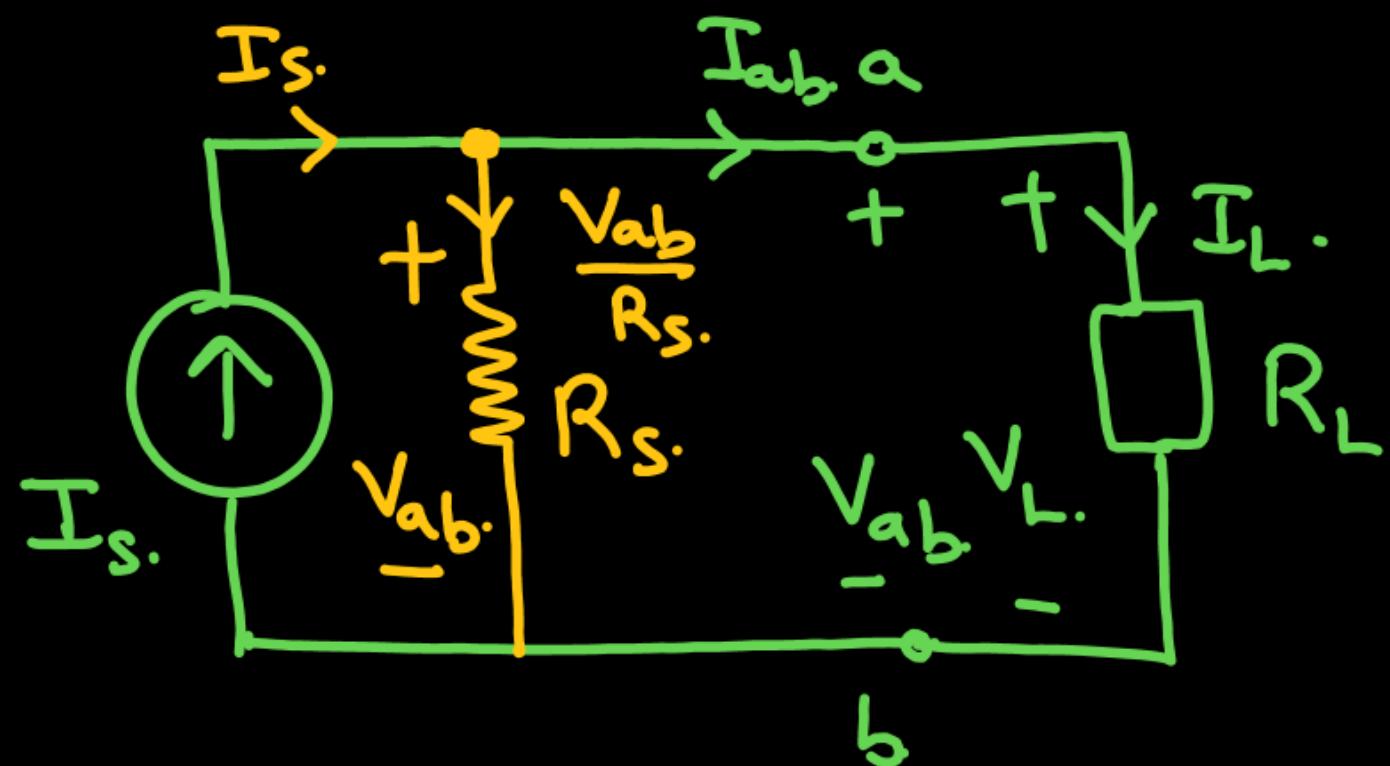

I_{ab} → can be any value.
 V_{ab} → can be any value.
 Depends upon load.


$$I_s. = \frac{V_{ab}}{R_s} + I_{ab.}$$

$$I_{ab} = \frac{V_s - V_{ab}}{R_s} \text{ curve } (I \text{ vs } V)$$



$$I_{ab} = I_s. - \frac{V_{ab}}{R_s}$$

$$\left[I_{ab} = -\frac{1}{R_s} \cdot V_{ab} + I_s \right]$$

$$\left[Y = -m \cdot x + C \right]$$

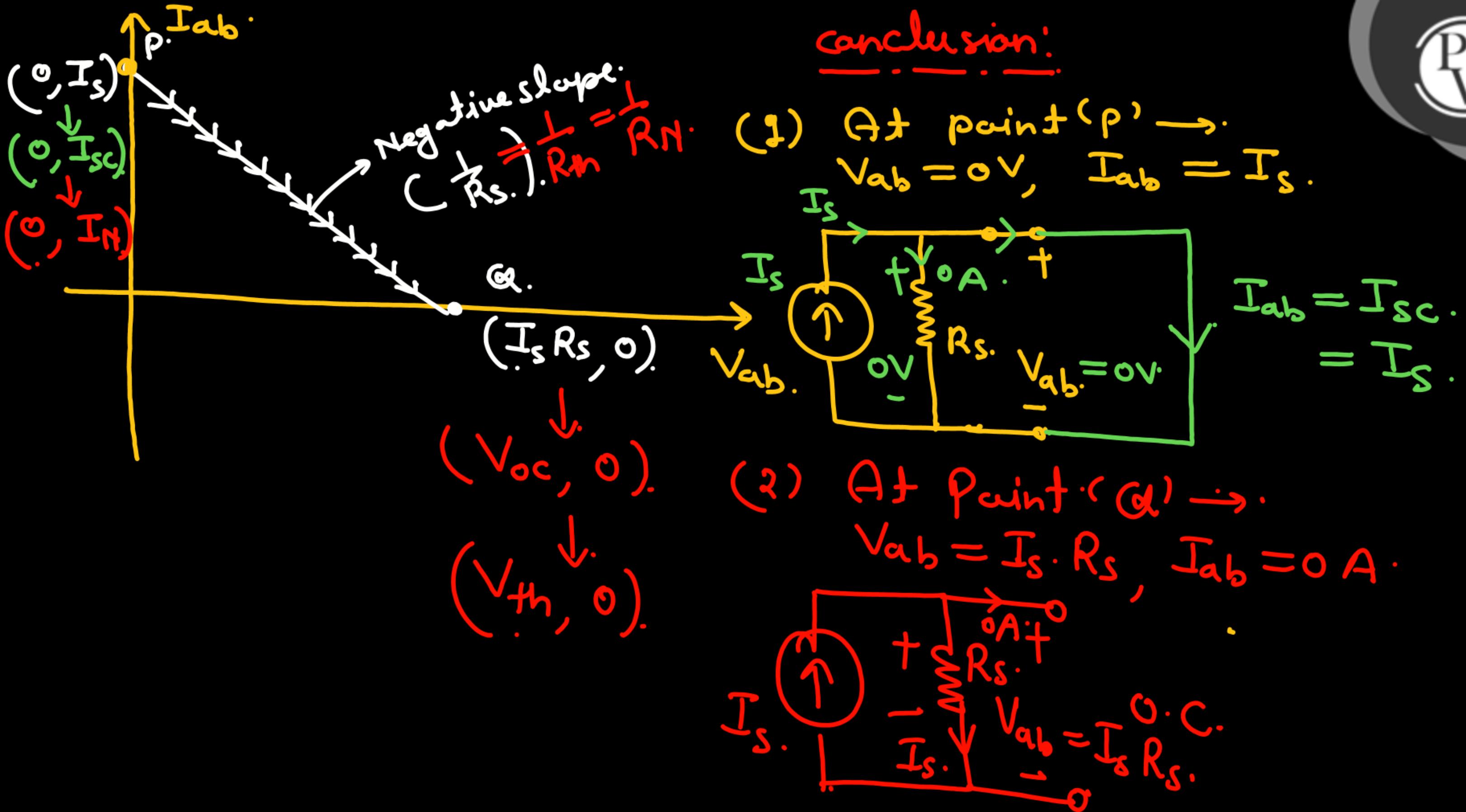

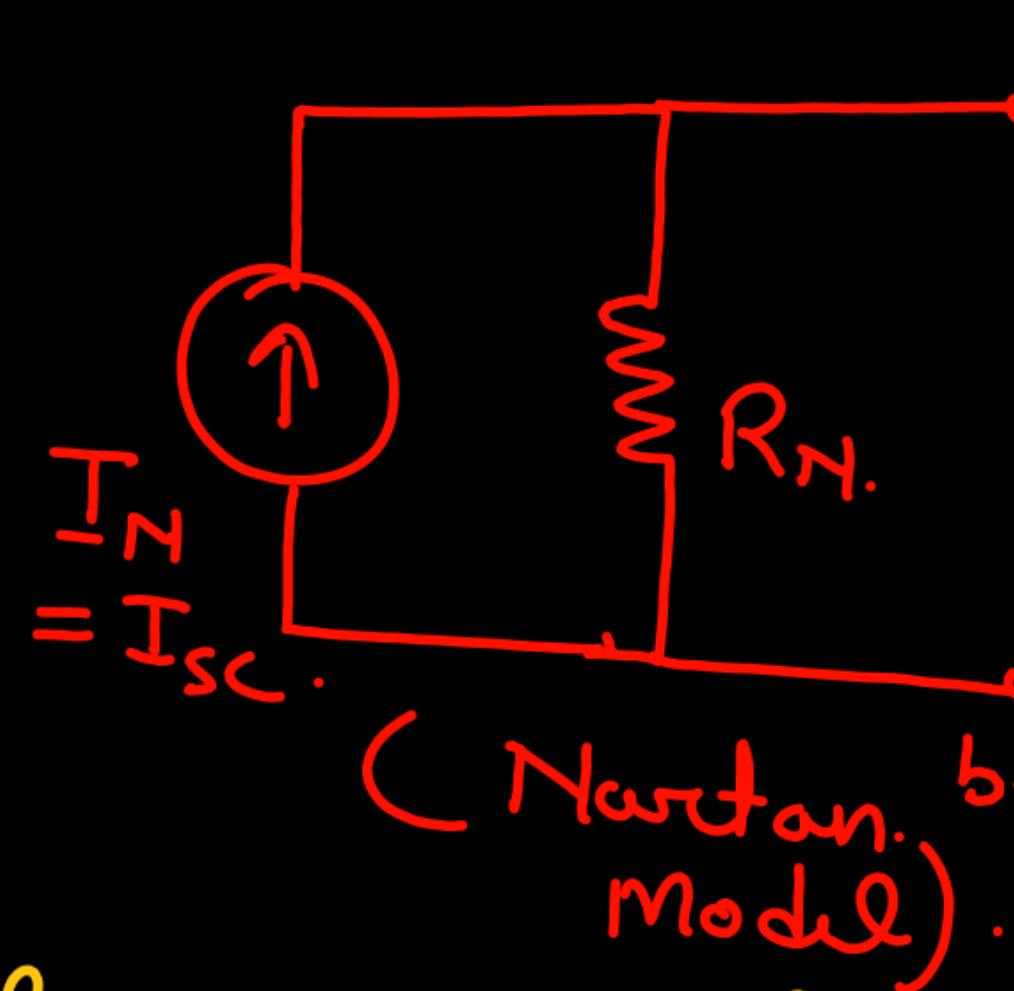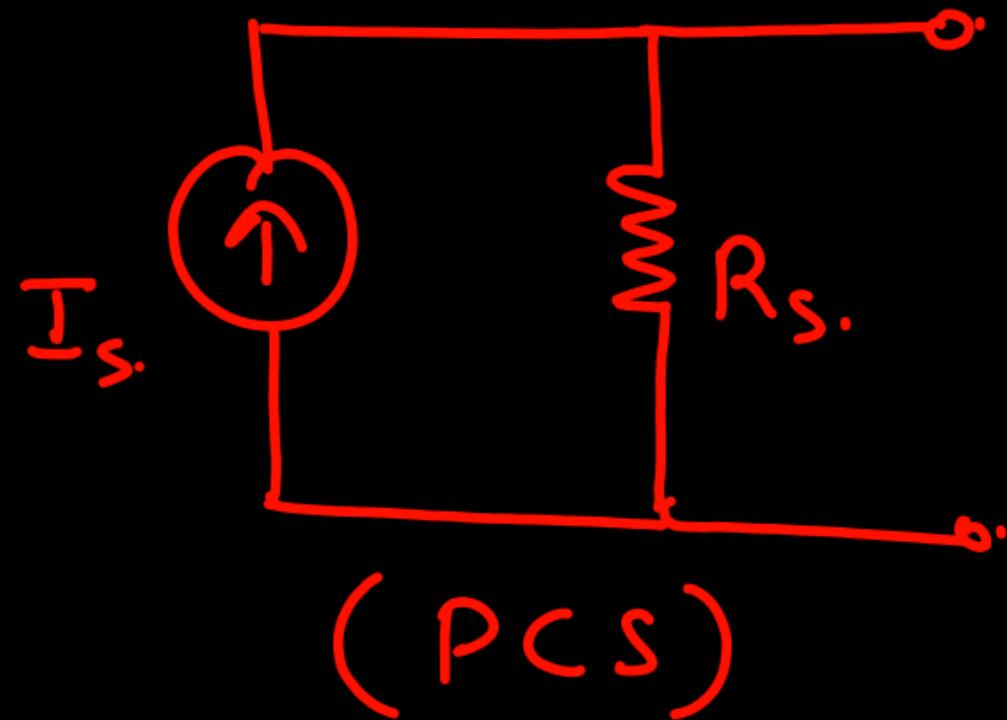- Hence a Practical current Source is equivalent of Norton Model.





- Hence from PVS & PCS modelling, we can say.

$$\left[I_{SC} = I_s = I_N = \frac{V_{th}}{R_{th}} = \frac{V_s}{R_s} \right] \rightarrow (P)$$

• $[V_{oc} = V_{th} = V_s = I_s R_s = I_{sc} \cdot R_{th} = I_N \cdot R_N]$ P.W.



Hence,

Case-I if we have PVS.

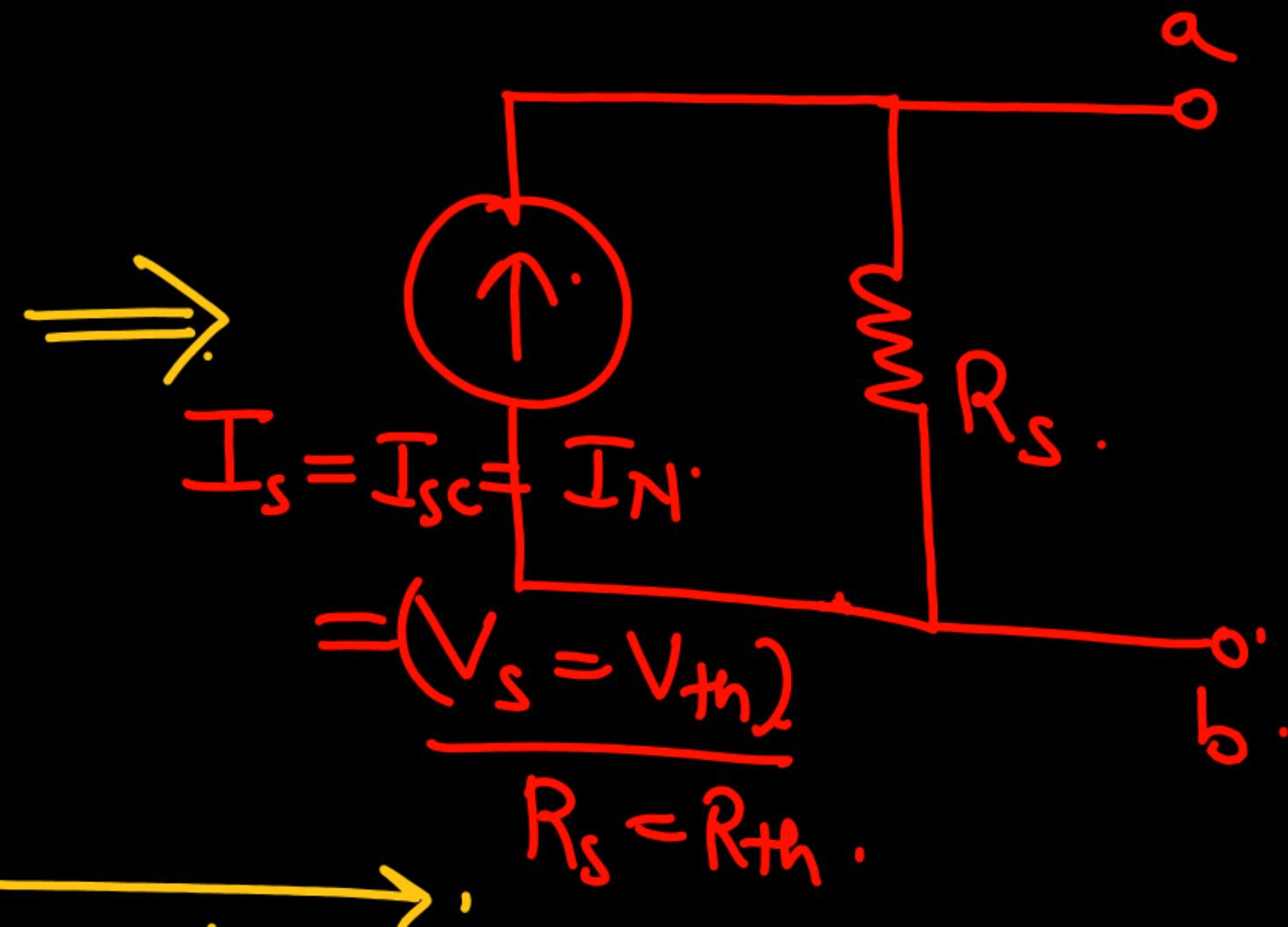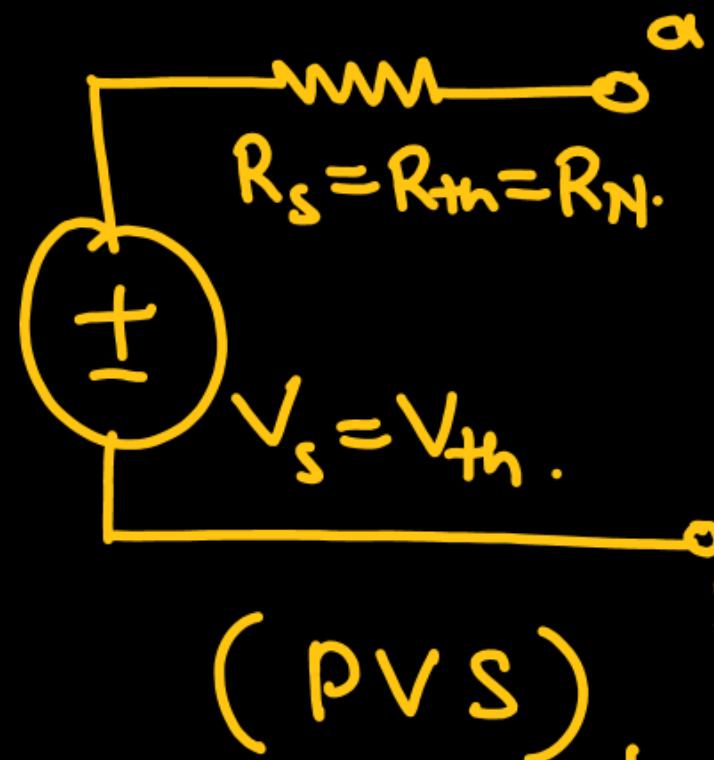

(Source transformation).


Case-II if we have PCS:


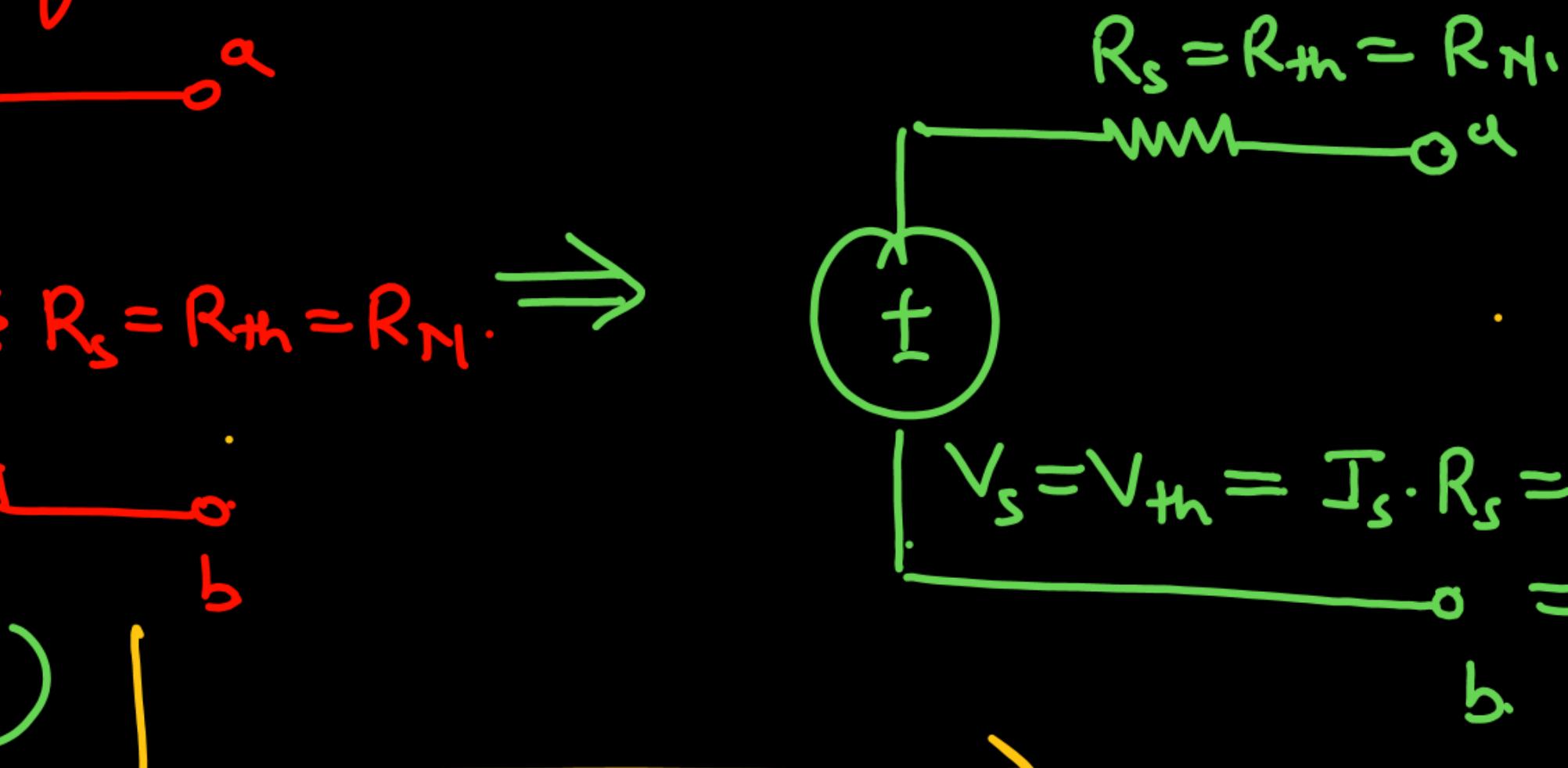
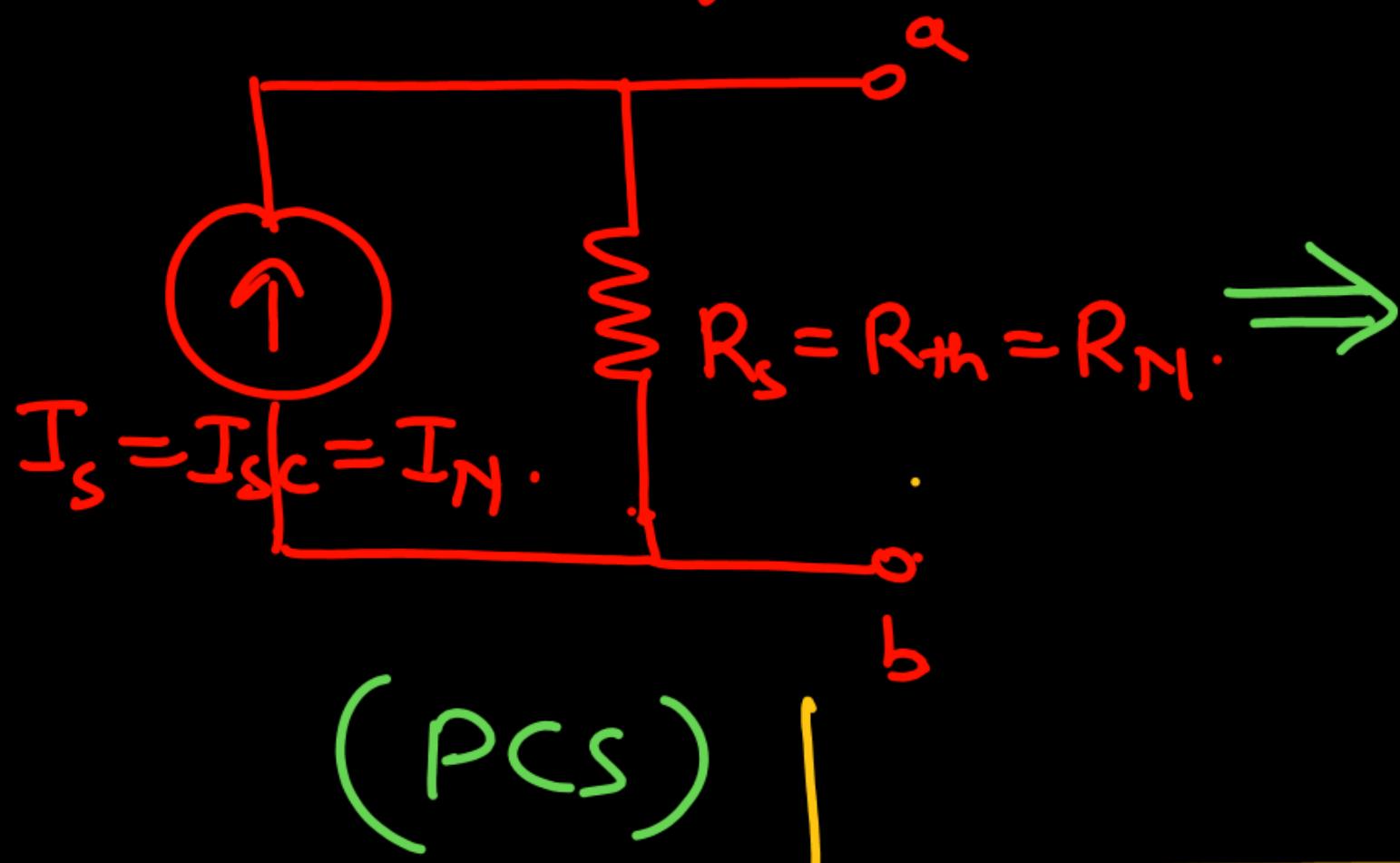


(Source transformation).

②

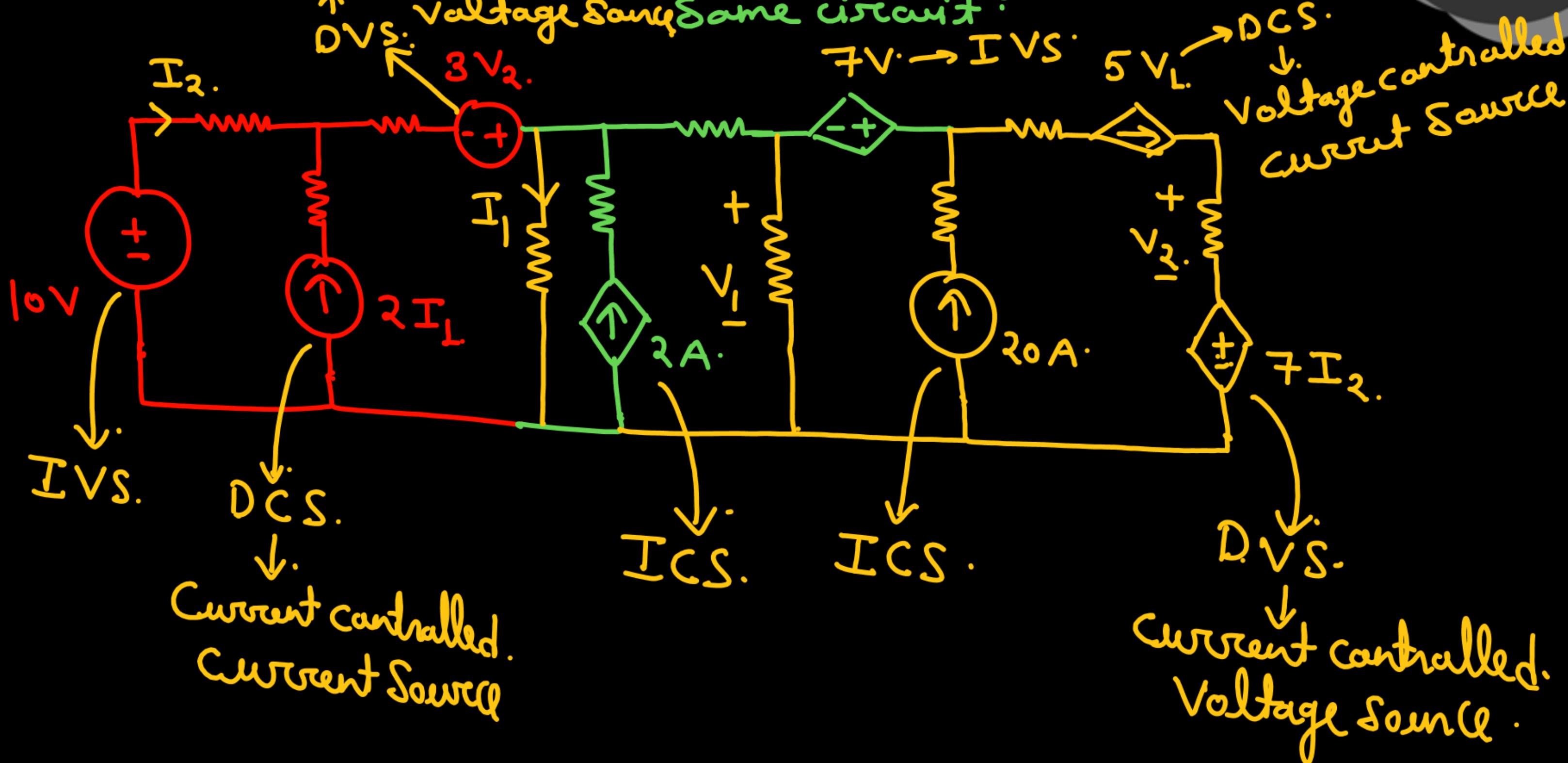Dependent Sources: The source which depends upon other.
Voltage controlled Branch voltage & current in the same circuit.




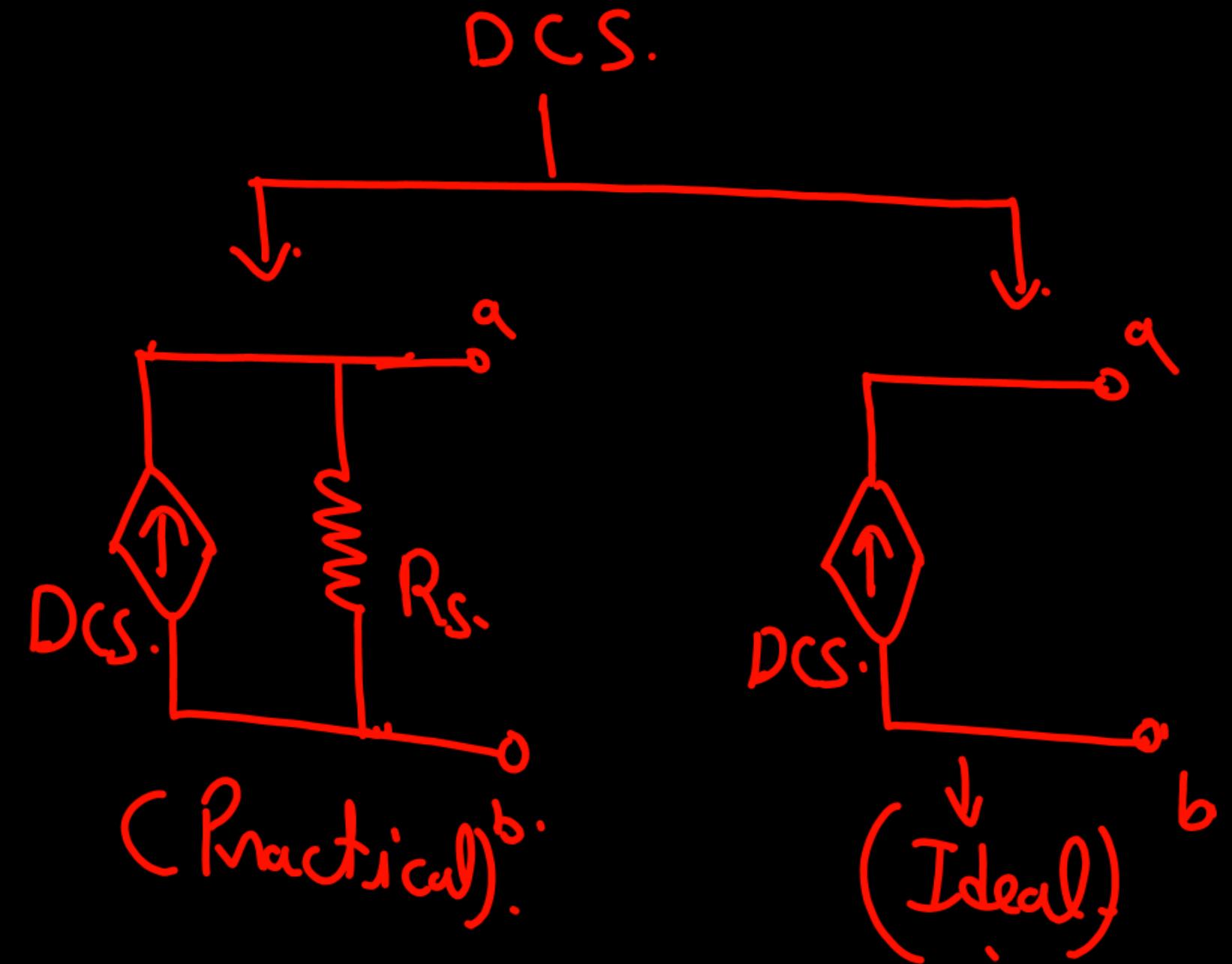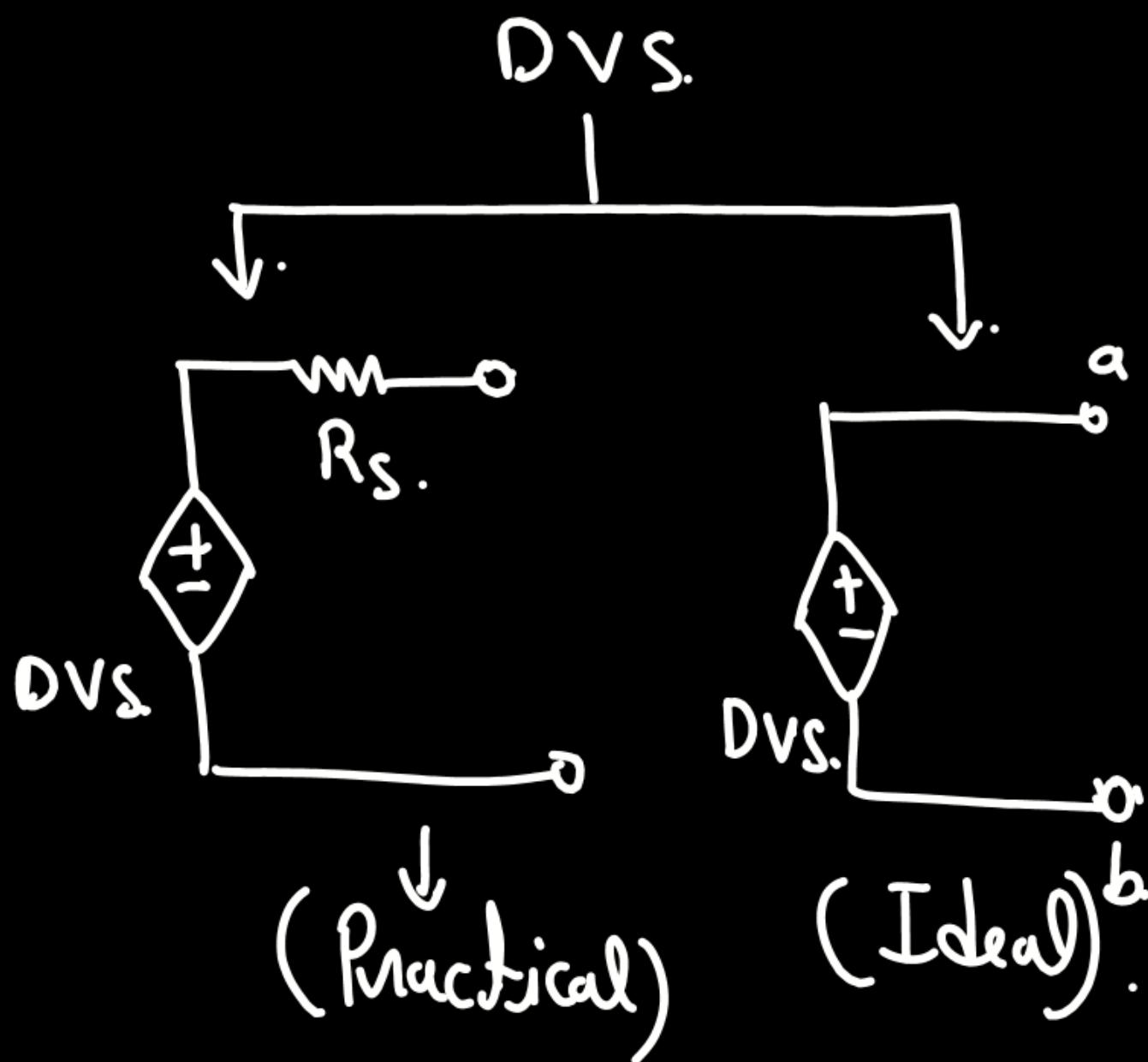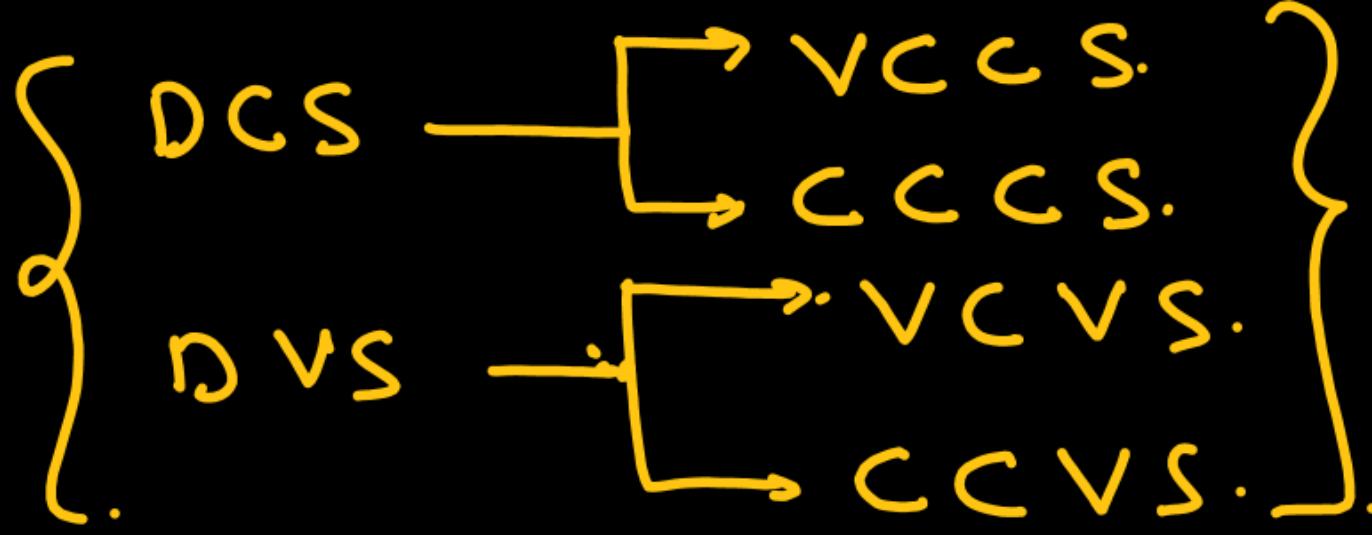

Note! (Always Remember).




(1) Short cut condition:

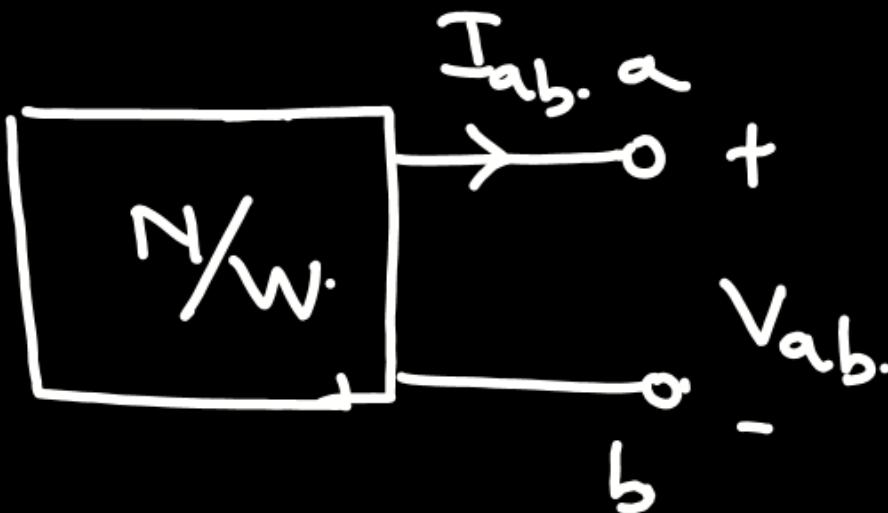


$V_{ab} = 0V$ (Always).

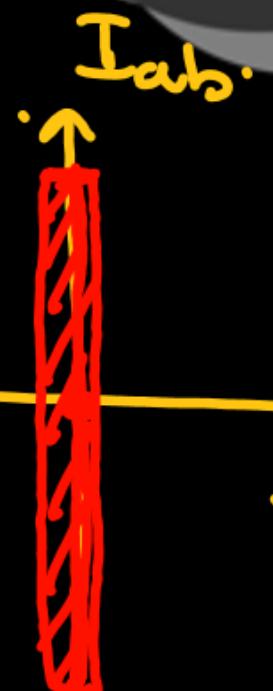$I_{ab} \Rightarrow$ anything ($0, +, -$).




(2) Open-circuit condition:

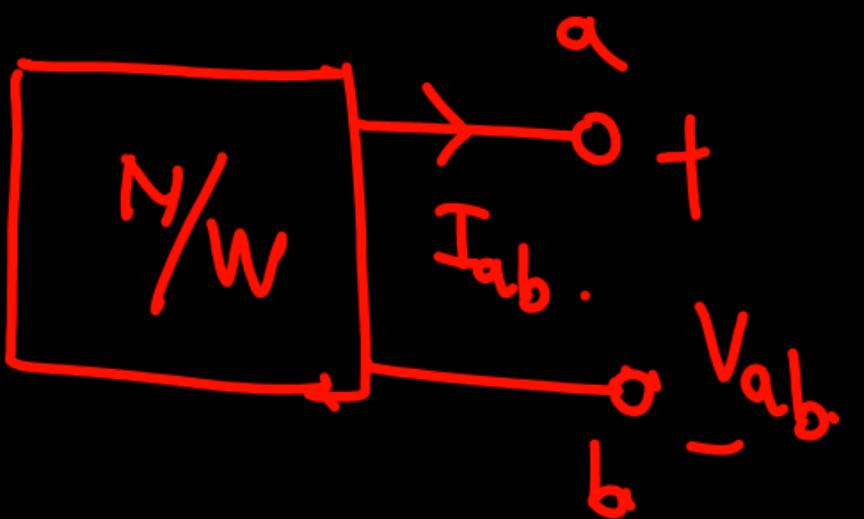


$I_{ab} = 0A$ (Always).

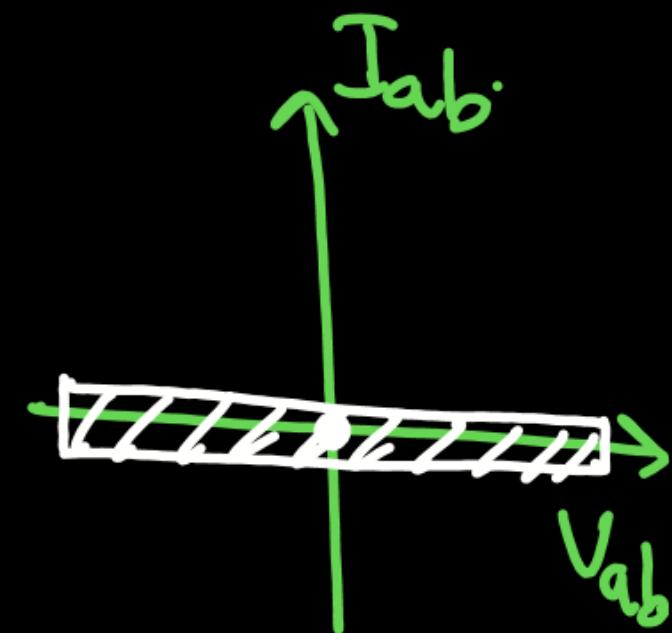$V_{ab} \Rightarrow$ Anything ($0, +, -$).



③ If in any Question, at 'ab' terminal.

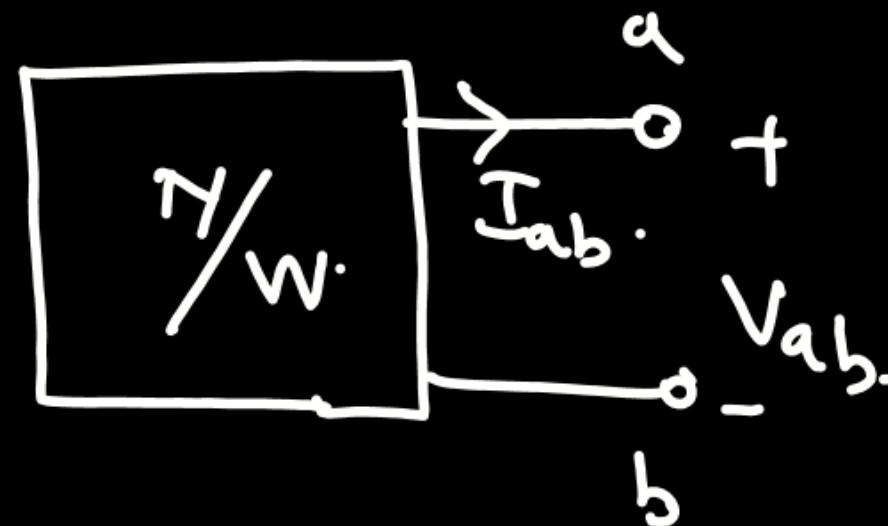
$$[V_{ab} = 0V \quad \& \quad I_{ab} = 0A]$$



You have your choice.

(You can short or You can open)

④ Ohm's law:

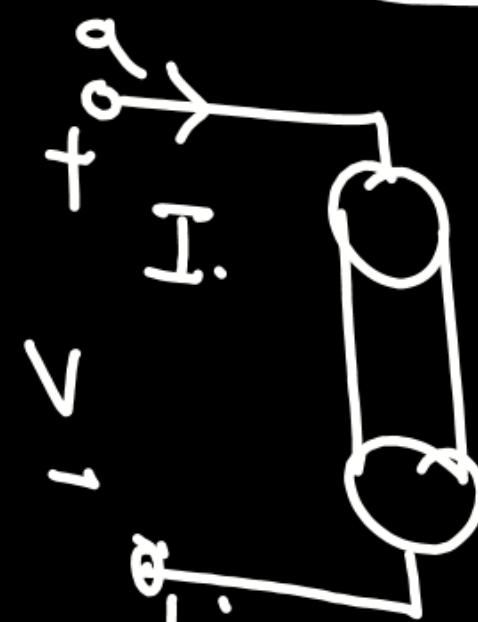

$$V \propto I \quad \text{or} \quad I \propto V$$

$$[V = RI] \quad \text{or.} \quad [I = G \cdot V]$$

$$(G = \frac{1}{R} = \sigma, \quad R \Rightarrow \Omega)$$

Topic-05 (KVL & KCL).




Note: This is the best Possible Numerical Solving technique.

KVL → [Kirschhoff's voltage law]

- In any loop or in any closed Path.
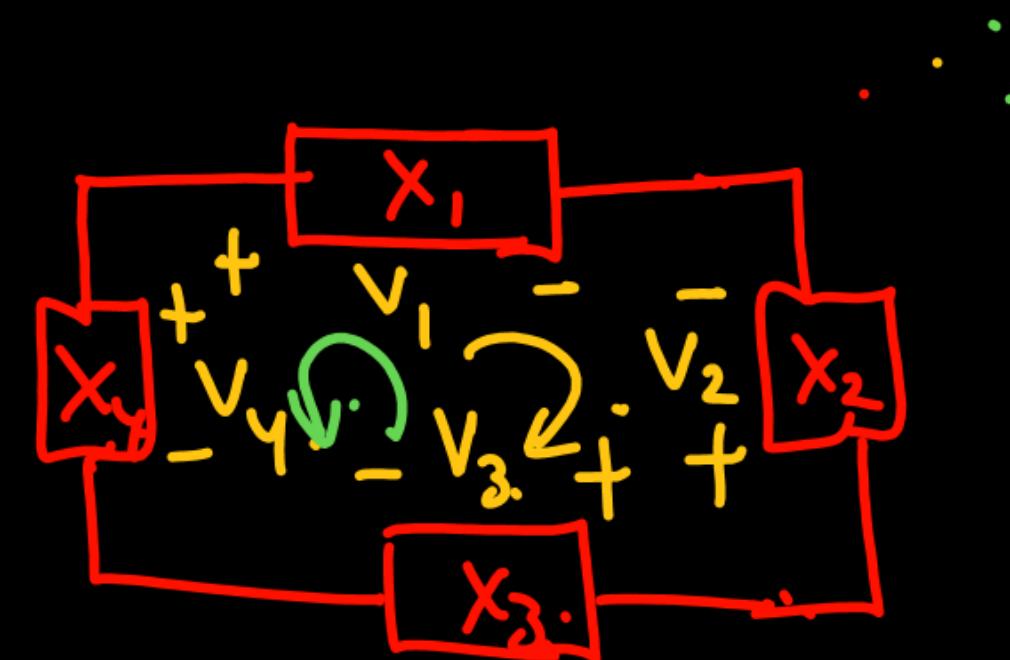
$$\left[\sum V_{\text{loop}} = 0 \right]$$



• In a loop,

$$\sum V_{loop} = 0V$$

• $\left[\sum V_{rise} = -\sum V_{drop} \right]$

{
- → + → Voltage rise.
+ → - → Voltage drop.

Step-1. choose one.

Direction.

Clockwise or.

Anticlockwise.

Case-I clockwise.

$$V_1 + V_3 = V_2 + V_4 \checkmark$$

V_{drop}

$$V_1 + V_3 = V_2 + V_4 \checkmark$$

V_{rise}.

$$\boxed{V_1 + V_3 - V_4 - V_2 = 0} \checkmark$$

Case-II Anticlockwise.

$$\underbrace{V_1 + V_3}_{\downarrow} = \underbrace{V_2 + V_4}_{\downarrow} \checkmark$$

V_{rise} V_{drop}

$$\boxed{V_1 + V_3 - V_2 - V_4 = 0} \checkmark$$

KCL \rightarrow (Kirchhoff's current law).

- At any node,

$$\left[\sum I_{\text{node}} = 0 \right]$$

↓.

$$\left[\sum I_{\text{incoming}} = \sum I_{\text{outgoing}} \right]$$



$$I_2 + I_3 = I_1 + I_4$$

$$\left[I_1 + I_4 - I_2 - I_3 = 0 \right]$$

(How to Solve Numericals of Chapter-01).

Step-01.

.....





Thank you
GW
Soldiers!

