

Electrical Engineering



Electronics and Communication Engineering

Instrumentation Engineering



Network Theory

Lecture No. 06

Basics of Network Theory



By- Pankaj Shukla sir



Recap of Previous Lecture

1. Series & Parallel operation.
- 2.
- 3.
- 4.
- 5.
- 6.



Topics to be Covered

1. Previous Continue.
2. Question Discussion.
- 3.
- 4.
- 5.
- 6.


②


Parallel operation of Voltage Sources:

(a)

Ideal Sources: Here the ideal voltage sources.

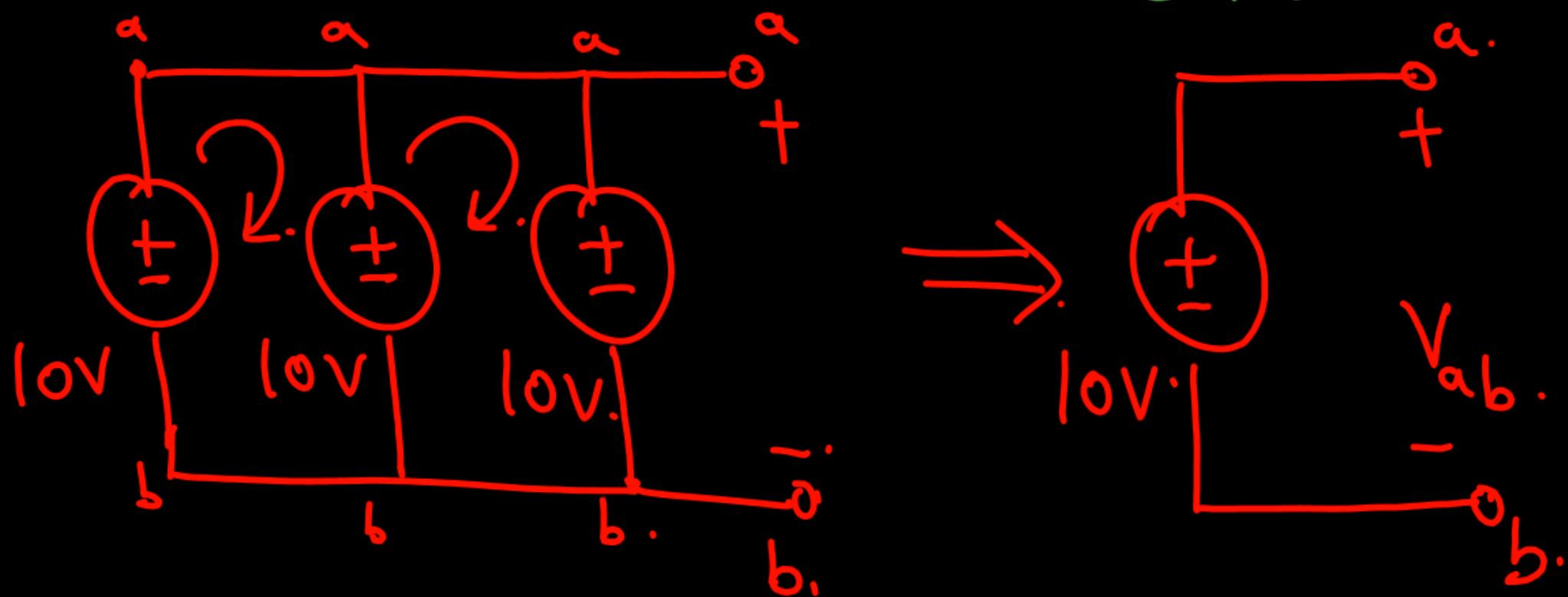
having same magnitude & same polarity can only be parallelly operated. if it is not satisfying i.e means KVL is failed. Hence cut will become invalid.



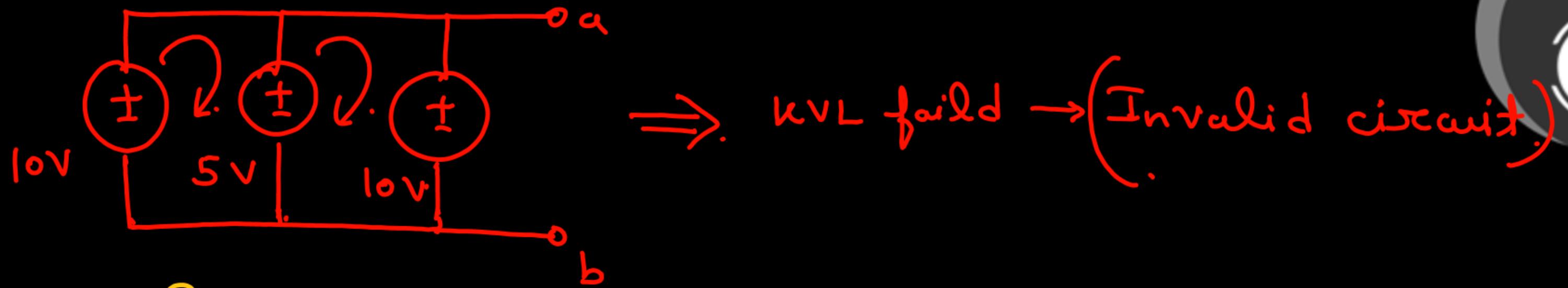

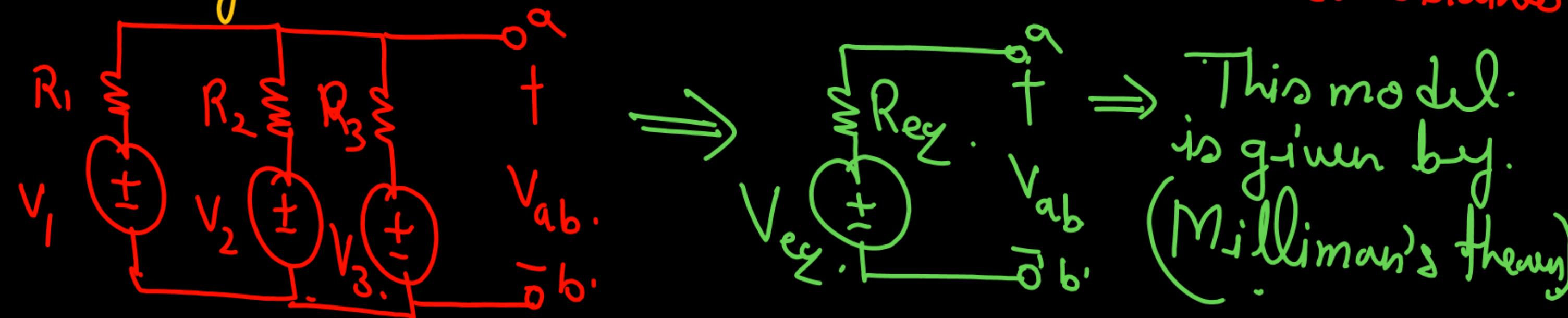
(b) Practical voltage sources:

- Hence there is no such condition as we have discussed in case of parallel operation of ideal voltage sources. Hence here there is no constraints.





③ Parallel operation of current sources:

- Simply apply KCL that's it.

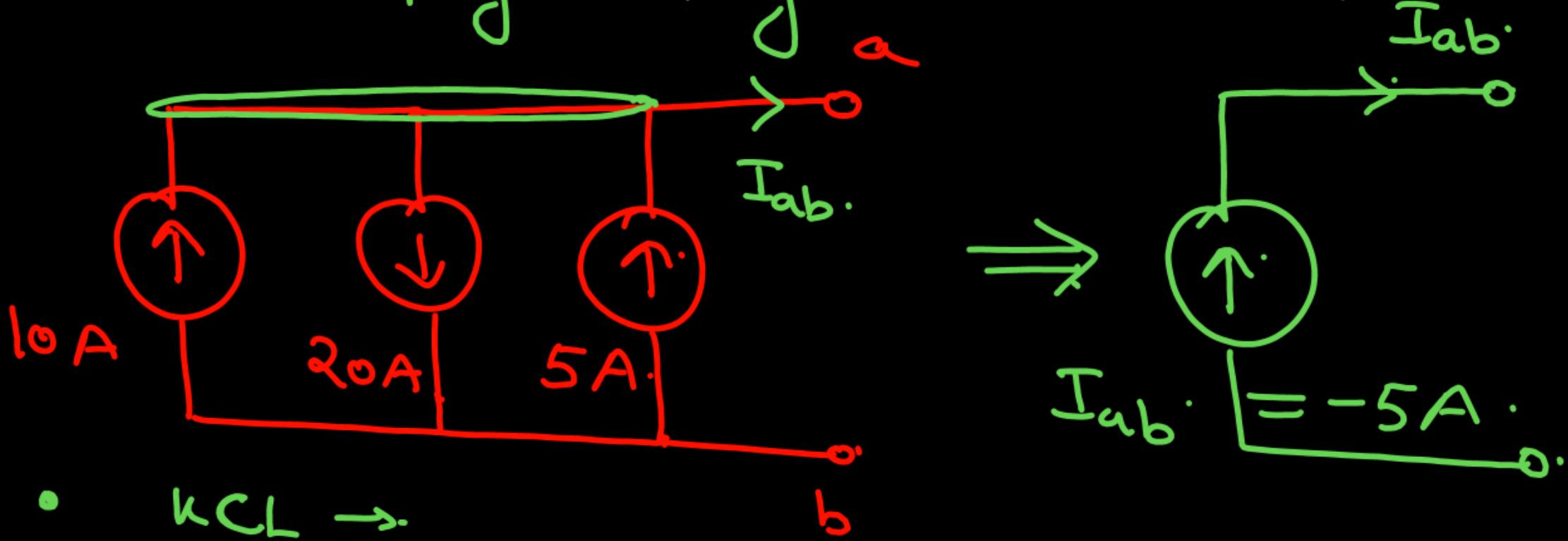

- KCL \rightarrow
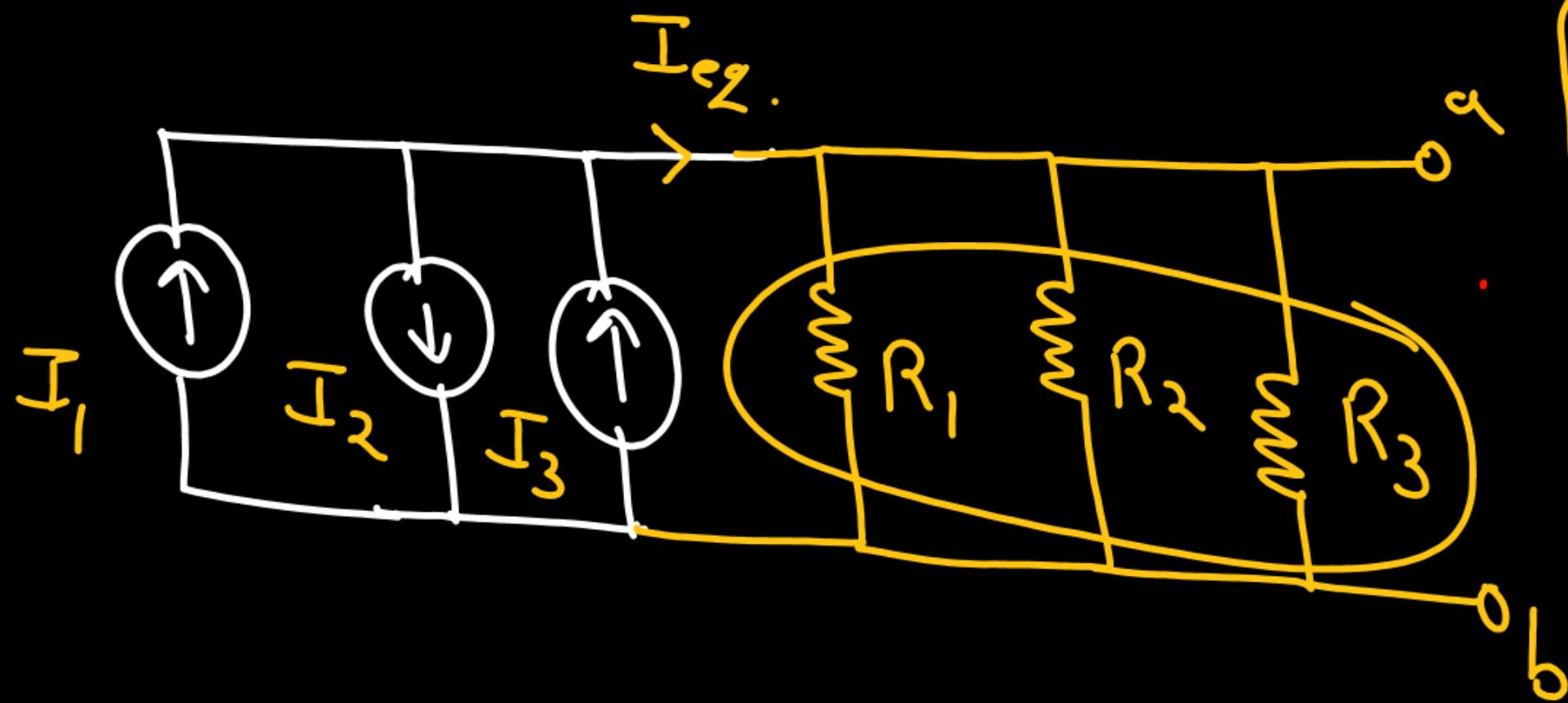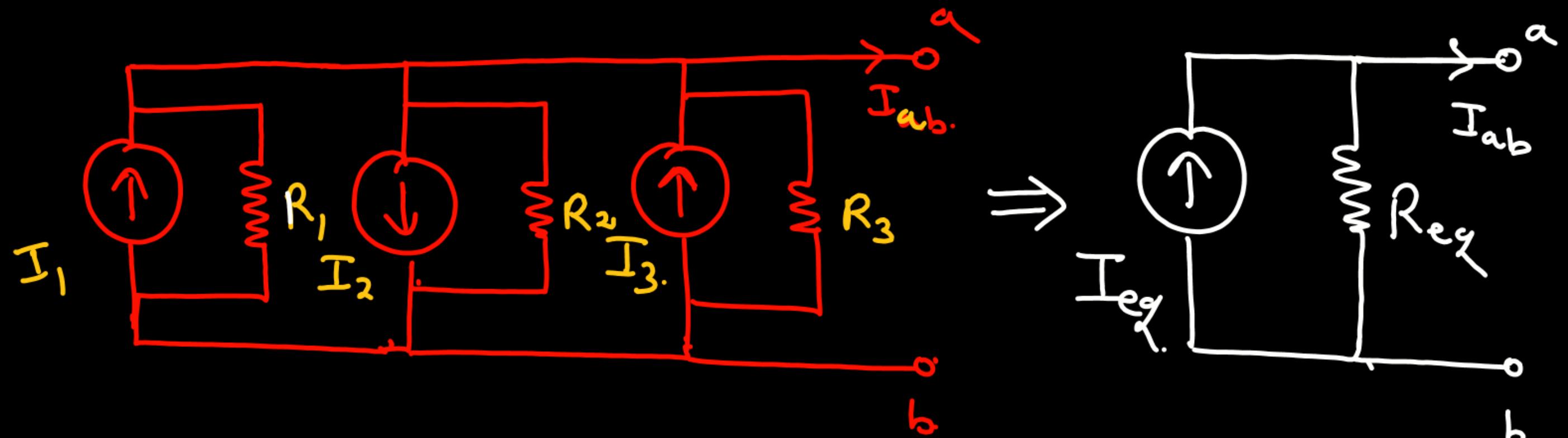
$$10 + 5 = 20 + I_{ab} \\ [I_{ab} = 15 - 20 = -5 \text{ A}]$$



$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$I_{eq} + I_2 = I_1 + I_3$$

$$I_{eq} = I_1 + I_3 - I_2$$

Note: Inspection Method \rightarrow O2.

Here Now,

Inspection method - O2 = (I.M - O1) + Series t.


Parallel operation

Question

Find the value of V_x & I_x in the Below circuit.


(Inspection Method)

$$I_x = 10 \Omega$$

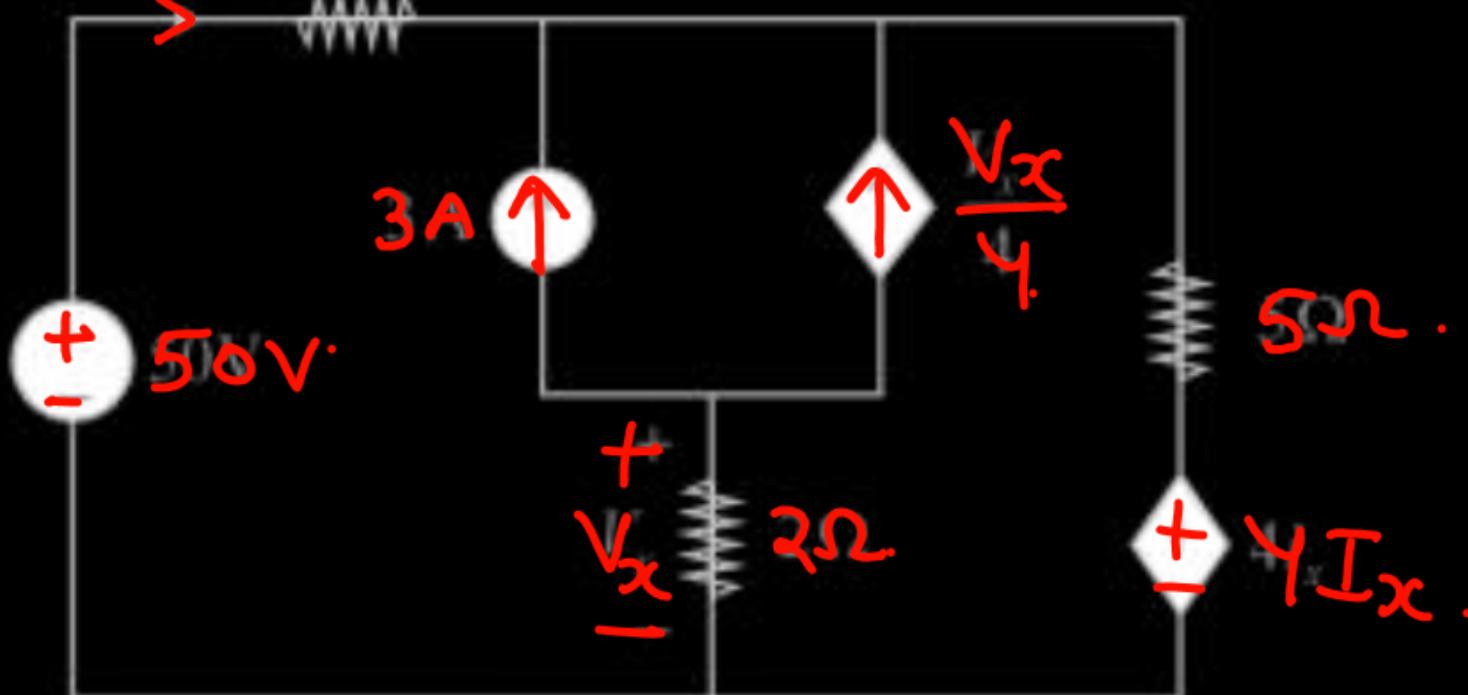

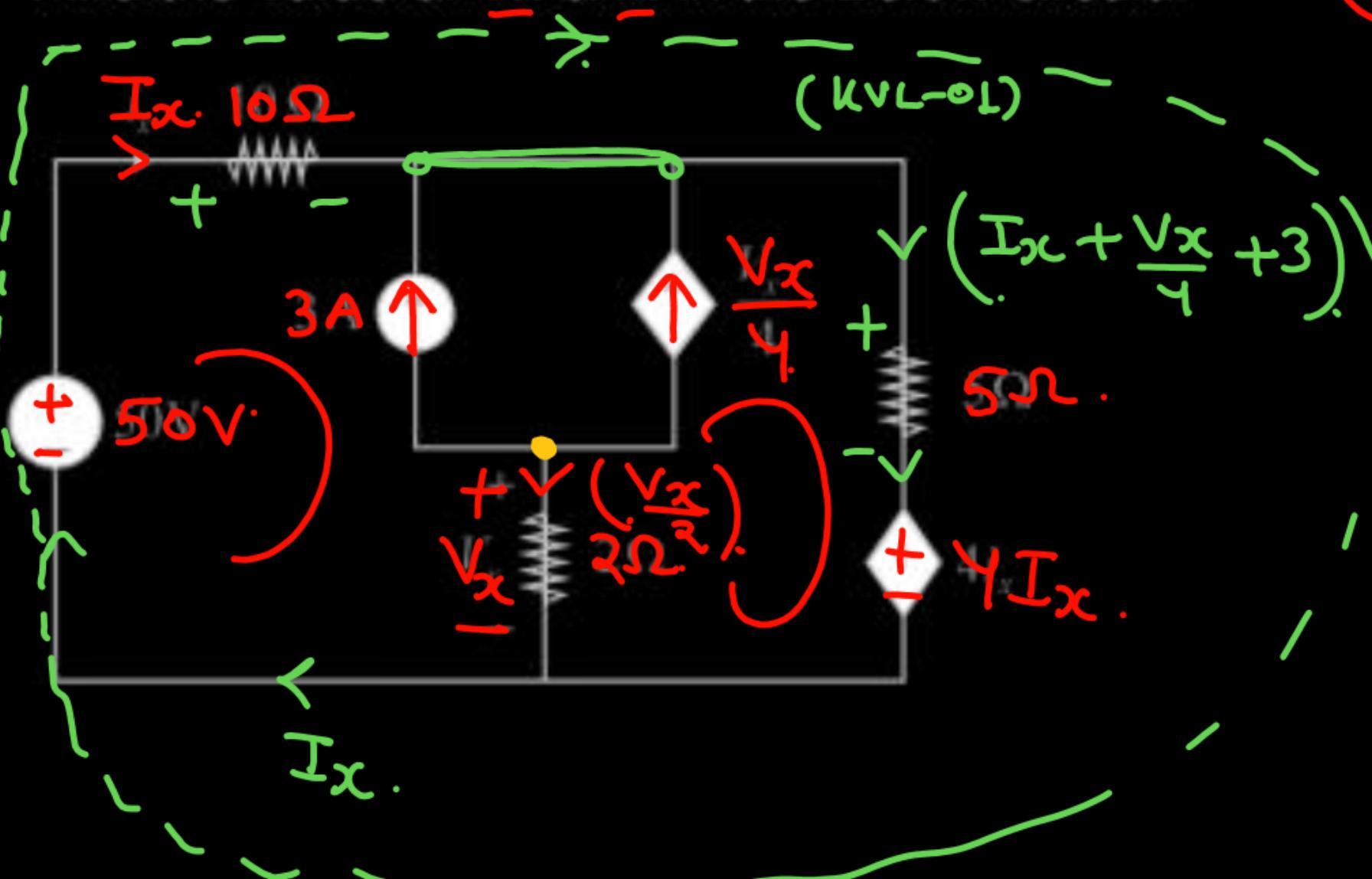Question

Find the value of V_x & I_x in the Below circuit.



(Inspection Method)

• KVL - OL.

$$10I_x + 5 \times (I_x + \frac{V_x}{4} + 3) + 4I_x = 50$$

$$19I_x + \frac{5}{4}V_x = 35$$

$$[19 \times 4 I_x + 5V_x = 140] \rightarrow \textcircled{1}$$

$$3 + \frac{V_x}{4} + \frac{V_x}{2} = 0 \quad \left| \begin{array}{l} V_x = -12 \\ \hline \end{array} \right.$$

$$\begin{aligned} V_x \left(\frac{1}{4} + \frac{1}{2} \right) &= -3. \quad \left| \begin{array}{l} V_x = -4 \text{ Volts} \\ \hline \end{array} \right. \\ V_x \left(\frac{1}{4} + 2 \right) &= -3. \end{aligned}$$

From eqn (1)

$$19 \times 4 I_x + 5 \times (-4) = 140$$

$$19 \times 4 I_x = 140 + 20 = 160$$


$$\left[I_x = \frac{160}{19 \times 4} = 2.1052 \text{ A} \right]$$

Question



Find the current "I" & Power Delivered by 2 A current source.


{ Inspection Method }

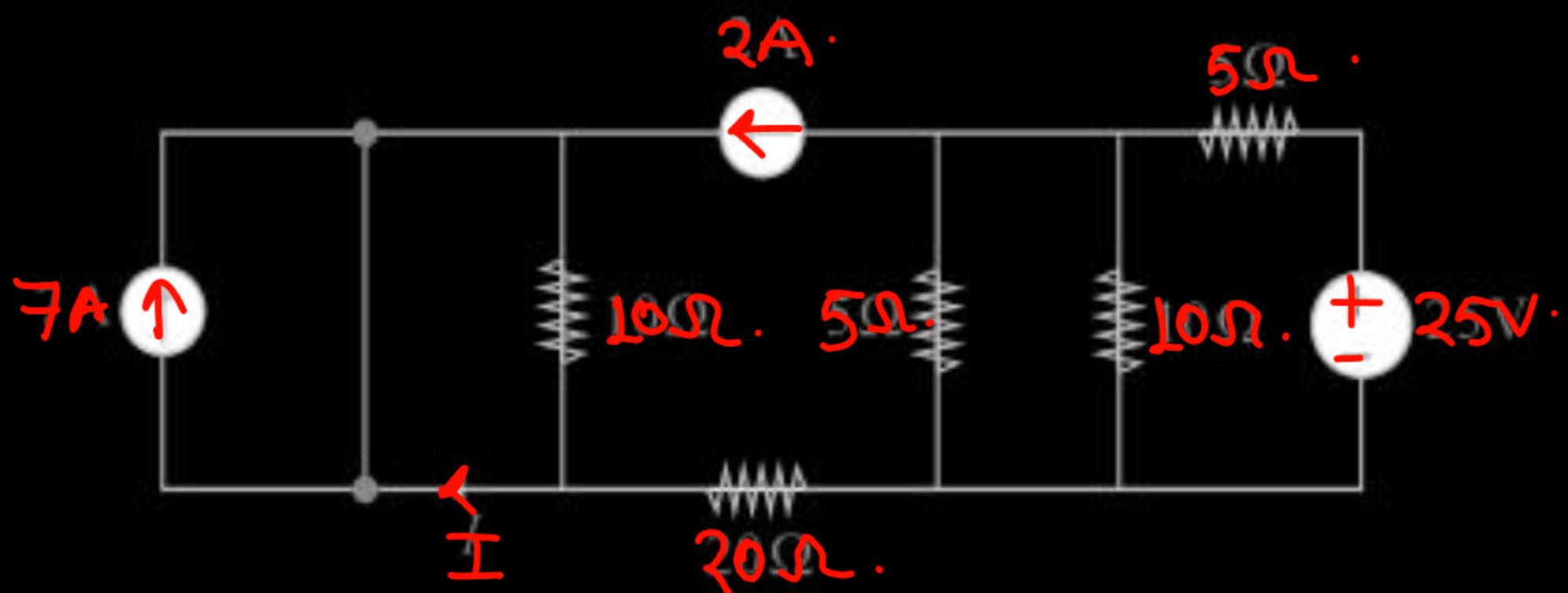

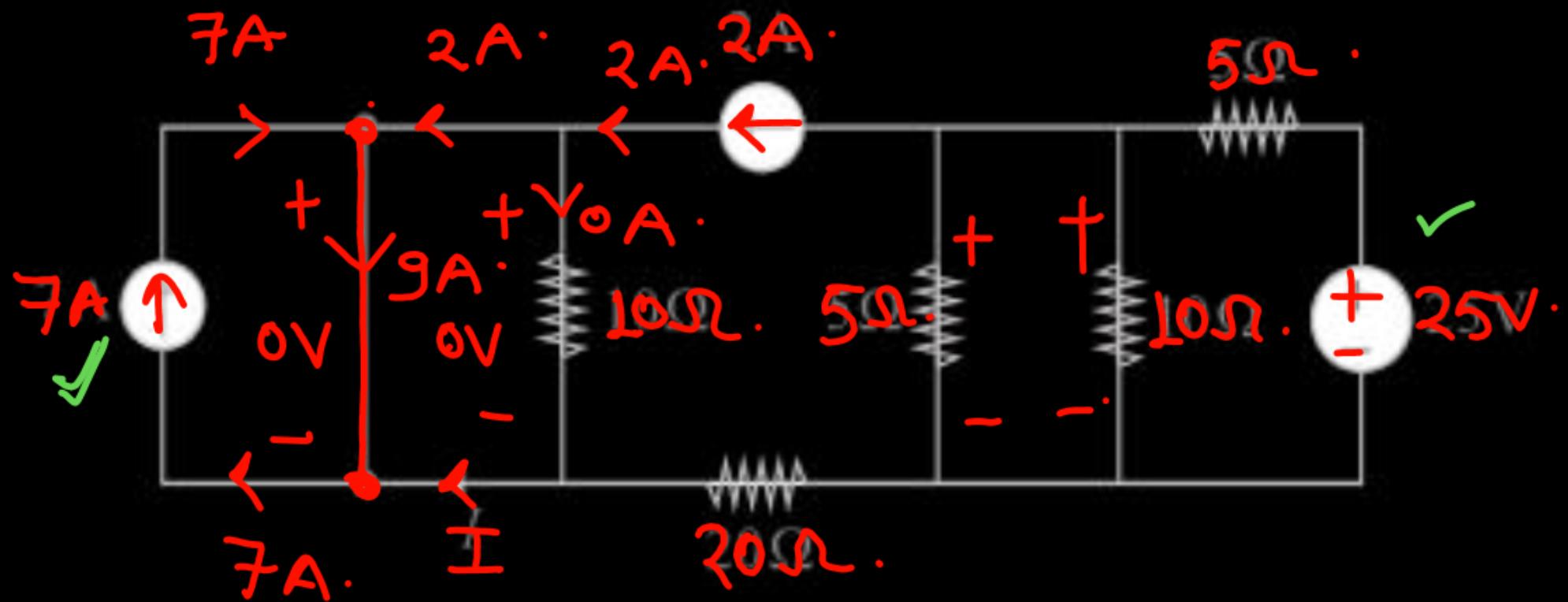Question



Find the current "I" & Power Delivered by 2 A current source.




$$\begin{aligned} \bullet \quad I + g &= 7 \\ [I = 7 - g &= -2A] \end{aligned}$$

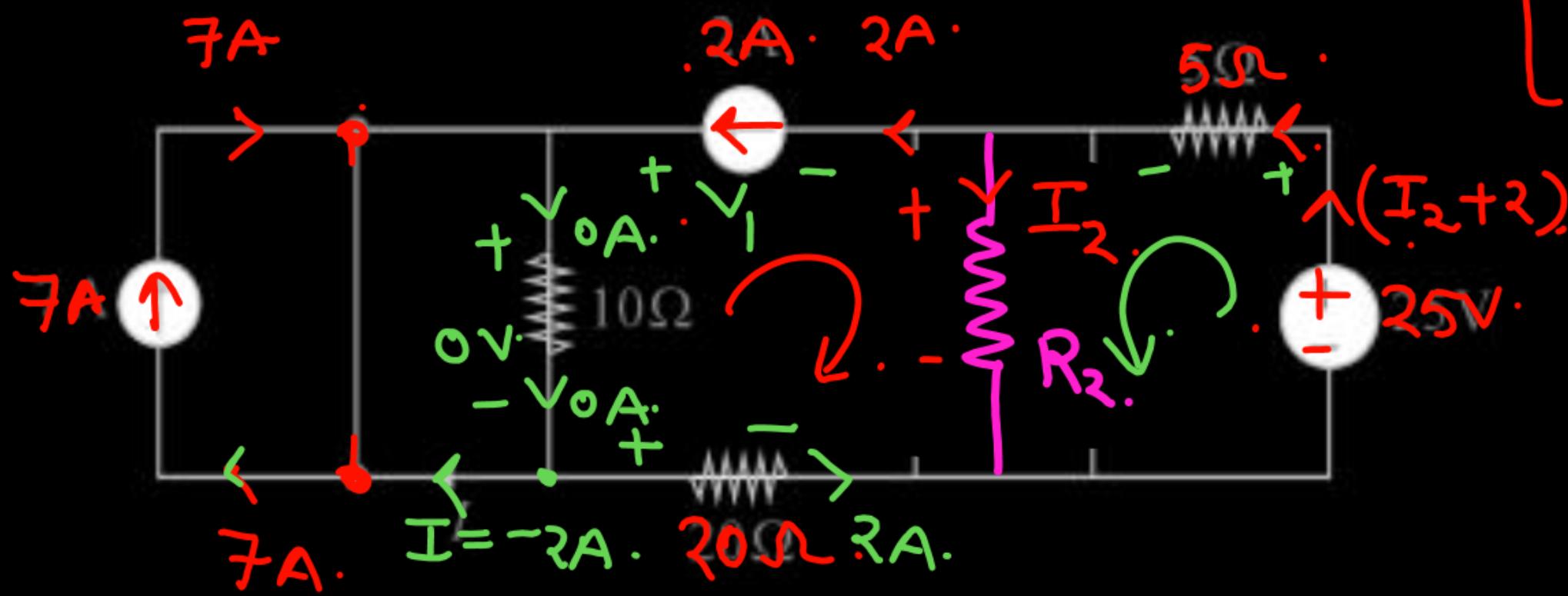Question



Find the current "I" & Power Delivered by 2 A current source.



$$R_2 = \frac{10 \times 5}{15} = \frac{10}{3} \Omega$$

$$5 \times (I_2 + 2) + \frac{10}{3} \times I_2 = 25$$

$$I_2 \left(5 + \frac{10}{3} \right) = 25 - 10$$

$$I_2 \times \left(\frac{25}{3} \right) = 15$$

$$\left[I_2 = \frac{15 \times 3}{25} = 1.8 \text{ A} \right]$$

$$20 \times 2 = V_1 + I_2 \times \frac{10}{3}$$

$$\left[3V_1 + 10I_2 = 20 \times 2 \times 3 \right] \quad (1)$$

From eqn (1).

$$[V_1 = \frac{40 \times 3 - 10 \times 1.8}{3} = 34 \text{ volt}]$$

• $P_{ZA} = V_1 \times 2 = 34 \times 2 = 68 \text{ watt (D).}$


on

$$- 68 \text{ watt (A).}$$

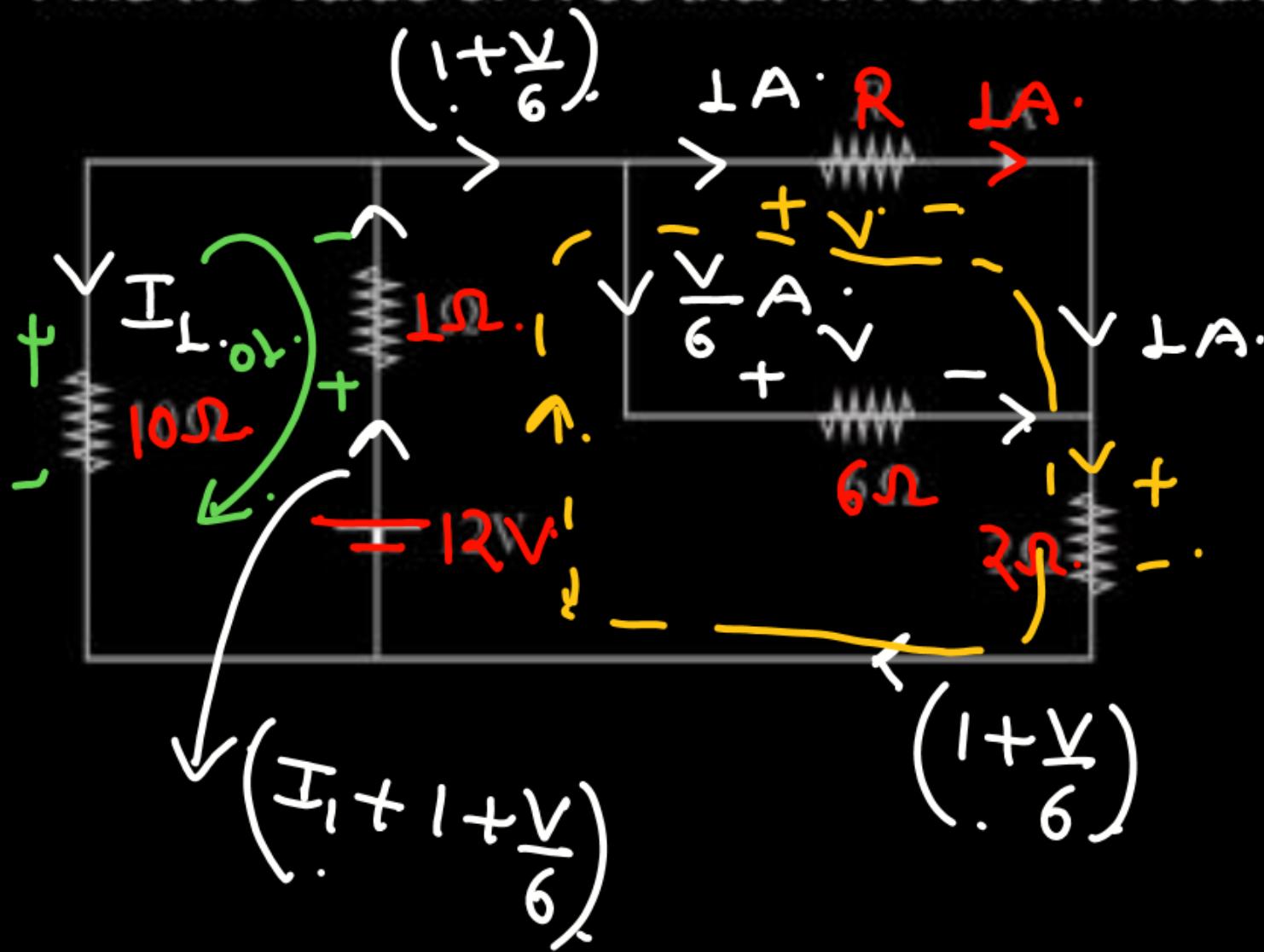Question



Find the value of R so that 1A current would flow in it, for the network shown.



"Inspection Method"

$$[R = \frac{V}{I} = \frac{V}{1}]$$

$$\bullet (kV_L - 0L)$$

$$10I_1 + 1 \times \left(I_1 + 1 + \frac{V}{6} \right) = 1R.$$

$$11I_1 + \frac{V}{6} = 11.$$

$$[66I_1 + V = 66] \rightarrow \textcircled{1}$$

• KVL-02.

$$12 = 2 \times \left(I_1 + L + \frac{V}{6} \right) + V + 2 \times \left(1 + \frac{V}{6} \right)$$

$$I_1 + V \left(\frac{1}{6} + L + \frac{2}{6} \right) = 12 - 3 = 9$$

$$[6I_1 + 9V = 6 \times 9] \quad \text{--- ②}$$

$$\left[R = \frac{V}{L} = 5 \cdot 3877 \right]$$

$$66I_1 + V = 66$$


$$12 \times [6I_1 + 9V = 6 \times 9]$$

$$V \left(L - 12 \times 9 \right) = 66 - 6 \times 9 \times 11.$$

$$\left[V = -\frac{528}{98} = 5.3877 \text{ volt} \right]$$

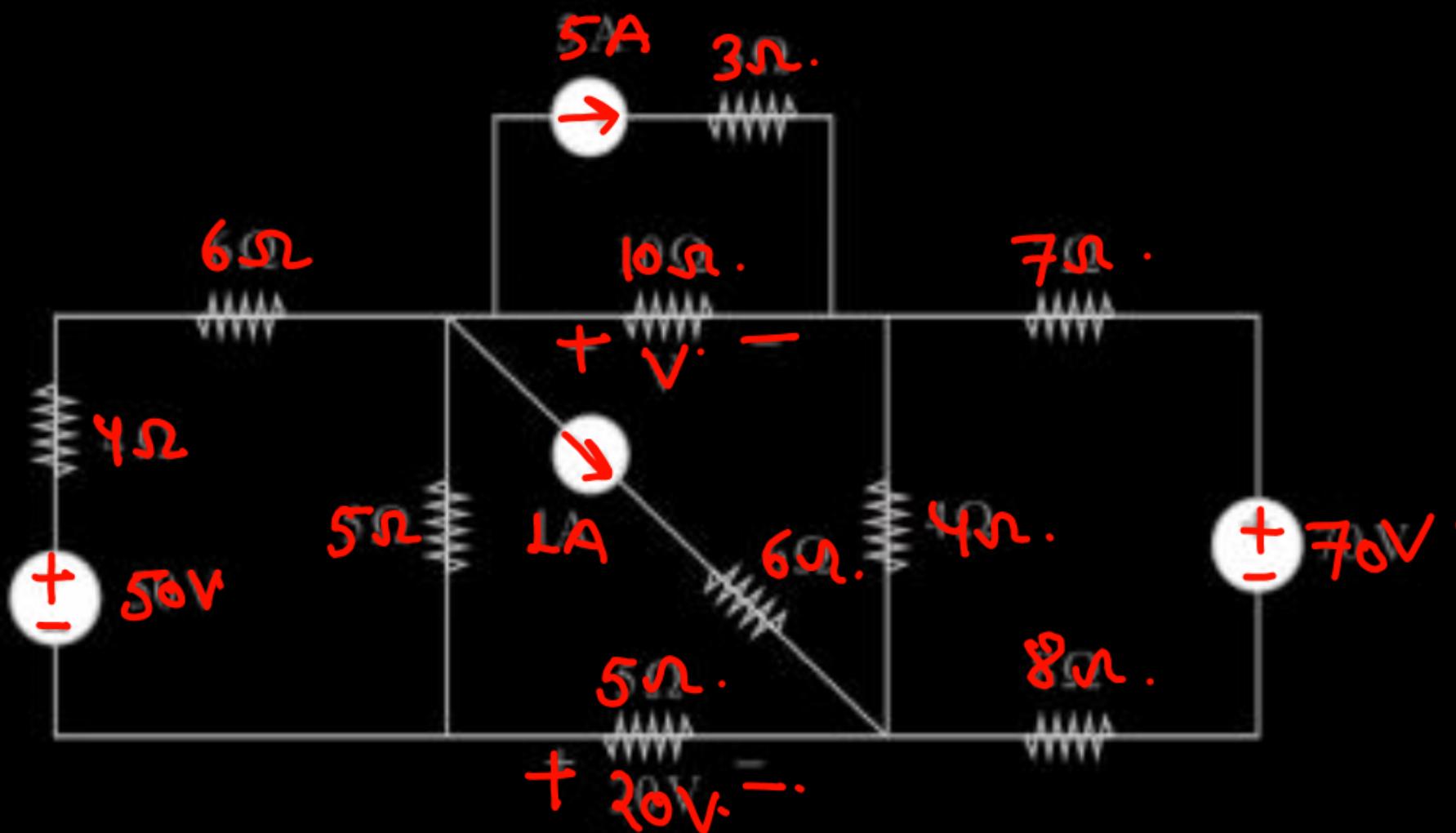Question

In the given circuit, the value of V in volt is _____. • (Inspection Method).




Question

In the given circuit, the value of V in volt is _____.

• (Inspection Method).


$$V = 10 \times (-10) = -100V$$

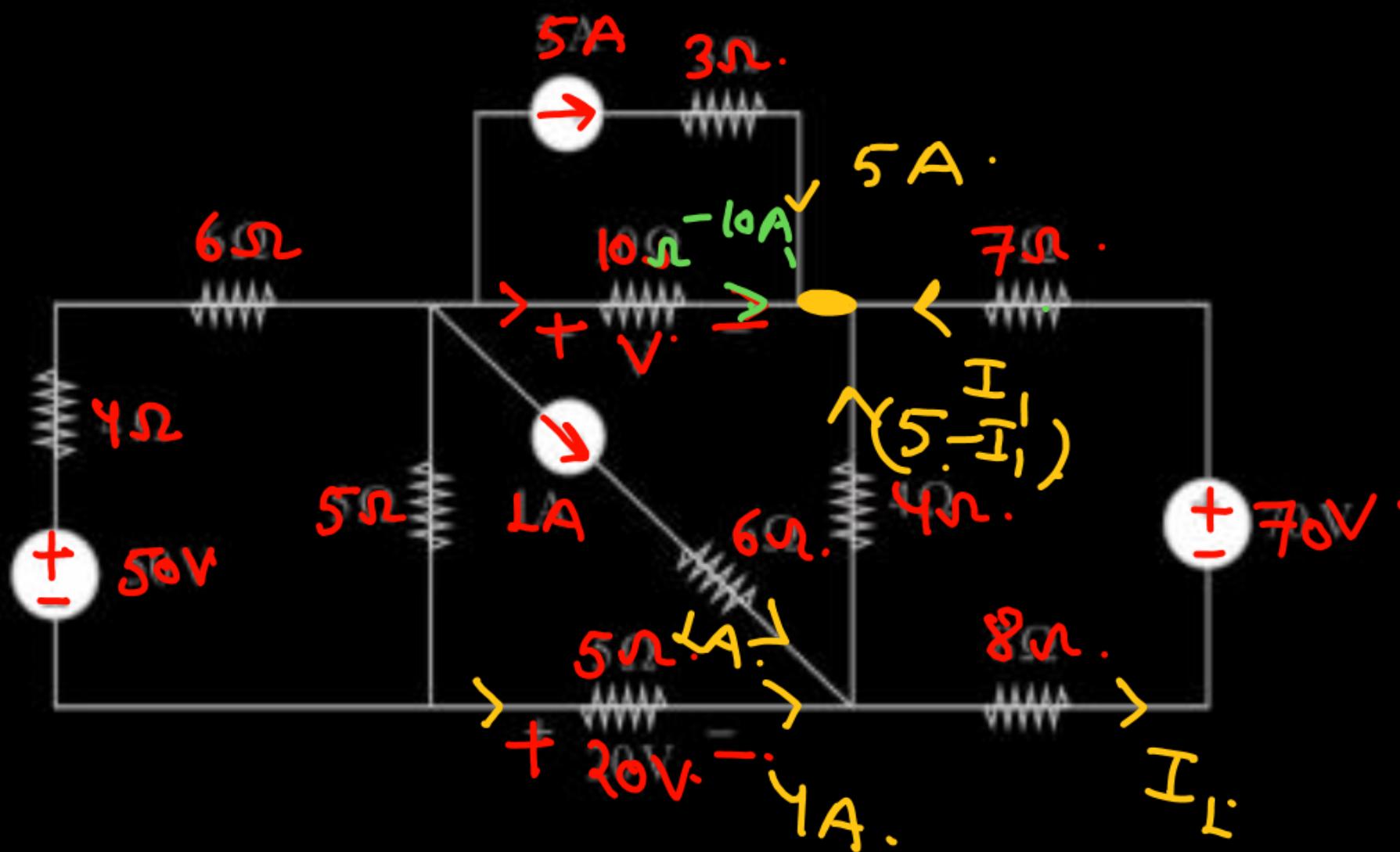

Question


In the given circuit, the value of current flowing in 15 ohm & the power delivered by dependent source will be?

(Inspection Method).

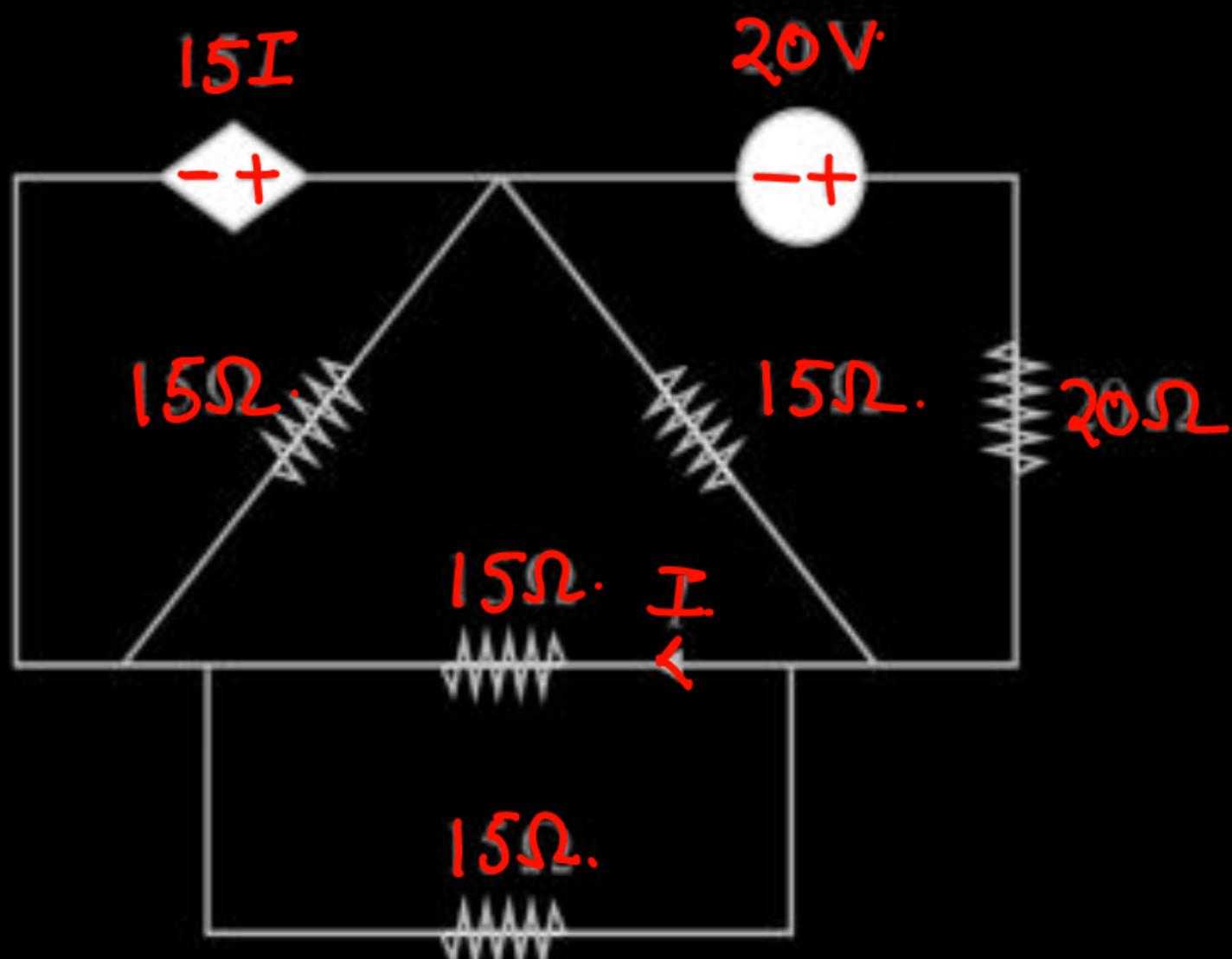

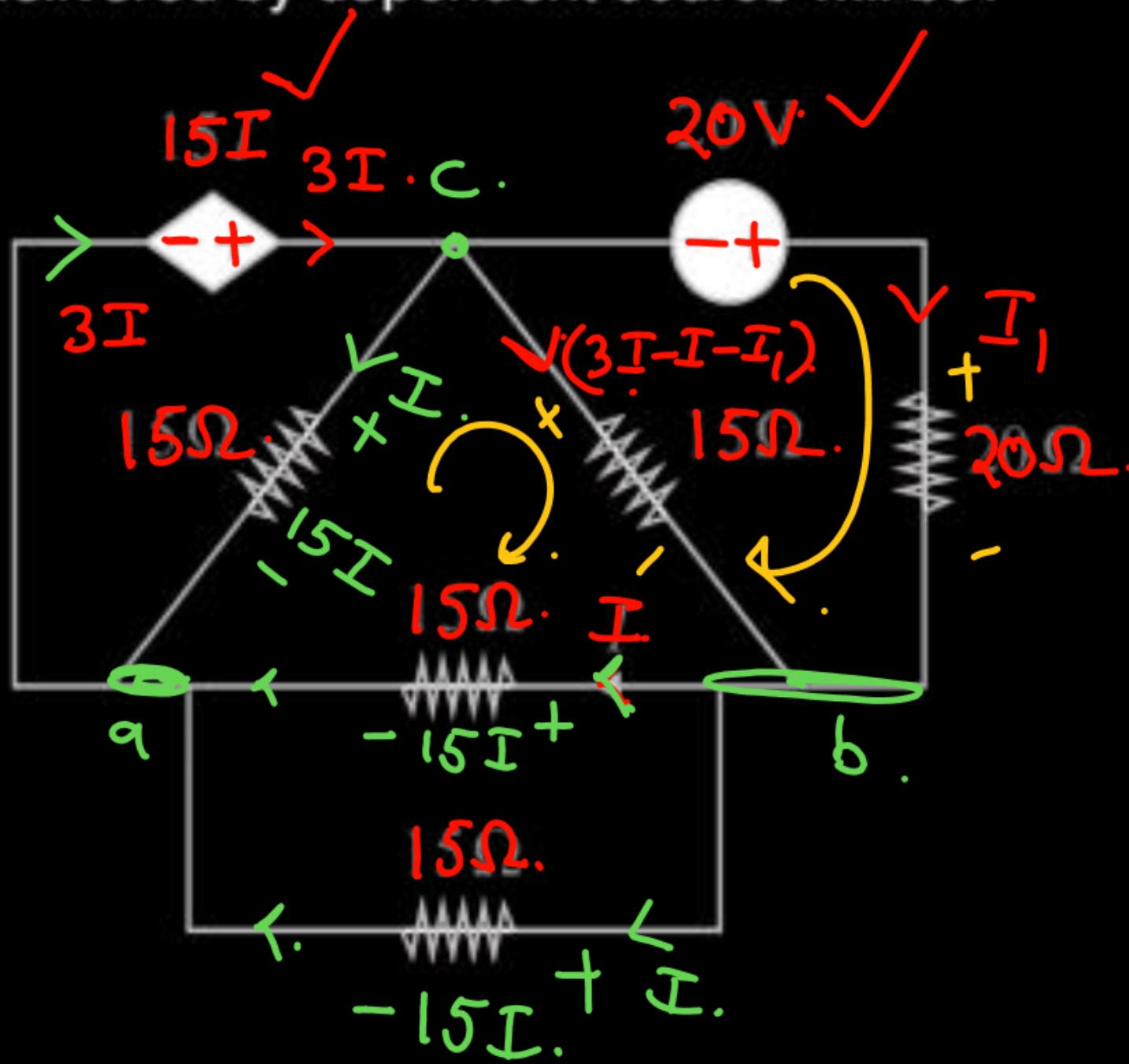Question

In the given circuit, the value of current flowing in 15Ω & the power delivered by dependent source will be?



- $\cancel{15I} = \cancel{15I} + 15 \times (3I - I - I_1)$

$$15 \times (2I - I_1) = 0$$

$$[2I - I_1 = 0] \quad \text{---} \quad I_1$$

- $20I_1 + 15 \times (2I - I_1) = 20$

From eqn (1) & (2).

$$20I_1 + 0 = 20$$

$$[I_1 = 1A]$$

$$2I - I_1 = 0$$

$$(I = 0.5A)$$

$$\begin{aligned}P_{15I} &= (15 \times I) \times (3I) \\&= 15 \times 0.5 \times 3 \times 0.5 = 11.25 \text{ watt (D).} \\&\quad \text{on.} \\&\quad - 11.25 \text{ watt (A).}\end{aligned}$$

Question


H.W.

telegram



The voltage V_y across the resistance is

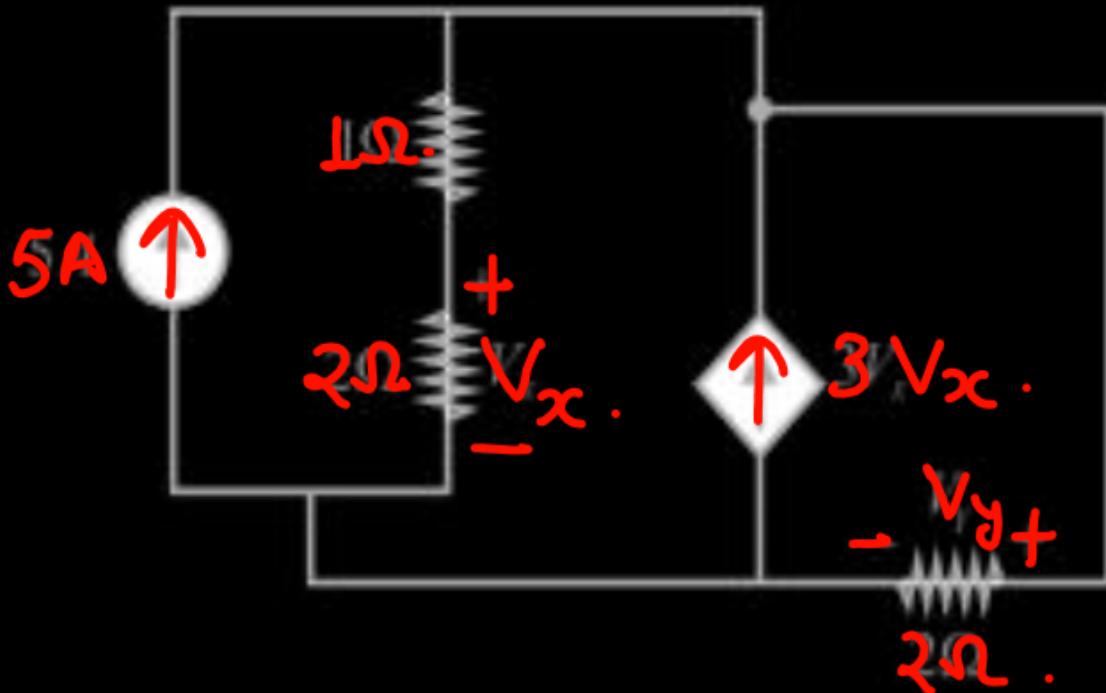- (a) -2V
- (b) -4.28V
- (c) -8.21V
- (d) -10V



pankajshukla@se.pw



Telegram Id



Thank you
GW
Soldiers!

